

Würth Electronics (UK) Ltd



Practical EMI Filter Design Considerations


22 JAN 2018

Presented by

Gopi Patel
Field Application Engineer
Würth Electronics UK


Agenda

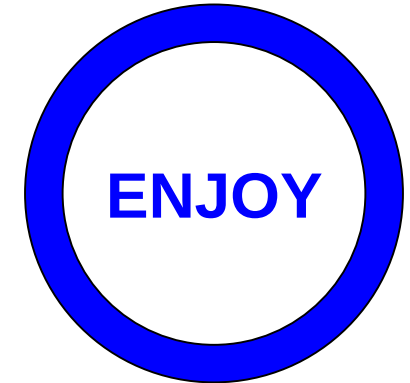- **DC/DC Converter Topologies** – Buck, boost & SEPIC
- **Causes of CM & DM Emissions** – LT Spice
- **Efficiency and Losses** – Core, Copper and AC
- **Criteria for selecting Inductor and Capacitor** – DC Bias
- **Practical Input Filter Design** – LC Filter
- **REDEXPERT** – Interactive component selection




- **DC/DC Converter Topologies** – Buck, boost & SEPIC
- Causes of CM & DM Emissions – LT Spice
- Efficiency and Losses – Core, Copper and AC
- Criteria for selecting Inductor and Capacitor – DC Bias
- Practical Input Filter Design – LC Filter
- REDEXPERT – Interactive component selection

DC to DC Converter Topologies

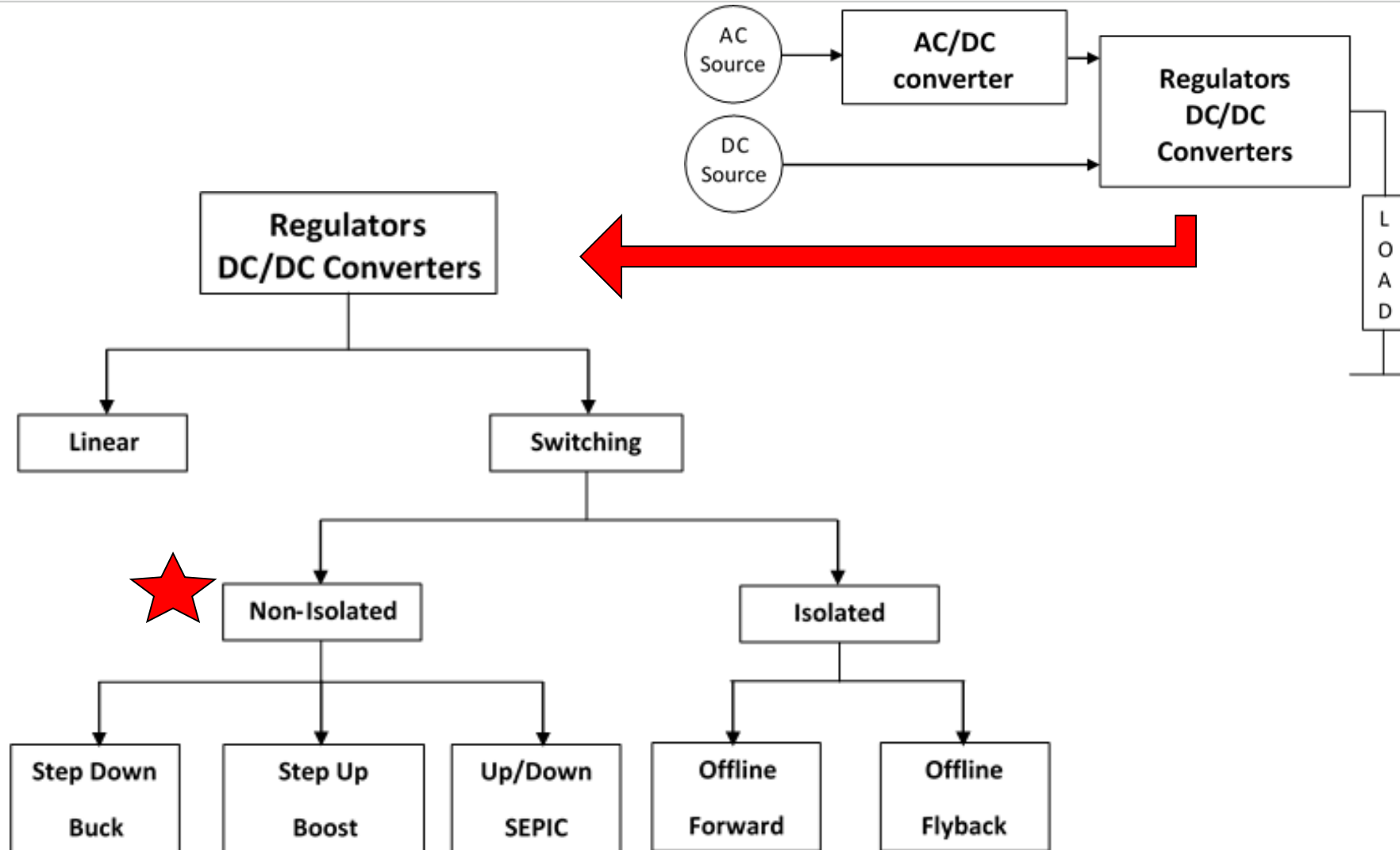


The Buck Converter

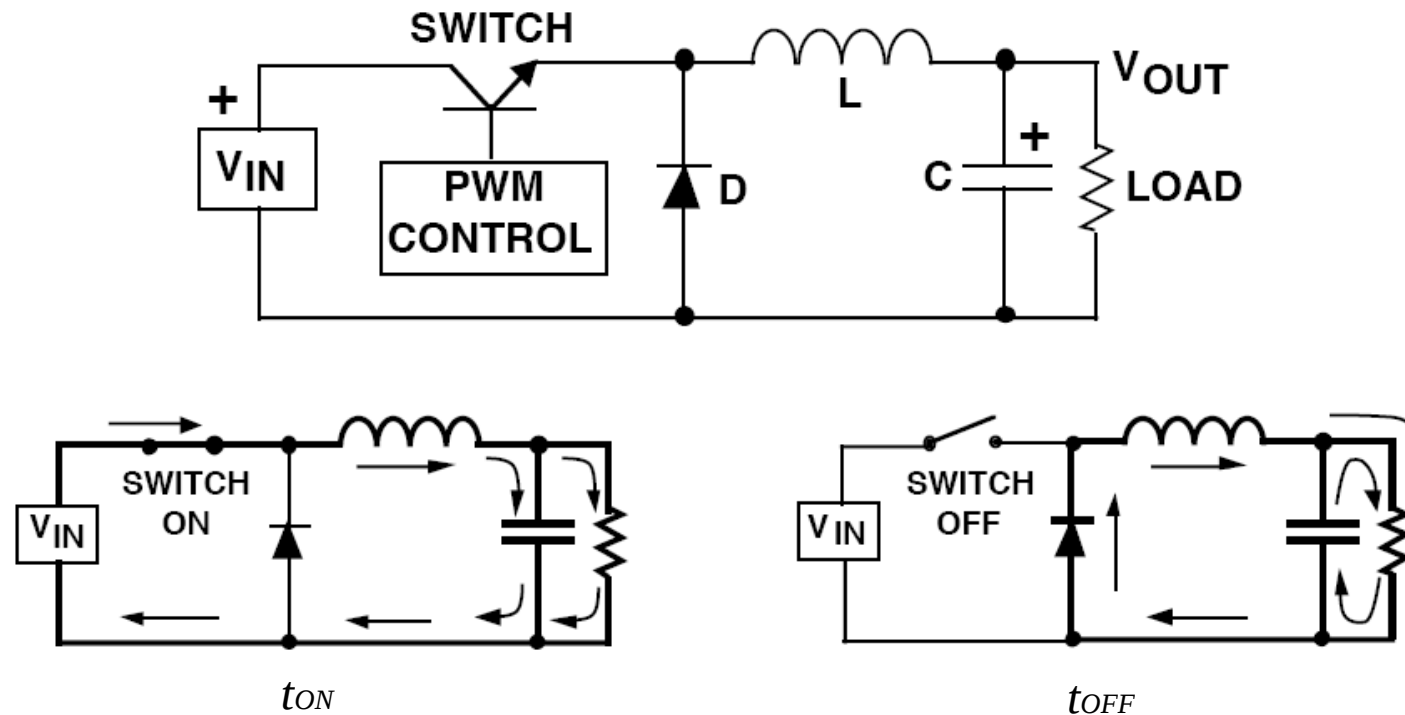- **The Buck Converter (Step Down)**
 - Converts a DC voltage to a lower DC voltage with the same polarity
 - Continuous and discontinuous conduction modes (CCM and DCM)



The Buck Converter – Ripple Current

Effects of ripple current (ΔI_L):

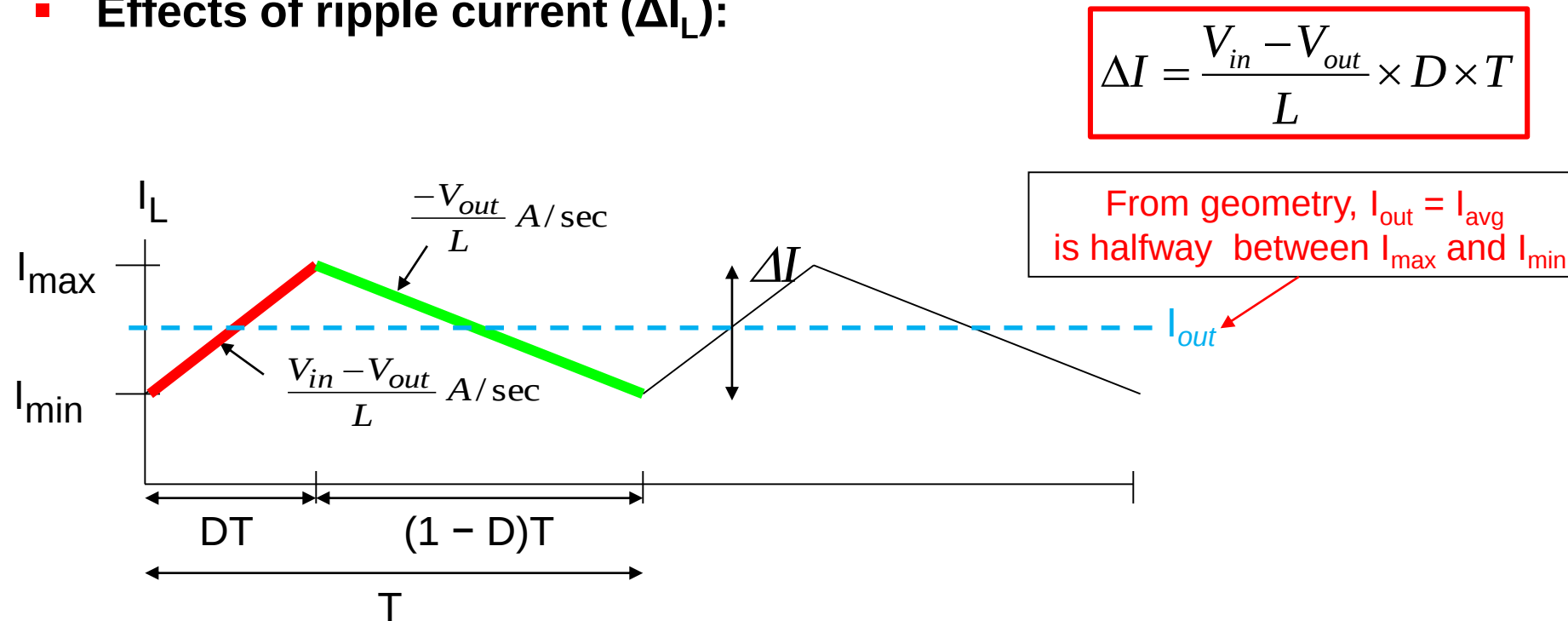


- CCM operation
- Emissions
- Core losses in the inductor
- Output voltage ripple (with the ESR of C_{out})

The Buck Converter – Inductance Value

■ Calculating inductance value (L):
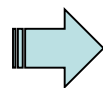
$$L = \frac{(V_{in} - V_{out})}{\Delta I} \times D \times T$$



Re-write as

$$L = \frac{V_{out} \cdot (1 - D)}{f_{switch} \cdot r \cdot I_{out}}$$


Terms:

- ✓ D = Duty cycle
- ✓ T = Time period of a cycle
- ✓ r = **Ripple % of o/p current**
- ✓ ΔI = Maximum ripple current
- ✓ F_s = Switching Frequency

■ Critical inductance value ($L_{critical}$):

- At Boundary of CCM/DCM ($\Delta I = 2I_{out}$)
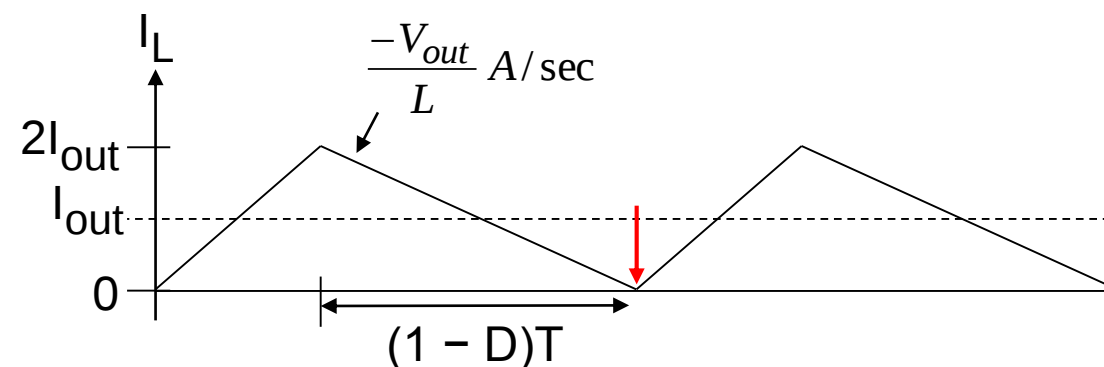
$$L_{Critical} > \frac{V_{out} (1 - D_{min})}{2I_{out_min} \cdot f_{switch}}$$




The Buck Converter – Capacitance Value

■ Calculating capacitance value (C):

$$C = \frac{\Delta I}{8 \cdot f_s \cdot \Delta V_{out}}$$

Remember:
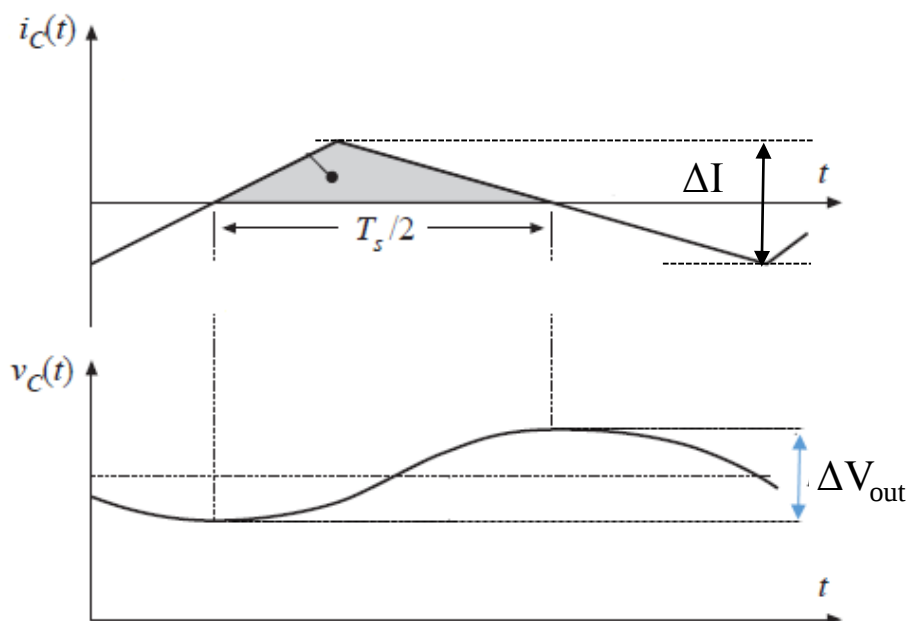
$$ESR \ll \frac{\Delta V_{out}}{\Delta I}$$




- Consider dynamic response
 - Overshoot, Undershoot
 - Damping, Leakage
- Think of ripple rating
- Estimate max ESR
- Don't forget dissipation factor

Terms:

- ✓ ΔV_{OUT} = Maximum output ripple voltage.
- ✓ ΔI = Maximum ripple current.
- ✓ ESR = Equivalent Series Resistance of C.
- ✓ F_s = Switching Frequency.

The Boost Converter

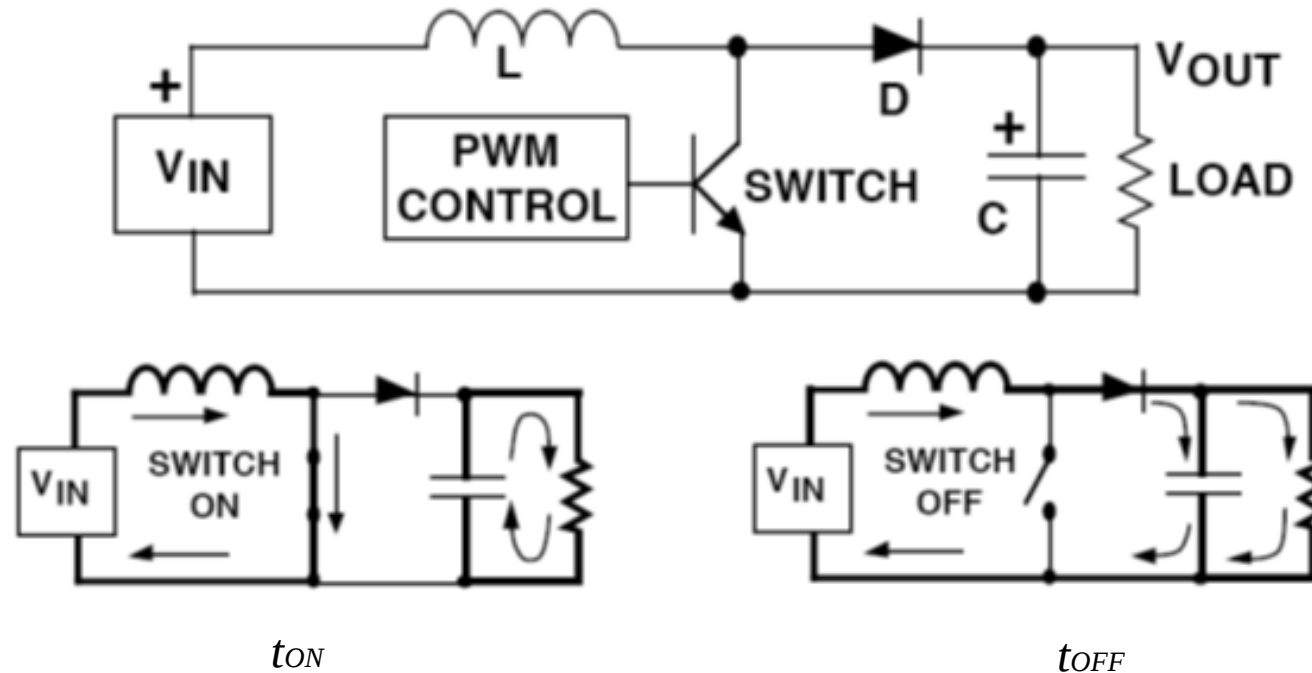
- **The Boost Converter (Step Up)**
 - Converts a DC voltage to a higher DC voltage with the same polarity
 - Continuous and discontinuous conduction modes (CCM and DCM)



The Boost Converter – Ripple Current

Effects of ripple current (ΔI_L):
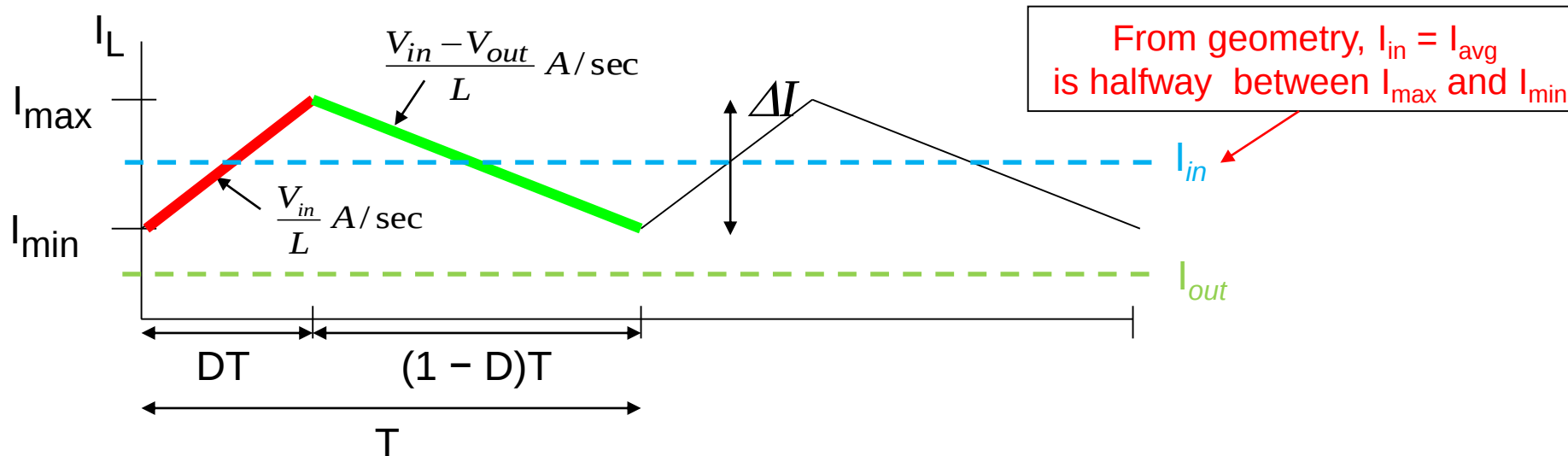
$$\Delta I = \frac{V_{in}}{L} \times D \times T$$




- CCM operation (as with the Buck)
- Output voltage ripple (with the ESR of C_{out})
- Core losses in the inductor
- Emissions

The Boost Converter – Inductance Value

■ Calculating inductance value (L):
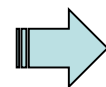
$$L = \frac{V_{in}}{\Delta I} \times D \times T$$



Re-write as

$$L = \frac{D \cdot V_{out} \cdot (1 - D)^2}{f_{switch} \cdot r \cdot I_{out}}$$


Terms:

- ✓ D = Duty cycle
- ✓ T = Time period of a cycle
- ✓ r = **Ripple % of o/p current**
- ✓ ΔI = Maximum ripple current
- ✓ F_s = Switching Frequency

■ Critical inductance value ($L_{critical}$):

- At Boundary of CCM/DCM ($\Delta I = 2I_{in}$ and $D = 0.33$)
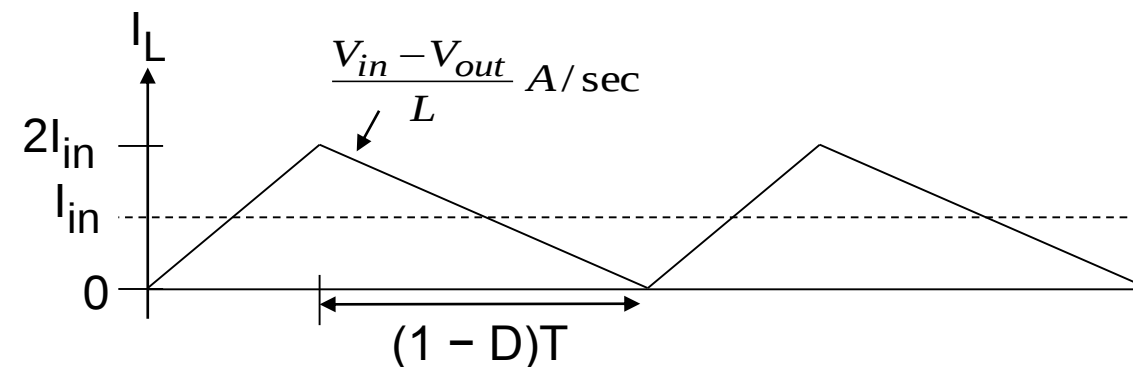
$$L_{Critical} > \frac{V_{out} \cdot D_{0.33} \cdot (1 - D_{0.33})^2}{2I_{out_min} \cdot f_{switch}}$$





The **SEPIC** Converter

■ The SEPIC Converter (Buck-Boost)

- Single Ended Primary Inductance Converter
- Converts a DC voltage to a lower or higher DC voltage with the same polarity

■ Single Inductors vs a Coupled Inductor

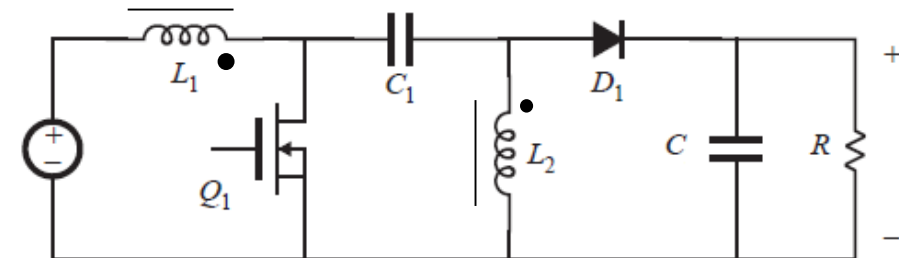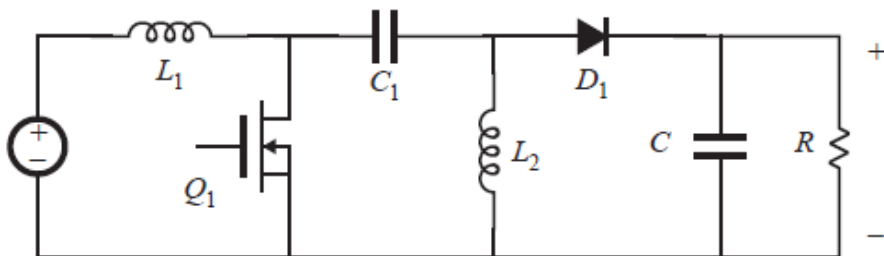- A coupled inductor is often selected due to:
 - Improved efficiency
 - Reduced component count, Reduced circuit area, lower cost
 - Lower inductance requirement compared to using two single inductors (half).
 - Input ripple current cancellation (resulting in smaller input capacitor and simpler EMI input filter)




- DC/DC Converter Topologies – Buck, boost & SEPIC
- **Causes of CM & DM Emissions** – LT Spice
- Efficiency and Losses – Core, Copper and AC
- Criteria for selecting Inductor and Capacitor – DC Bias
- Practical Input Filter Design – LC Filter
- REDEXPERT – Interactive component selection

Causes of EM Emissions – Where to look ??

- ✓ There are many ways unwanted “Electromagnetic” waves can escape
- ✓ Circuit that switches fast can become source of noise
- ✓ Every wave have harmonics, except pure sinusoidal
- ✓ Square wave have infinite number of ODD harmonics
- ✓ Differential noise is caused by flow of circuit current
- ✓ Common mode noise is mainly due to parasitic / stray capacitance
- ✓ Leakage inductance of transformer
- ✓ Track length of $\frac{1}{4}$ or Half wavelength
- ✓ Earthing, PCB Ground or power plane
- ✓ MCU or FPGA – Clock, Data bus, I²C and SPI ...
- ✓ Loose cable – Ethernet, HDMI, RS485, CAN, Mains ...
- ✓ Metallic coupling – enclosure, connector, cover, heatsink ...
- ✓ LCD – Processor, touch screen, frame, cable, connector ...






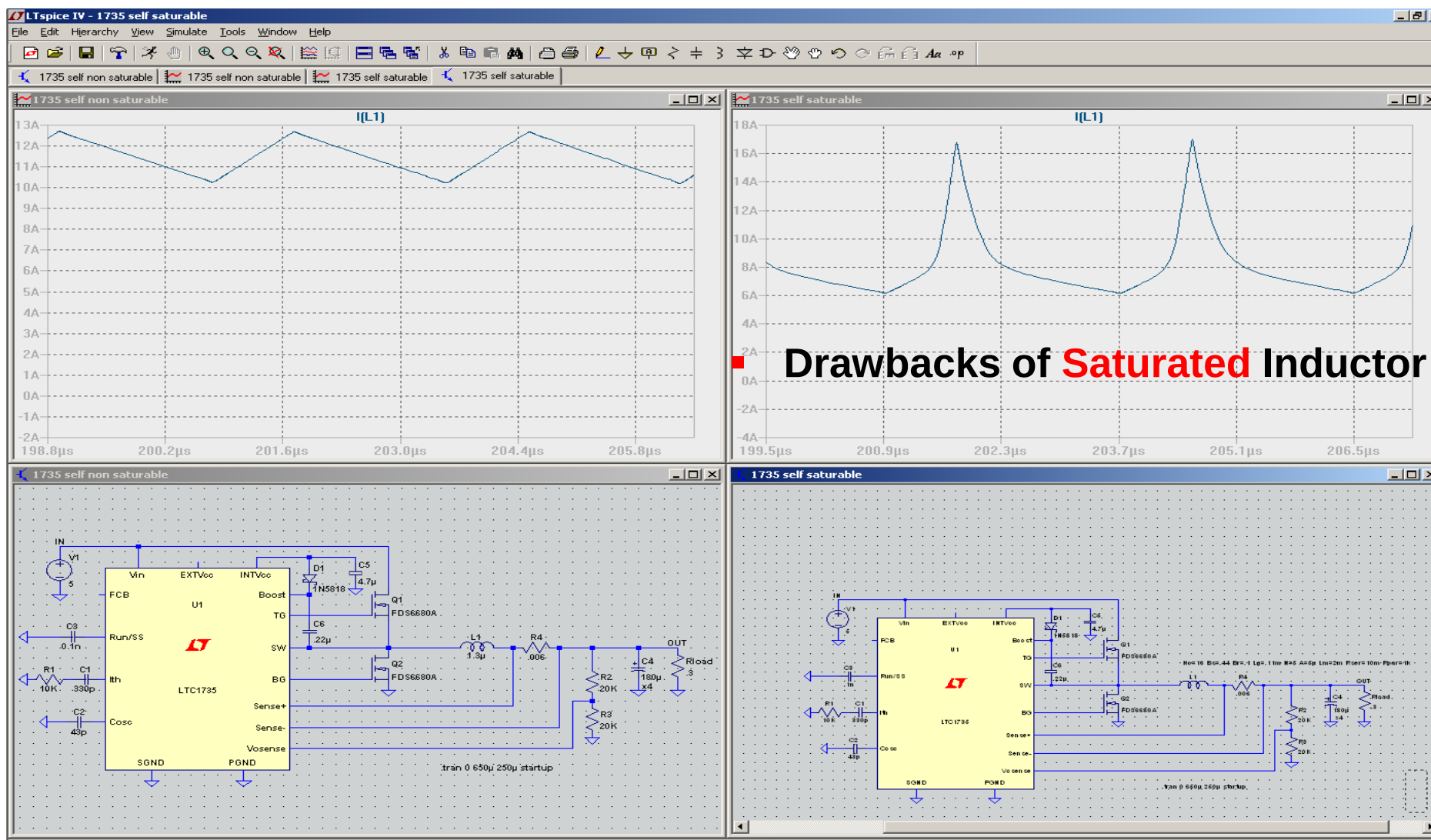Causes of EM Emissions - Wrong or Missing Filter ??



Drawbacks of **Saturated** Inductor

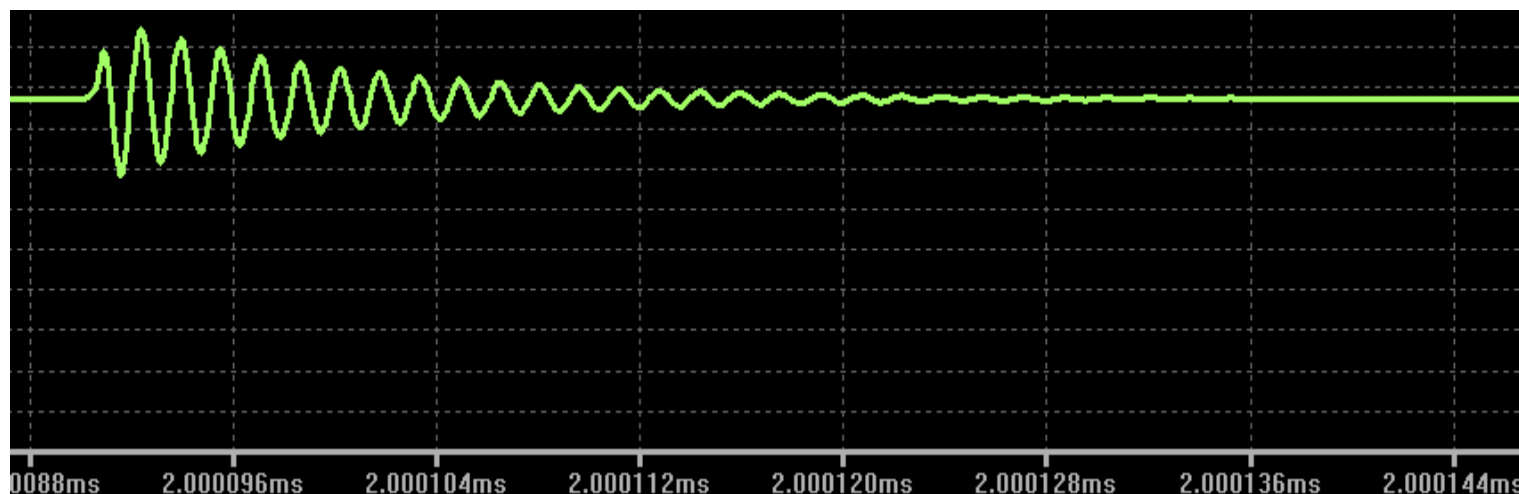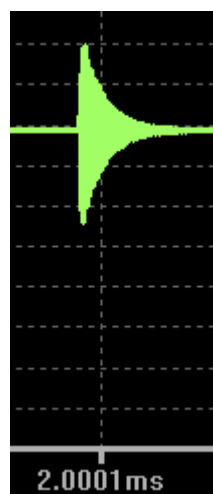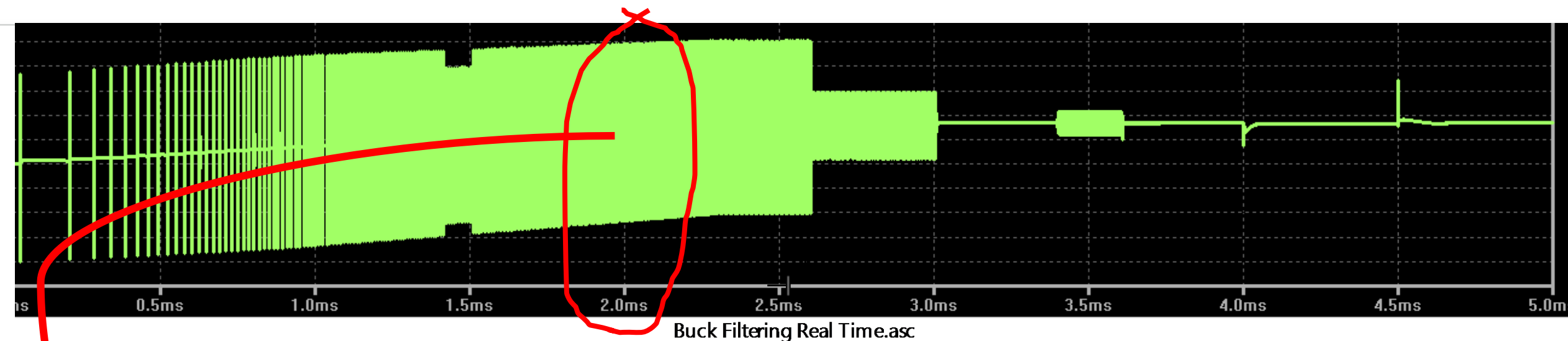Causes of EM Emissions → Rectangular + Sine wave = Ringing



Buck Filtering Real Time.asc

- DC/DC Converter Topologies – Buck, boost & SEPIC
- Causes of CM & DM Emissions – LT Spice
- **Efficiency and Losses** – Core, Copper and AC
- Criteria for selecting Inductor and Capacitor – DC Bias
- Practical Input Filter Design – LC Filter
- **REDEXPERT** – Interactive component selection



Efficiency - Importance

Advantages of Highly Efficient Design

- ✓ Smaller size
- ✓ Lower costs
- ✓ Higher reliability
- ✓ Longer battery life
- ✓ Low thermal losses
- ✓ Better performance
- ✓ Longer operating life
- ✓ Higher power density
- ✓ Reduced maintenance
- ✓ Less cooling, no fan, small heatsink
- ☐ Difficult to copy
- ☐ Brand reputation
- ☐ Sustainable design
- ☐ Customer satisfaction
- ☐ Competitive advantage
- ☐ “Green” environmentally friendly


$$P = I^2 \textcolor{red}{R} T \quad ??$$

A small efficiency increase
greatly reduce losses !!

No Fan – No bulky heat sink

INDUCTOR LOSSES

T1 = 58°C T2 = 69°C T3 = 50°C

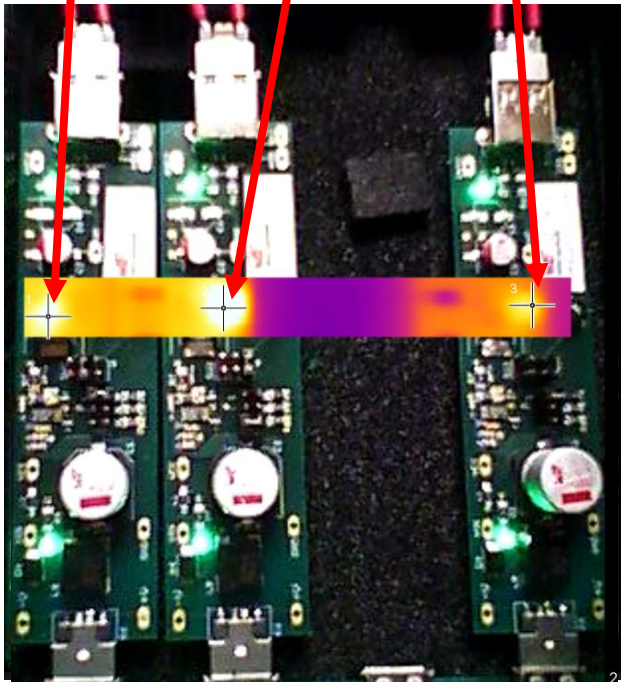



What causes self-heating of the inductor ?

- Can you estimate ?
- Can you reduce ?

TYPE of LOSSES

- Core Losses – *Eddy, Flux, Field, μ , etc.*
- Copper Losses – *R_{DC} , CSA, Current, Length, Litz*
- Switching Losses – *R_{DS} , ON Time, F , V*
- Leakage Losses – *Snubber, reflections*
- AC Losses – *F , $DS\%$, Waveform, Skin, Proximity*
- *EMI Radiations – CM, DM, C, R, shielding*

Magnetic Fields – The magnetic field

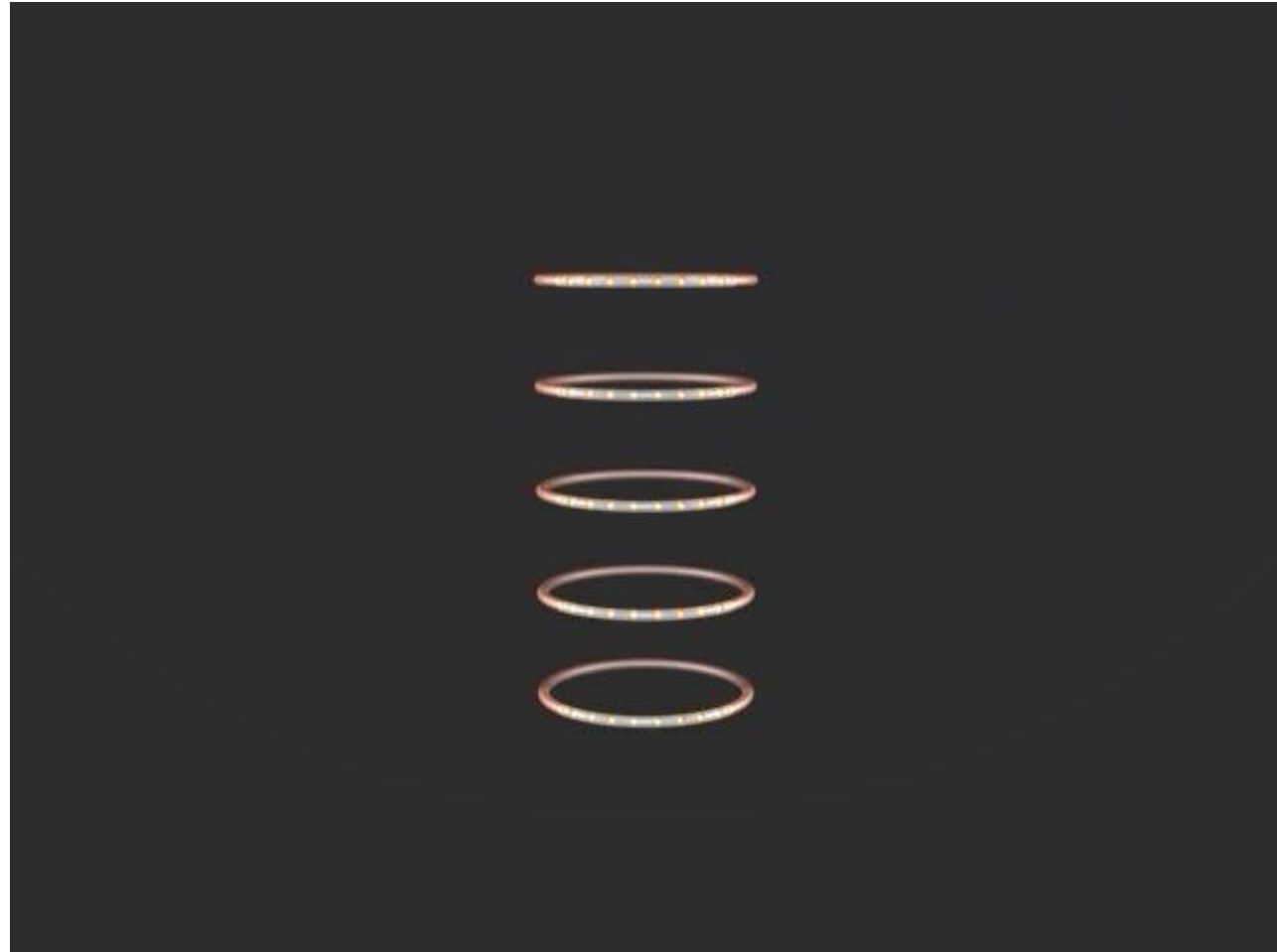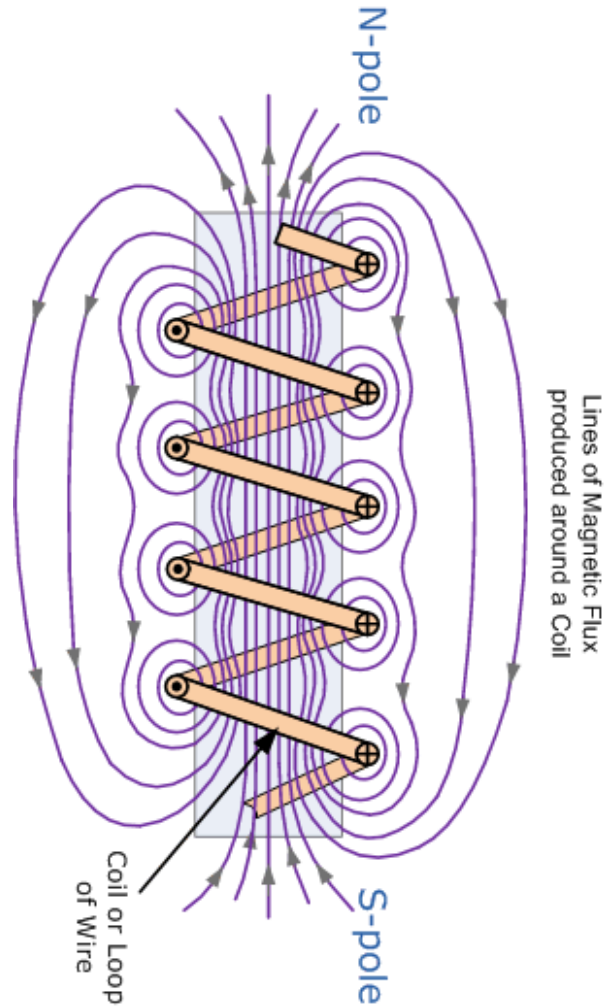

INDUCTOR LOSSES

$$P_{total} = P_{core} + P_{copper}$$


Core losses:

Hysteresis losses
Eddy current losses


Copper losses:

DC losses – depending on DCR
AC losses – dep. on winding structure

→ Skin-Effect
→ Proximity-Effect

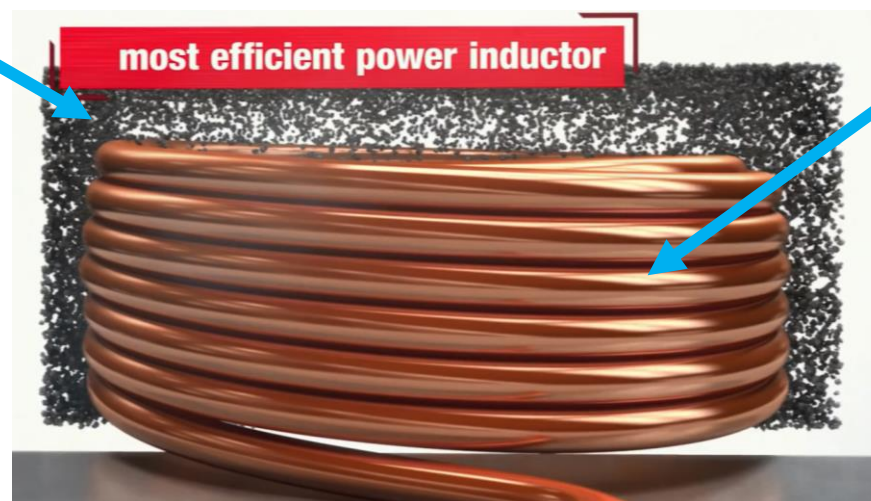

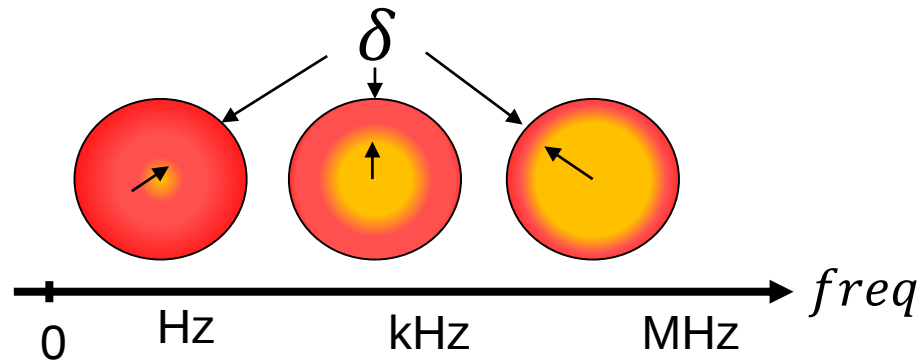
INDUCTOR LOSSES : Copper AC Losses, Skin effect (River Rafting)



$$\delta = \sqrt{\frac{2 * \rho}{w * \mu}} \text{ mm} \quad \delta = \frac{76}{\sqrt{f}} \text{ mm} @ 100^{\circ}\text{C}$$

For Copper

δ @	50Hz	= 9.38 mm
δ @	10kHz	= 0.66 mm
δ @	100kHz	= 0.22 mm

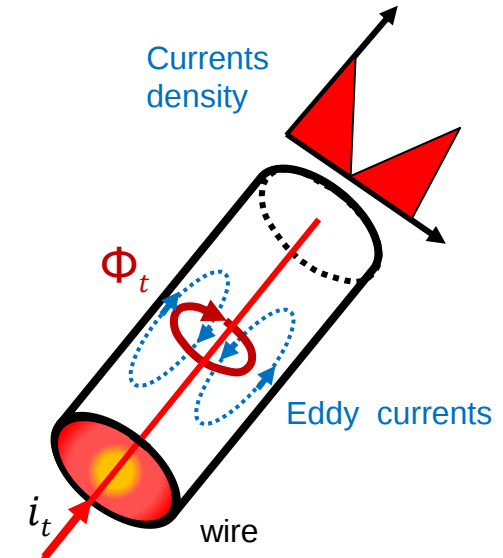

Terms:


δ = skin depth

ρ = resistivity

w = angular frequency $2\pi f$

μ = permeability

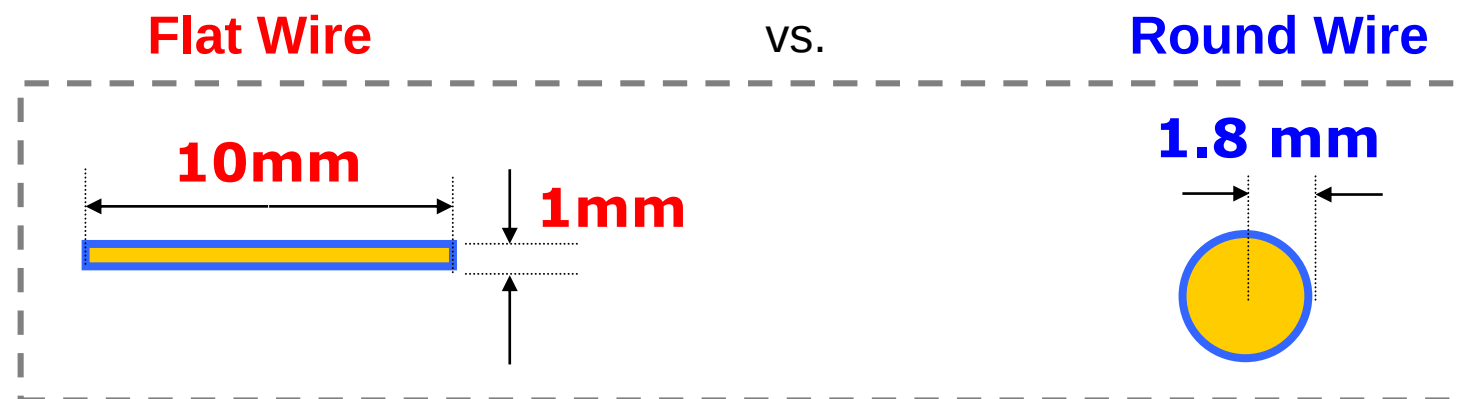INDUCTOR LOSSES : Copper AC losses, Skin effect



- ✓ Cross section of both wires = 10mm^2
- ✓ Flat wire has much more bigger surface
- ✓ Flat wire surface = 22mm^2 / Round wire = 11mm^2 $S_{\text{FLAT}} = 1.9 \times S_{\text{RUND}}$
- ✓ High frequency currents only uses the surface → Skin effect



Flat wire has a higher surface,
thus less copper losses at higher frequencies !




INDUCTOR LOSSES : DC Copper Losses



$$P_{cu} = R_{DC} * I_{RMS}^2$$

$$R_{DC} = \rho * \frac{l}{A}$$

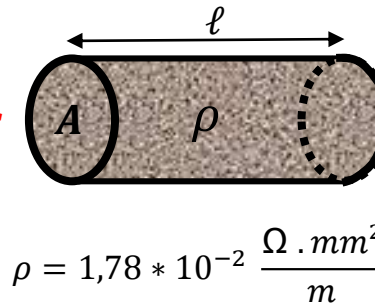


$$\rho = 1,78 * 10^{-2} \frac{\Omega \cdot mm^2}{m}$$





$$R_{DC} \downarrow \Rightarrow P_{cu} \downarrow$$

- ρ : Resistivity of copper
- l : Length of wire
- A : Cross Sectional area



Optimization

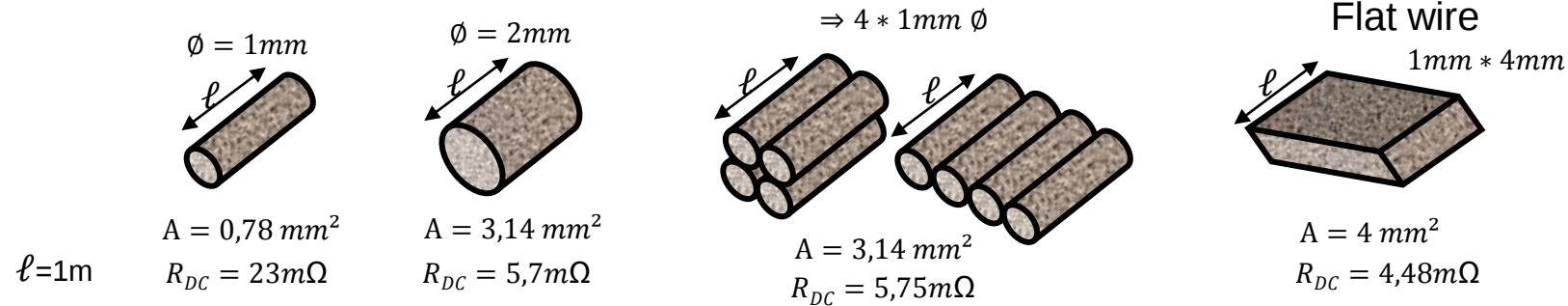

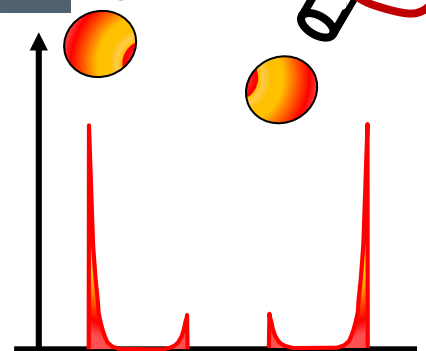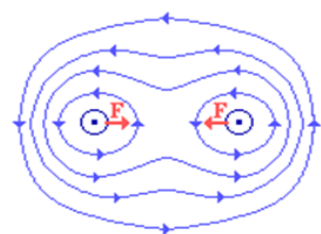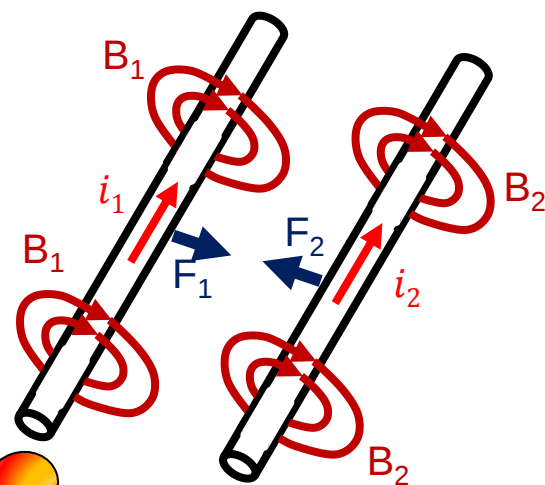
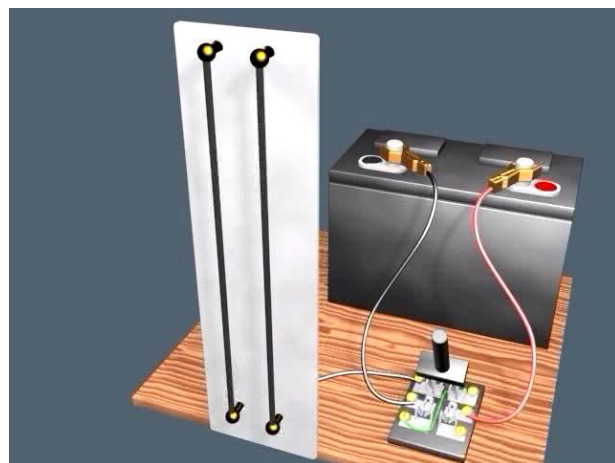
INDUCTOR LOSSES : AC Copper losses, Proximity effect



Current in same direction

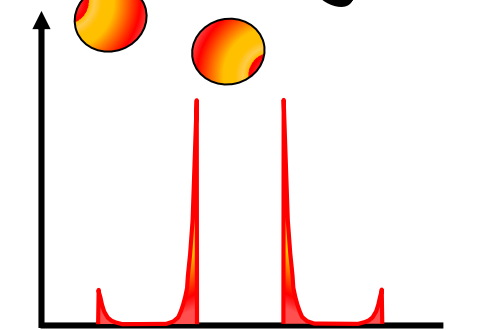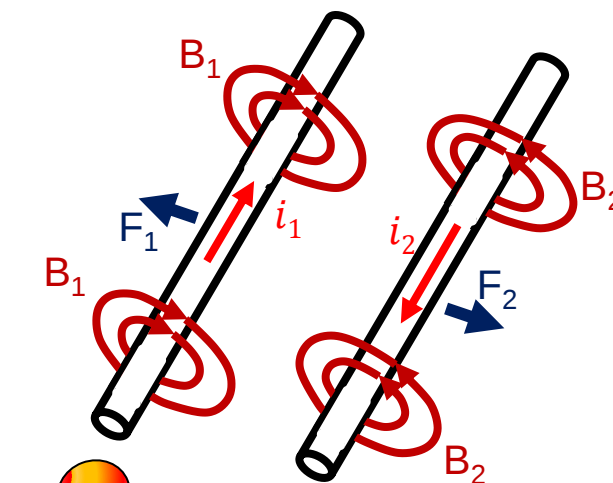

Current in opposite direction

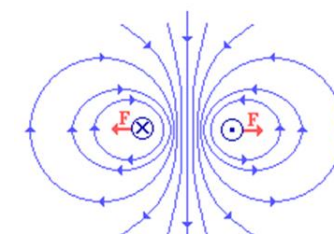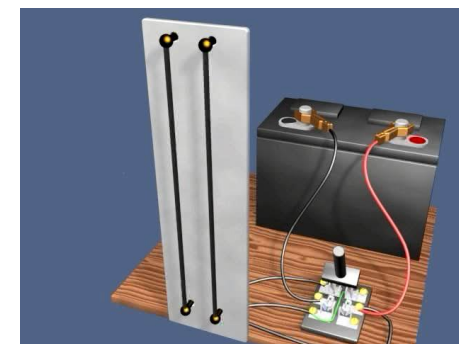

- Proximity Effect creates more loss than Skin Effect
 - Dowell's curves for simple geometries
 - Bruce Carsten or Charles Sullivan for more in-depth

$$f \uparrow \Rightarrow R_{AC} \uparrow$$

Like the skin effect, the distribution of current inside the wire is reduced


- DC/DC Converter Topologies – Buck, boost & SEPIC
- Causes of CM & DM Emissions – LT Spice
- Efficiency and Losses – Core, Copper and AC
- **Criteria for selecting Inductor and Capacitor – DC Bias**
- Practical Input Filter Design – LC Filter
- REDEXPERT – Interactive component selection



Inductor Selection Parameters

■ Inductor Parameters:

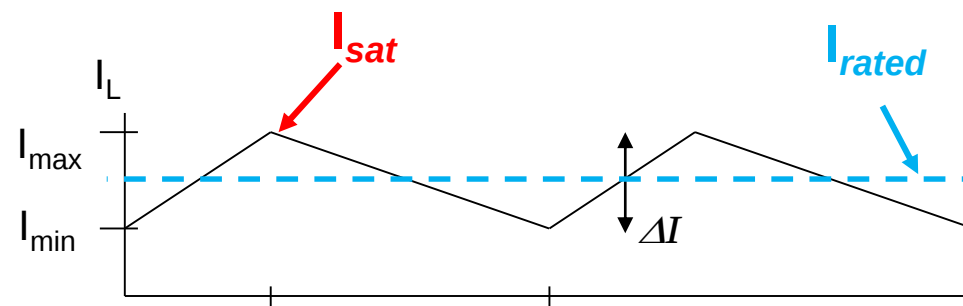- Rated Current
- Saturation Current
- DC Losses - R_{DC}
- AC Core Losses
- AC Copper Losses
 - Proximity effect
 - Skin effect
- Resonant Frequency / Q
- Inductance vs Current Curve
- Impedance vs Frequency Curve
- Temperature rise vs Current Curve




■ Other Criteria:


- Size
- Approvals*
- Availability
- Shielding – E, B, H Fields
- Material, manufacturing techniques

Inductor Selection Parameters – Saturation Current

Drop of the inductance value

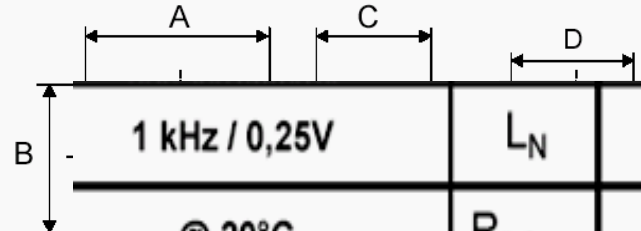Spezifikation für Freigabe / specification for release			
Kunde / customer : _____			
Artikelnummer / part number :		7447709001/LF	
Bezeichnung : SPEICHERDROSSEL WE-PD			
description : POWER-CHOKE WE-PD		 WÜRTH ELEKTRONIK	
DATUM / DATE : 2004-06-03			
A Mechanische Abmessungen / dimensions:		Typ XXL	
		A	12,0 ± 0,5 mm
		B	12,0 ± 0,5 mm
		C	10,0 max. mm
		D	7,6 ref mm
			5,0 ref mm
			mm


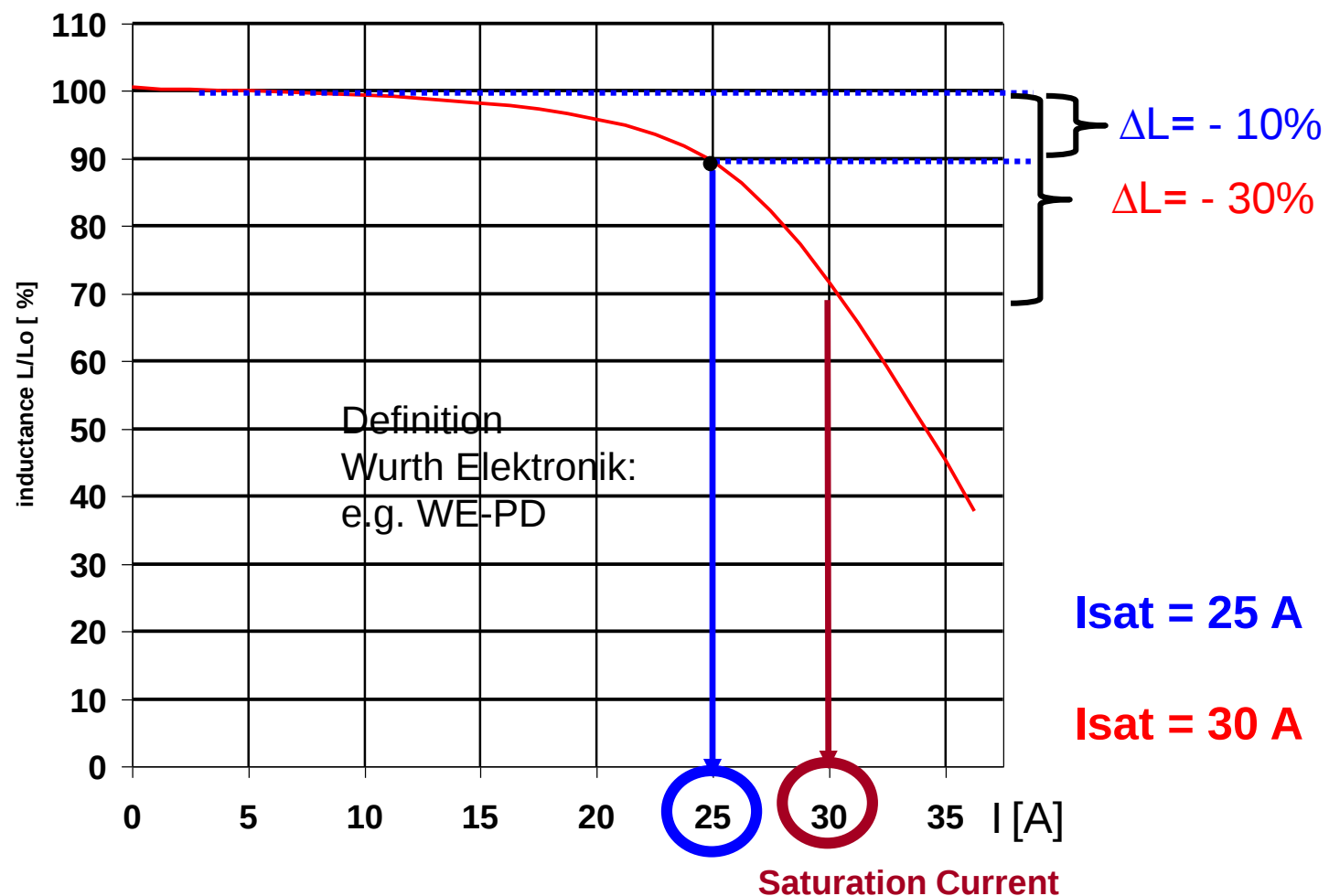
Inductor Selection Parameters – Saturation Current



- the saturation current always refers to a certain inductance drop

Inductor Selection Parameters – Material

■ Saturation Current vs material

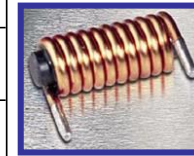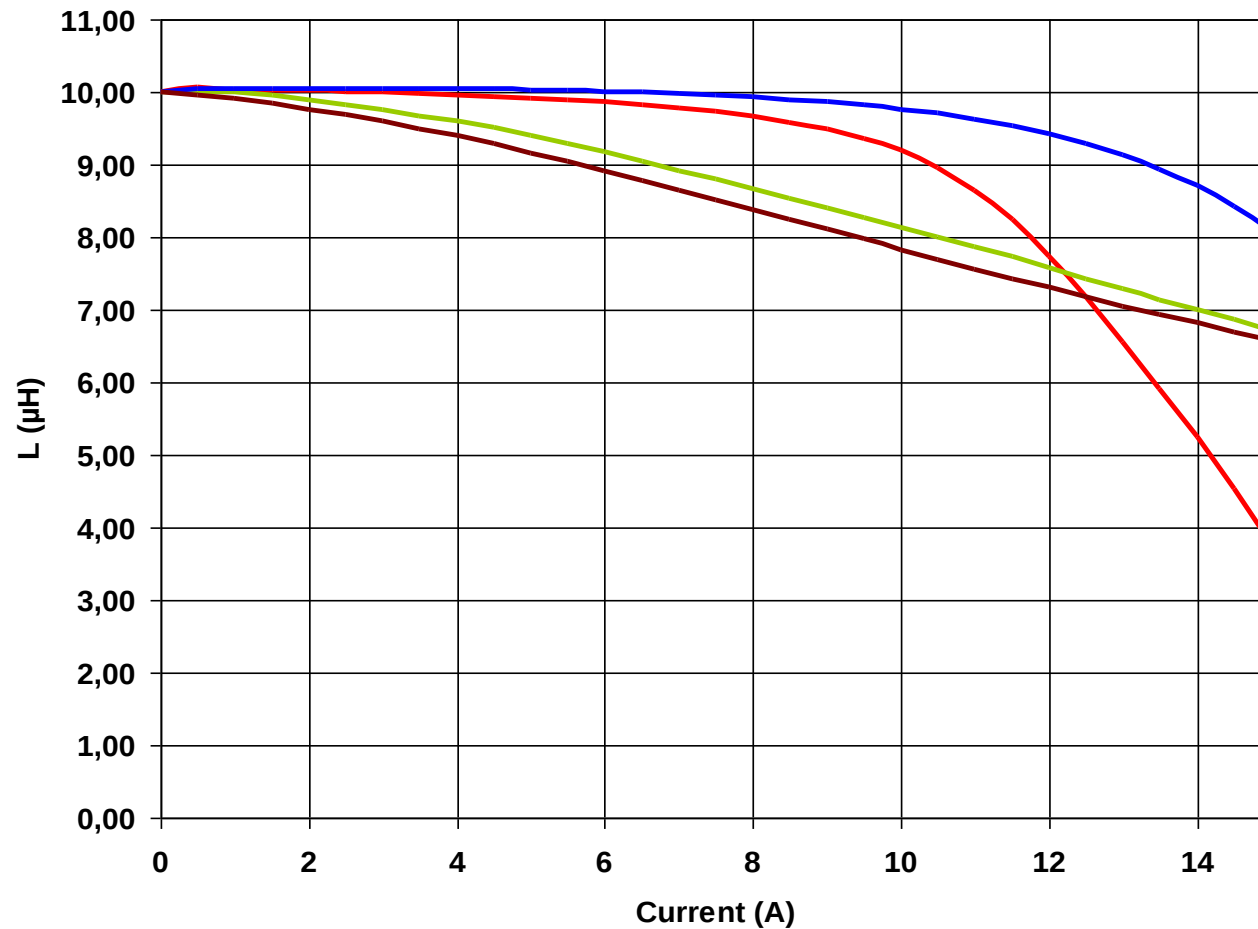

WE-SD

Material: NiZn
AirGap: big



WE-HCI

Material: WE-Perm
AirGap: small



WE-SI

Material: Iron
AirGap: distributed



WE-PD

Material: NiZn
AirGap: small

Inductor Selection Parameters – Rated Current

=> **Increase temperature with a DC current**



Spezifikation für Freigabe / specification for release

Kunde / customer : _____

Artikelnummer / part number : 7447709001/LF

Bezeichnung : SPEICHERDROSSEL WE-PD

description : POWER-CHOKE WE-PD




DATUM / DATE : 2004-06-03

A Mechanische Abmessungen / dimensions:


	Typ XXL	
A	12,0 ± 0,5	mm
B	12,0 ± 0,5	mm

DC-Widerstand / DC-resistance	@ 20°C	R _{DC max}	5,60	mΩ
Nennstrom / rated current	ΔT=40 K	I _{DC}	13,00	A
Sättigungsstrom / saturation current	ΔL/L < 10%	I _{sat}	25,00	A

Induktivität / inductance	1 kHz / 0,25V	L _N	1,0	μH	±20%
DC-Widerstand / DC-resistance	@ 20°C	R _{DC typ}	3,86	mΩ	typ.
DC-Widerstand / DC-resistance	@ 20°C	R _{DC max}	5,60	mΩ	max.
Nennstrom / rated current	ΔT=40 K	I _{DC}	13,00	A	max.
Sättigungsstrom / saturation current	ΔL/L < 10%	I _{sat}	25,00	A	typ.
Eigenres.-Frequenz / self-res.-frequency		SRF	120,0	MHz	typ.

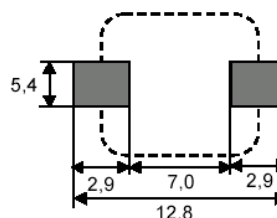

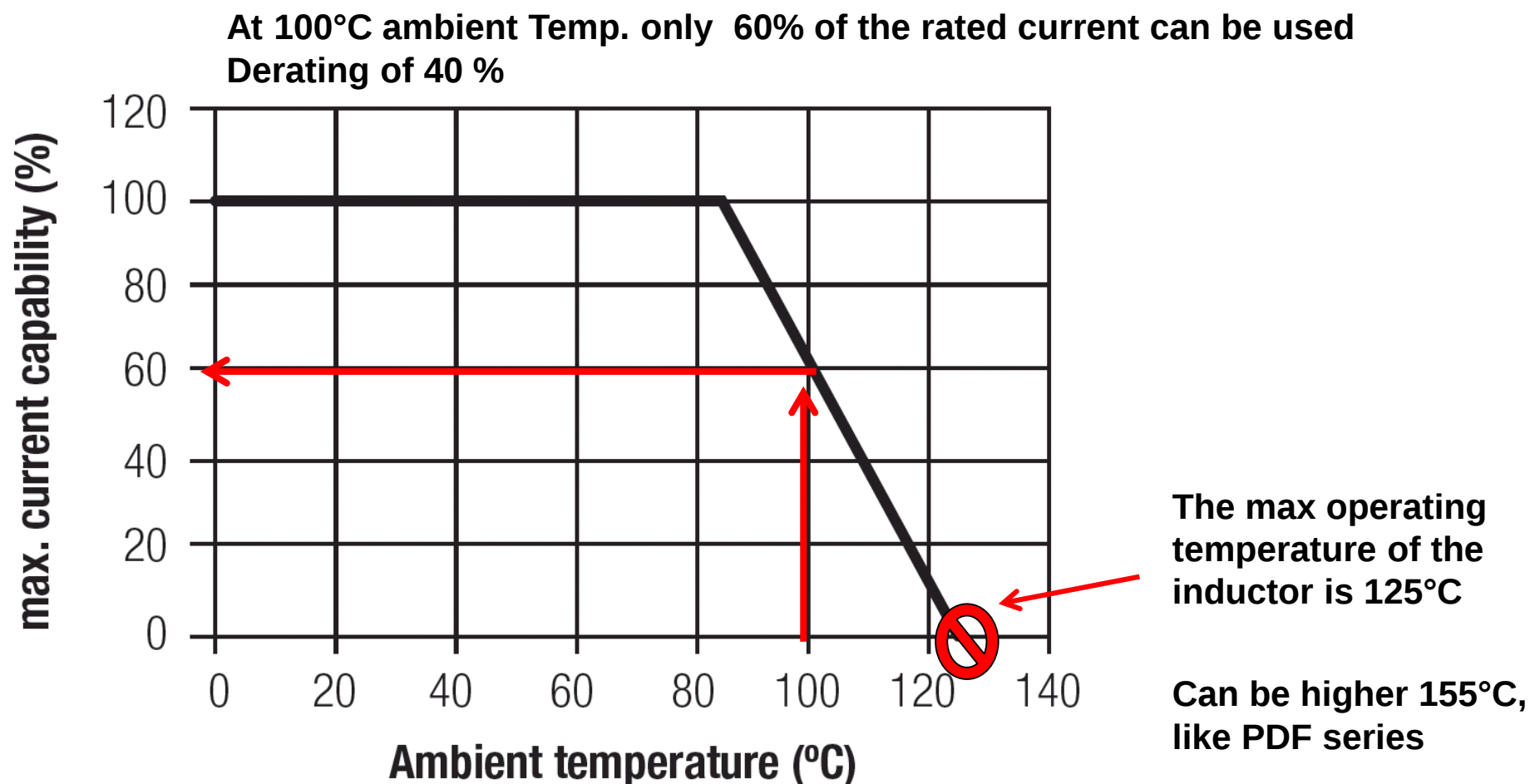Inductor Selection Parameters – Current De-rating



Capacitor Selection Parameters

■ Top 20% :

- Voltage, Operating Temperature
- Expected Life, ESR, Ripple Current
- Leakage Current, Dissipation Factor




■ Bottom 80%:

- Impedance, resonance frequency, Q/DF factor
- Drying out of electrolyte, self-healing
- Ambient → Capacitance vs Temperature Curve
- DC Bias → Capacitance vs Voltage Curve
- Durability → Capacitance vs Time Curve
- MLCC Class → 1 (NPO/COG, low perm) and 2 (X7R, Y5V)



Expected Life

Capacitors Selection

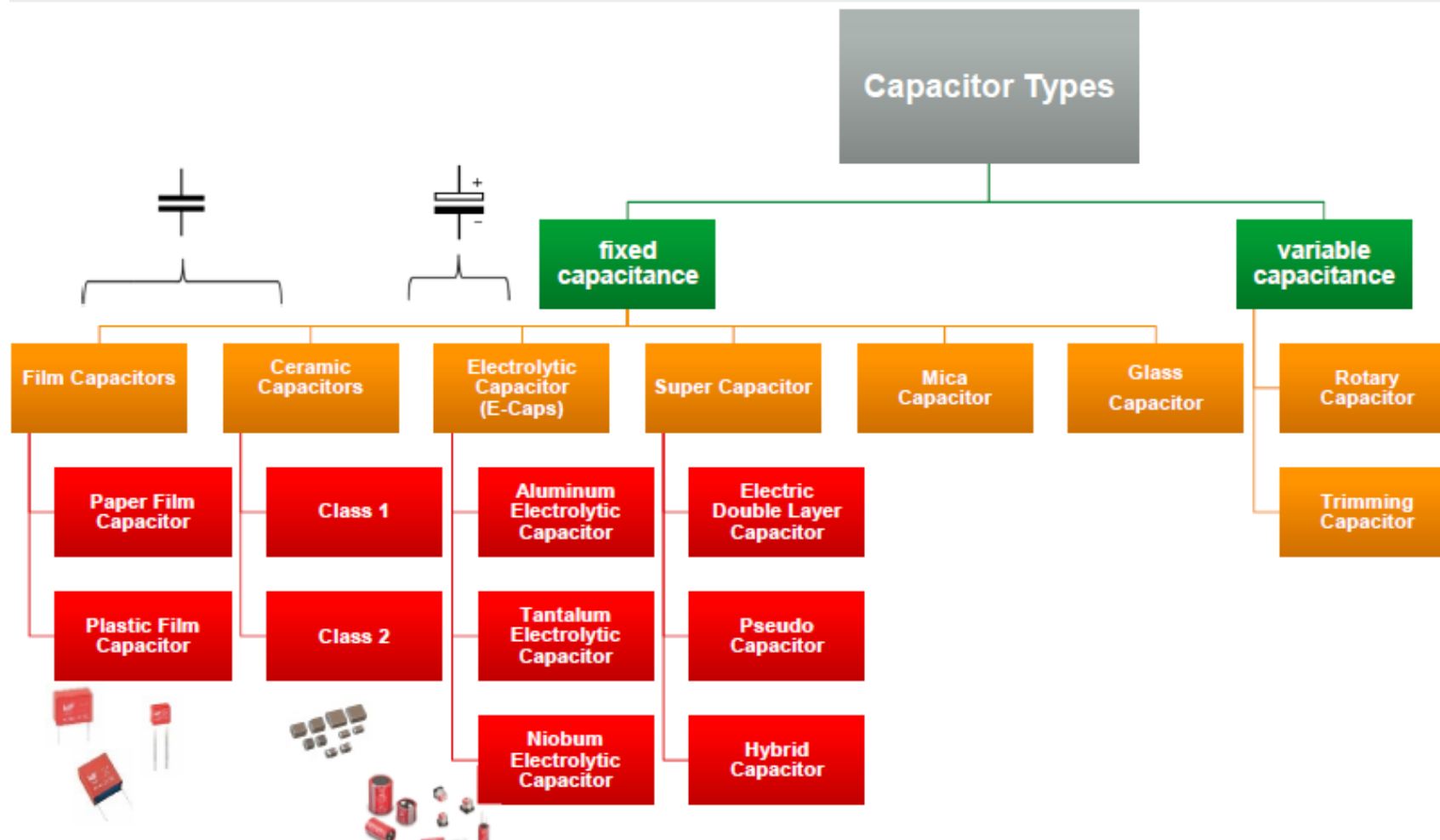

Electrolytic **vs** Polymer Capacitors

Electrolytic Caps:


- ✓ Higher voltage rating up to 600v
- ✓ Relatively lower prices
- ✓ Better leakage current behaviour

- X Liquid electrolyte, drying out
- X Lower volumetric capacity
- X Lower life expectancy

Polymer Caps:

- ✓ Lower ESR
- ✓ Higher ripple rating
- ✓ Solid polymer, No drying out effect
- ✓ Longer expected life
- ✓ Higher operating temperature

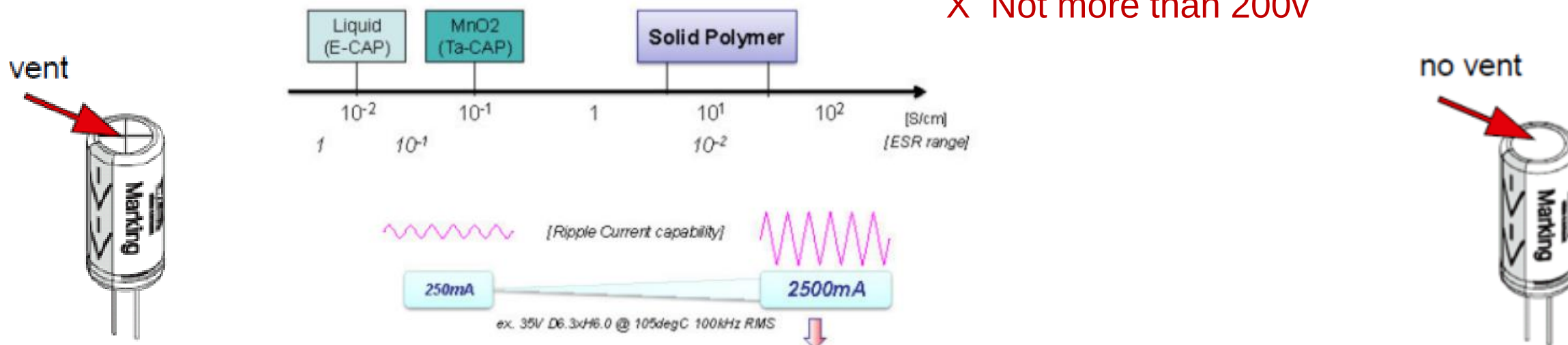- X Limited can size
- X Not more than 200v



Electrolytic vs Polymer Capacitors



Aluminum Polymer Capacitors:

$$L_x = L_{Nom} * 10^{\frac{T_{max} - T_A}{20}}$$

Aluminum Electrolytic Capacitors

$$L_x = L_{Nom} * 2^{\frac{T_{max} - T_A}{10}}$$




Capacitor Temperature	Aluminum Polymer Capacitor		Aluminum Electrolytic Capacitor			
125 °C	2.000 h	-	-	-	-	-
115 °C	6.325 h	-	-	-	-	-
105 °C	20.000 h	2.000 h	5.000 h	2.000 h	-	-
95 °C	63.246 h	6.325 h	10.000 h	4.000 h	-	-
85 °C	200.000 h	20.000 h	20.000 h	8.000 h	5.000 h	2.000 h
75 °C	632.455 h	63.246 h	40.000 h	16.000 h	10.000 h	4.000 h
65 °C	2.000.000 h	200.000 h	80.000 h	32.000 h	20.000 h	8.000 h



MLCC - Classifications

Class 1 ceramics (NP0 = C0G)

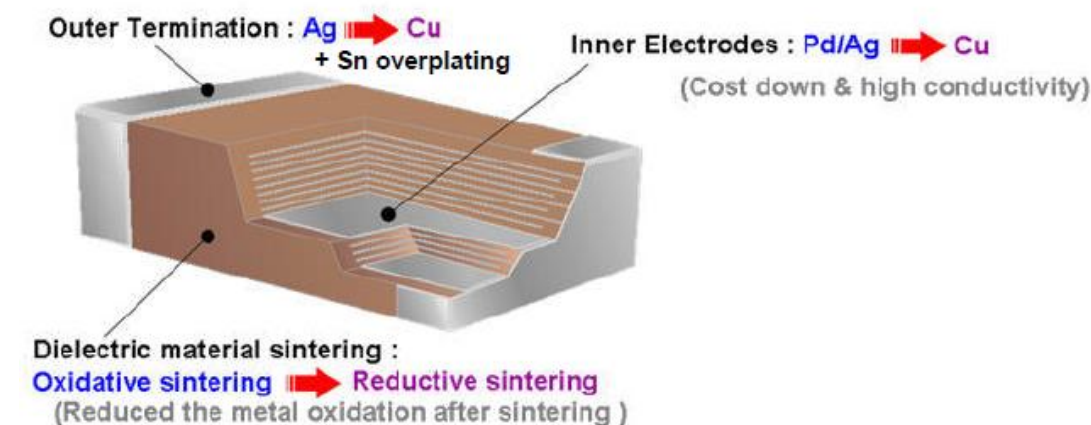- ✓ Built with titanium oxide
- ✓ Minimum aging behaviour
- ✓ Linear temperature dependency
- ✓ Low (down to none) voltage dependency
- ✓ Low relative permittivity $\epsilon_r \rightarrow$ smaller capacitance




Class 2 ceramics (X7R, X5R, Y5V)


- ✓ Built with barium titanate
- ✓ Higher relative permittivity $\epsilon_r \rightarrow$ higher capacitance
- ❑ Aging behaviour
- ❑ High voltage dependency
- ❑ Piezoelectric effects can result in microphonic noise
- ❑ Not linear (and stronger distinct) temperature dependency



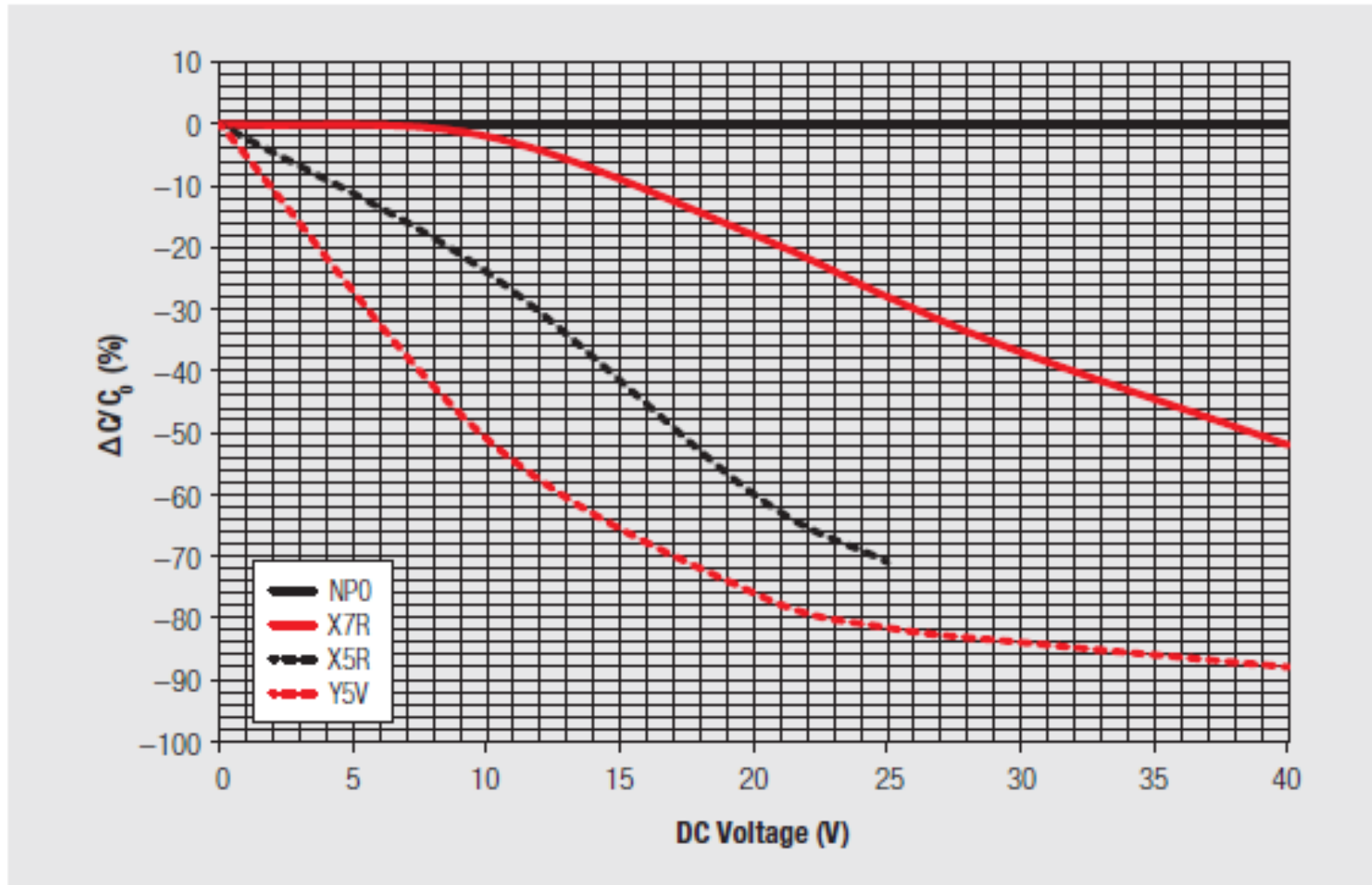MLCC – DC Bias Effect → $\Delta C/C_0$ vs DC Voltage



Temperature Dependency of Ceramic

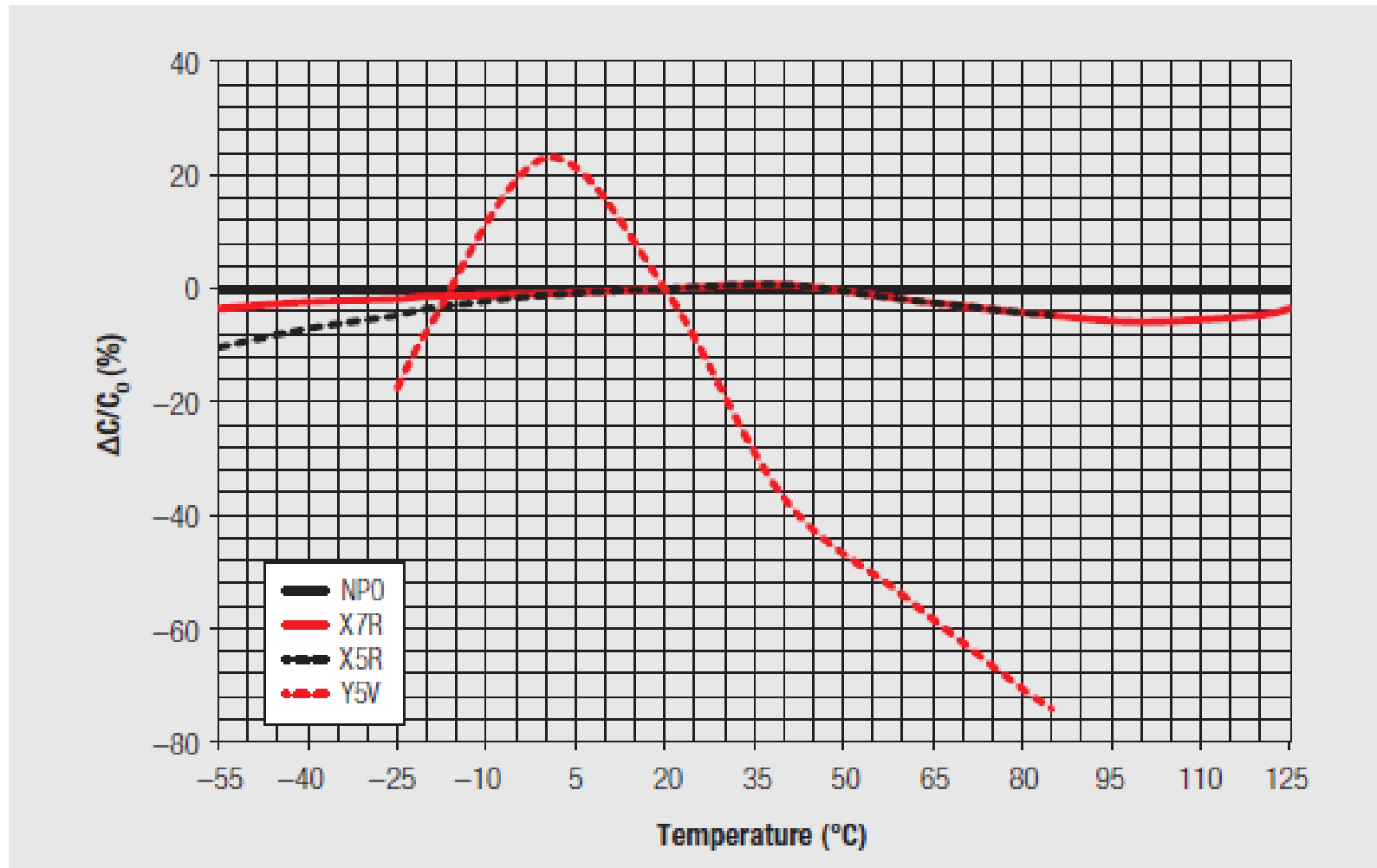


EIA-RS-198 Coding for Ceramic Caps



EIA-RS-198 coding for class 2 ceramic capacitors					
1st character		2nd character		3rd character	
Letter	Lower temperature limit	Number	Upper temperature limit	Letter	Capacitance change over the permissible temperature range
X	−55 °C	2	+45 °C	A	±1.0%
Y	−30 °C	4	+65 °C	B	±1.5%
Z	+10 °C	5	+85 °C	C	±2.2%
		6	+105 °C	D	+3.3%
		7	+125 °C	E	+4.7%
		8	+150 °C	F	+7.5%
		9	+200 °C	P	±10%
				R	±15%
				S	±22%
				T	+22/−33%
				U	+22/−56%
				V	+22/−82%

Self-Healing of Film Capacitors

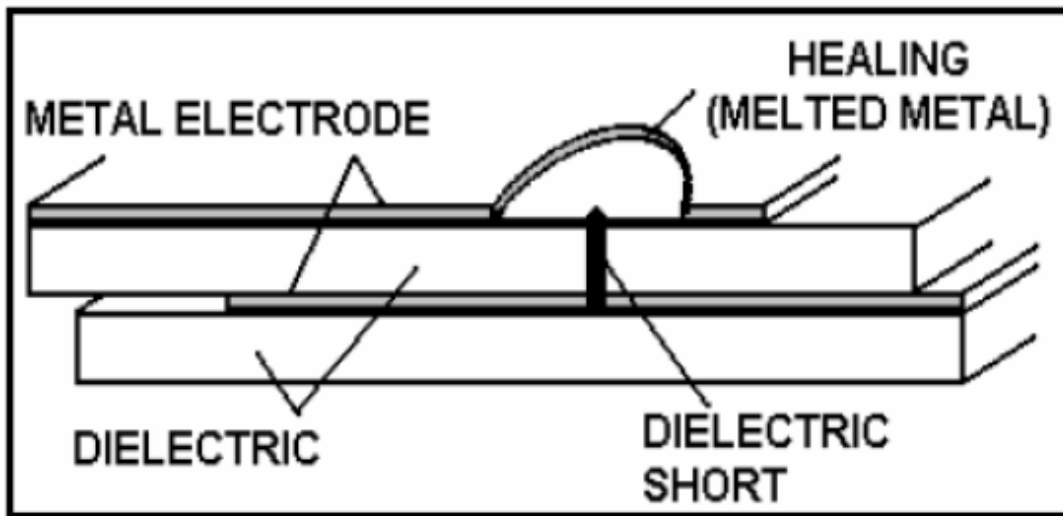X & Y Safety Classes
According IEC 60384-14 / UL 60384-14:




Safety Class	Max. Impulse according IEC-60384-14
X1	4kV ($C \leq 1\mu\text{F}$)
X2	2,5 kV ($C \leq 1\mu\text{F}$)
Y1	8 kV
Y2	5 kV
Y3	Not anymore in IEC standard (in the past defined by manufacturer)

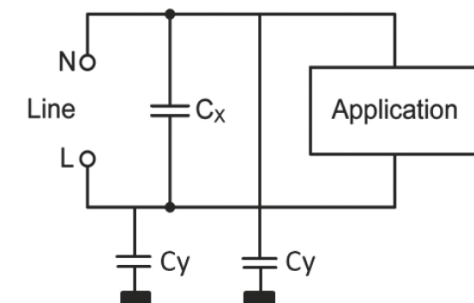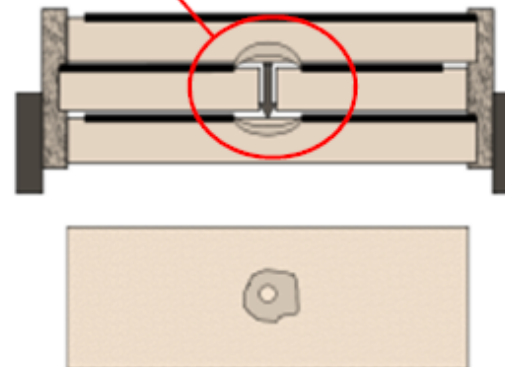

- DC/DC Converter Topologies – Buck, boost & SEPIC
- Causes of CM & DM Emissions – LT Spice
- Efficiency and Losses – Core, Copper and AC
- Criteria for selecting Inductor and Capacitor – DC Bias
- **Practical Input Filter Design – LC Filter**
- REDEXPERT – Interactive component selection




Oscillation At Converter Input

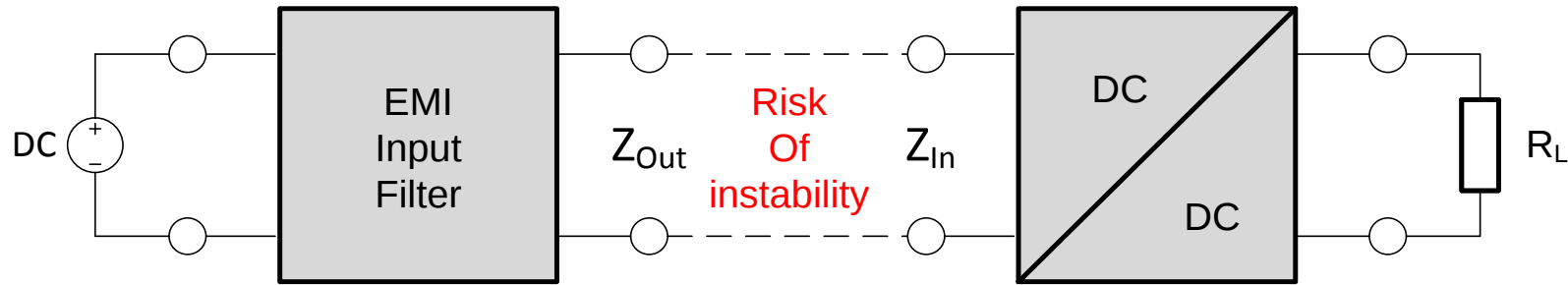

- ☐ Adding an input filter may cause oscillations
- ☐ Converter no longer meets response specs, and may become unstable
- ☐ Why?

(DC) Input Impedance Of Converter (an explanation)

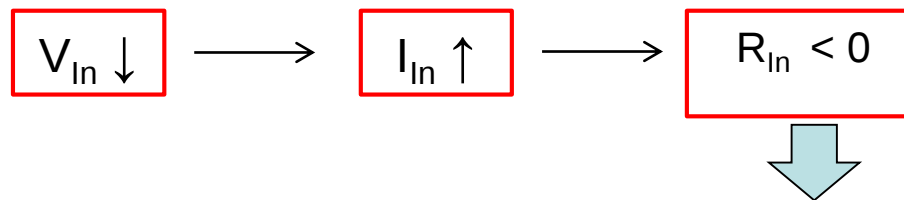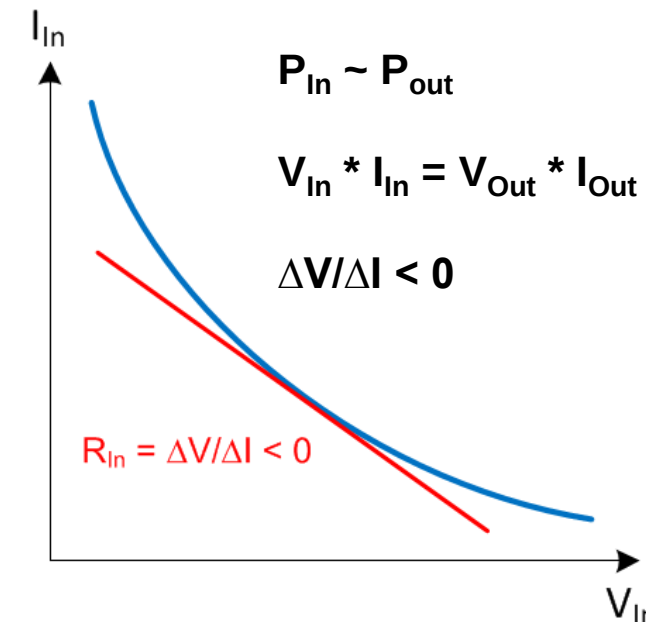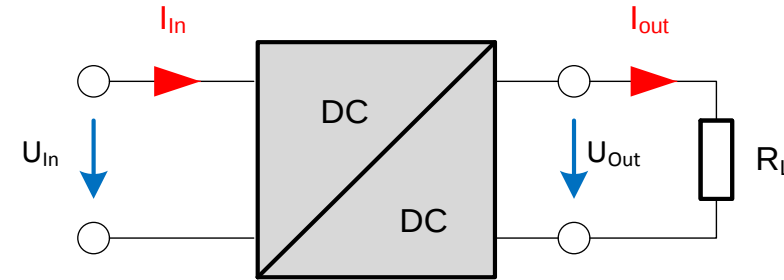
- Input and output power of converter is near the same (efficiency drop)
- Under stable conditions output power is constant
- If the input voltage falls, the input current increases
- Voltage-current line has a negative slope




NEGATIVE DC INPUT RESISTANCE

What could happen?

- Simplified model

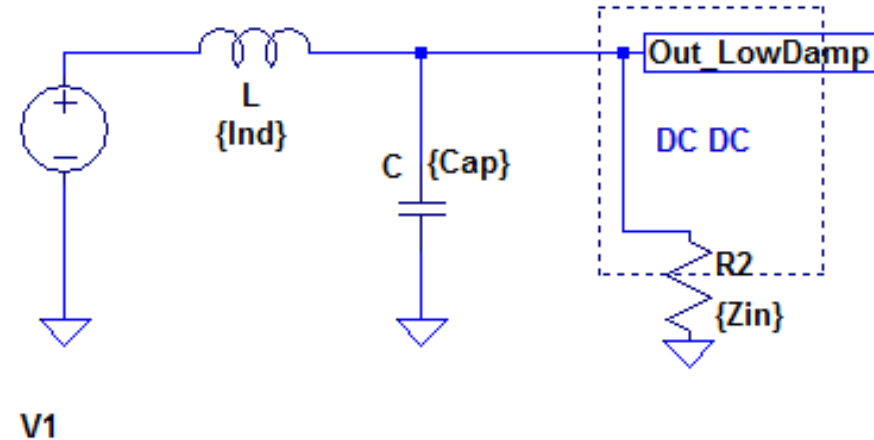

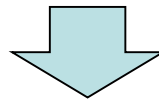- R_L : Rdc of the inductor
- ESR: serie resistance of the capacitor
- Input impedance of the buck converter (looking negative – see previous slide)




- This is a LC filter loaded by a negative resistance!!!!
- NICE WAY TO CREATE OSCILLATORS

Calculating Input Filter Components values → Fx

Gain-Bandwidth product:

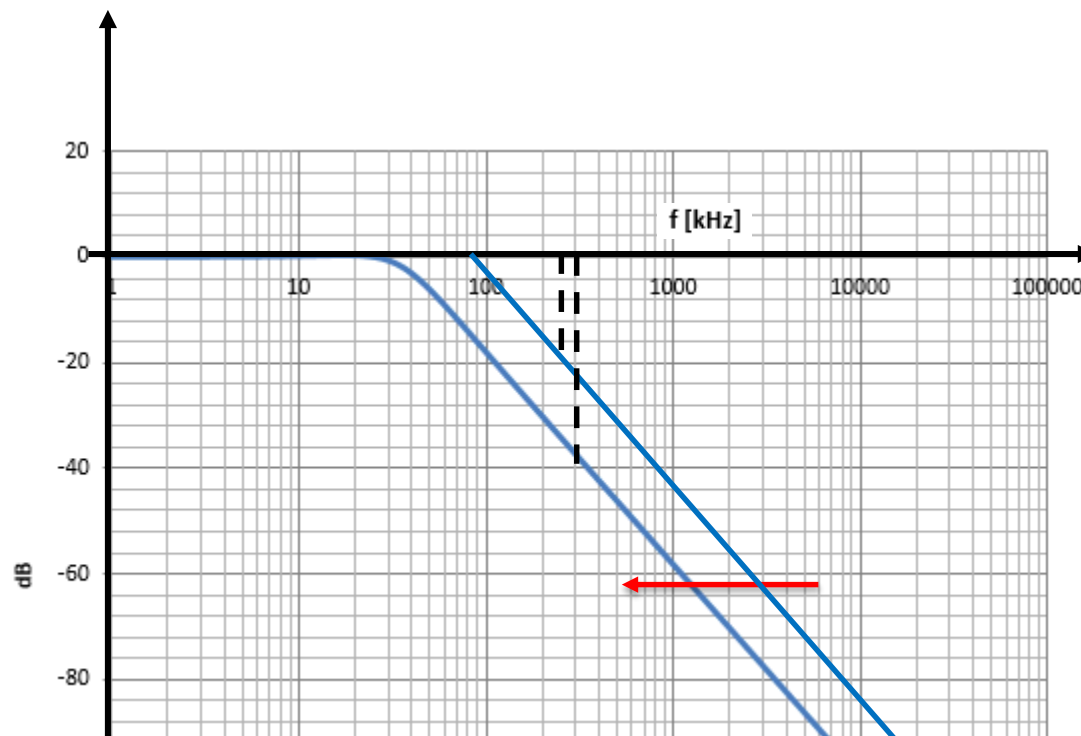Give the right filter cutoff freq to have the attenuation required with the choosen filter topology (order)



$$f_{co} = f_{sw} \cdot 10^{\left(\frac{-A_{db}}{n \cdot 20}\right)}$$

Our design:

Adb: 32 dbuV
 2nd order filter
 Fsw: 150kHz



F_{0calc} : 23 kHz


- **Adb**: attenuation required
- **n**: filter order
- **Fsw**: switching frequency
- **Fco**: filter cut off frequency

Calculating Input Filter Components values → L + C

Selection of the L and C value:

Different values for L and C occurs. In our design we can choose as follows:

C	2,2	uF
L	27	uH

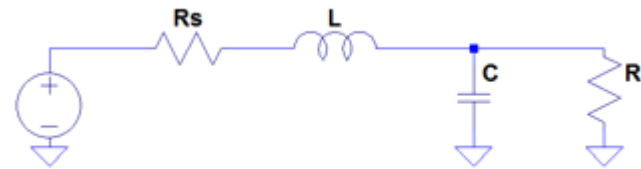


Overshoot

In order to have

$$f_0 = \frac{1}{2 \cdot \pi \cdot \sqrt{L \cdot C}} \approx 21\text{kHz}$$

(20,65kHz calculated)

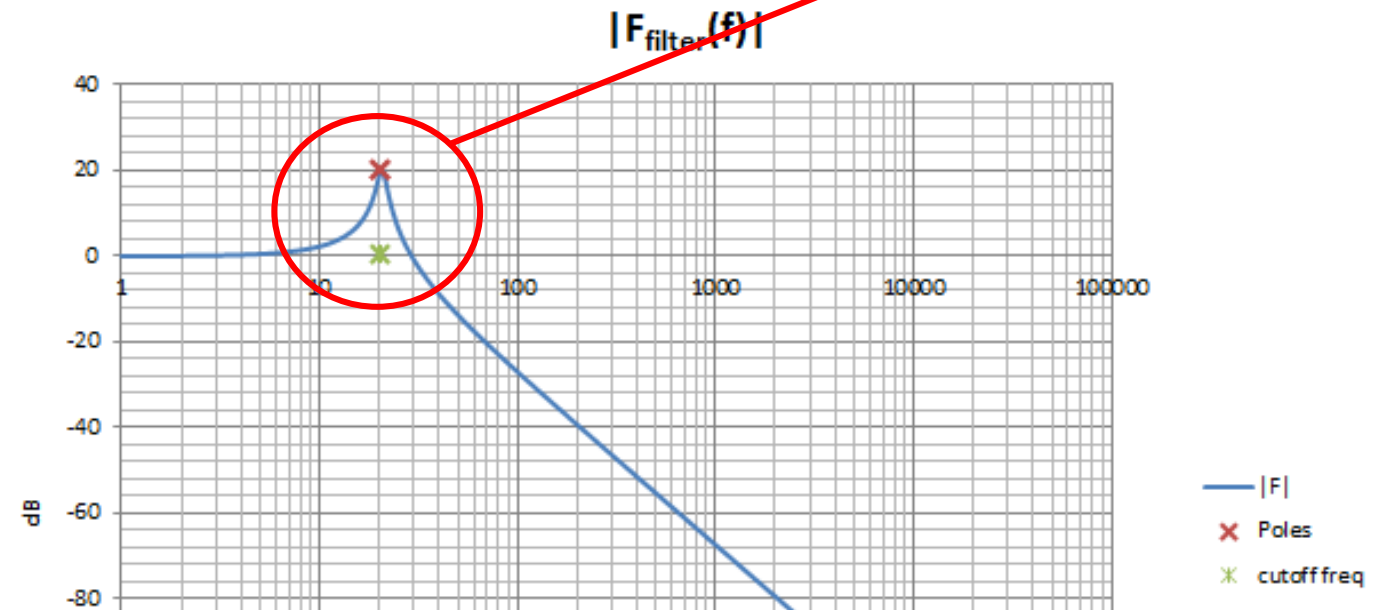

Calculating Input Filter Components values → Cd + Rd

1) Calculate damping capacitor


$$C_d = n \cdot C_f \quad \text{with } n = 4 \text{ or } 6$$

2) Calculate damping Resistor

$$R_d = \sqrt{\frac{L_f}{C_f} \frac{(n+1)}{2n}} \sqrt{\frac{2n^2(4+n)}{(2+n)(4+3n)}}$$



Keeping the same values of undamped filter, we can add an Rd and a Cd as follows:

Rd	3,57548	Ω
Cd	8,8	uF
C	2,2	uF
L	27	uH
n	4	


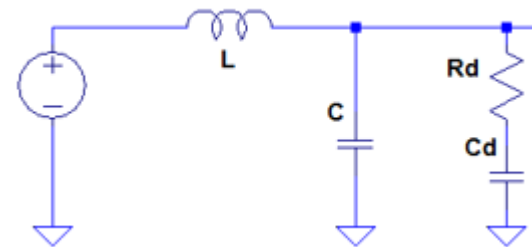


*See Input Filter Design for Switching Power Supplies, Michele Sclocchi – National App Note 2010

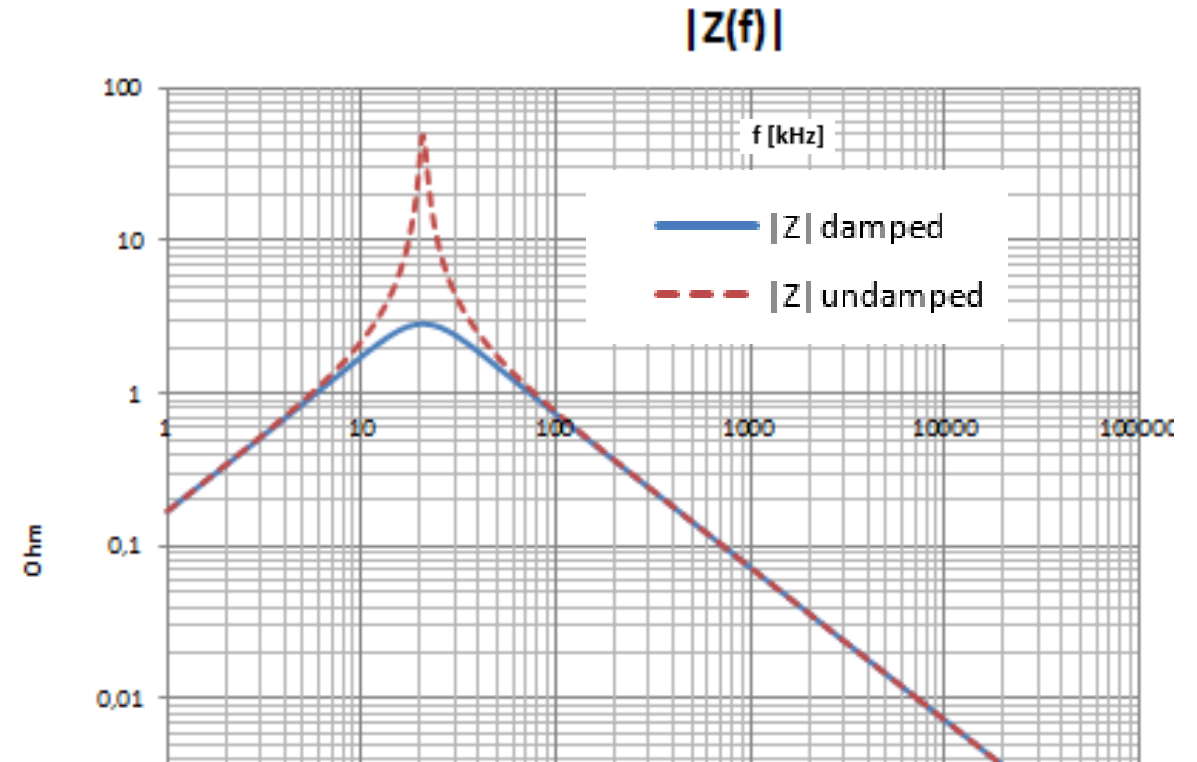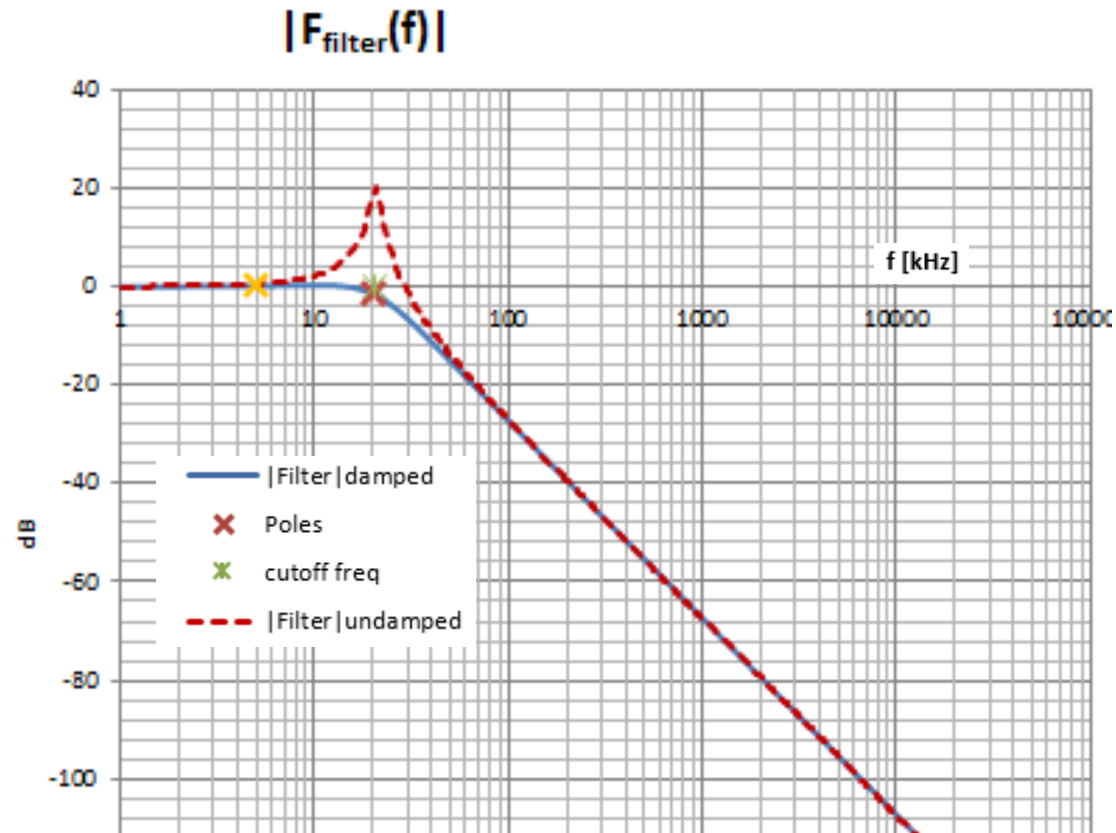
Calculating Input Filter Components values - Damping



Check using LT Spice Simulation

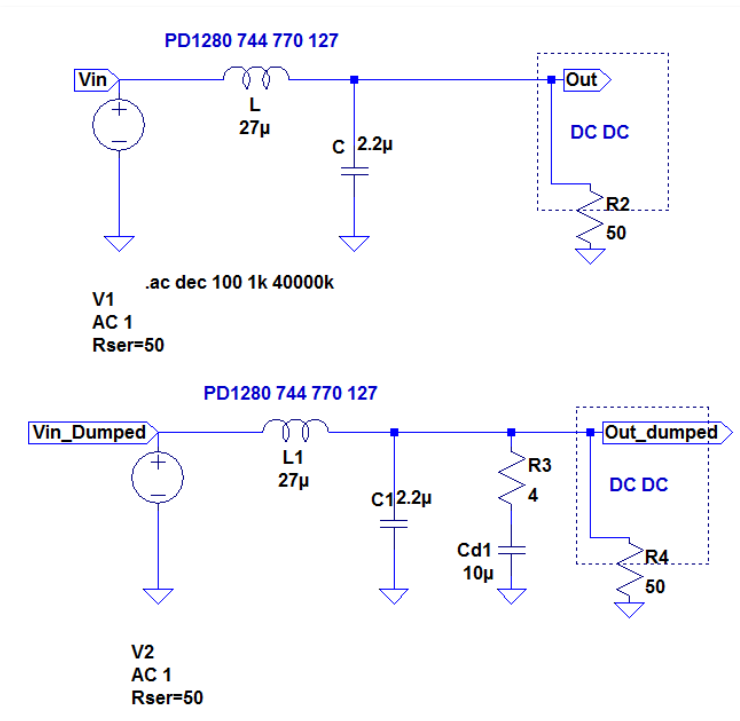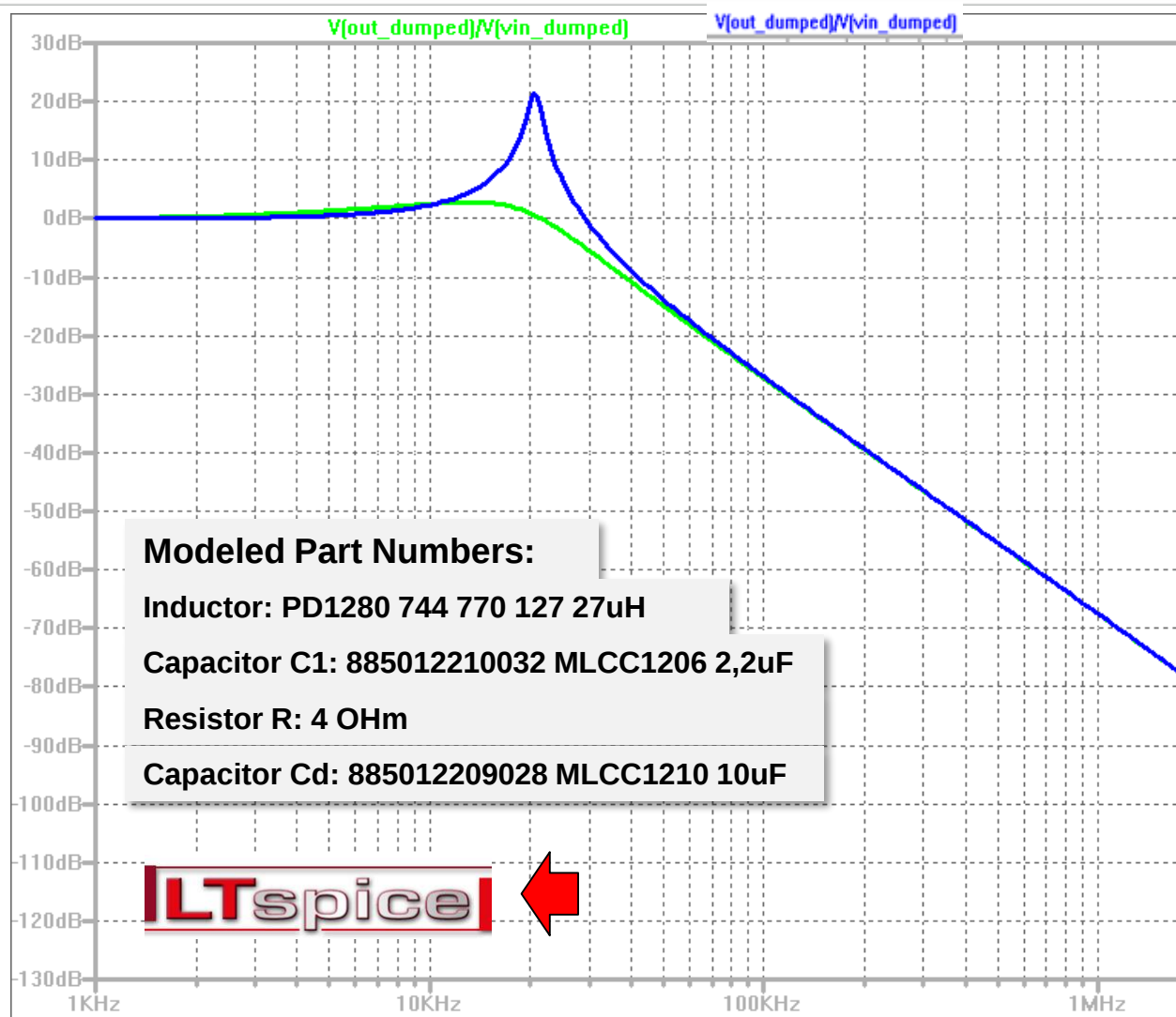

EMI Component for DC/DC Converter

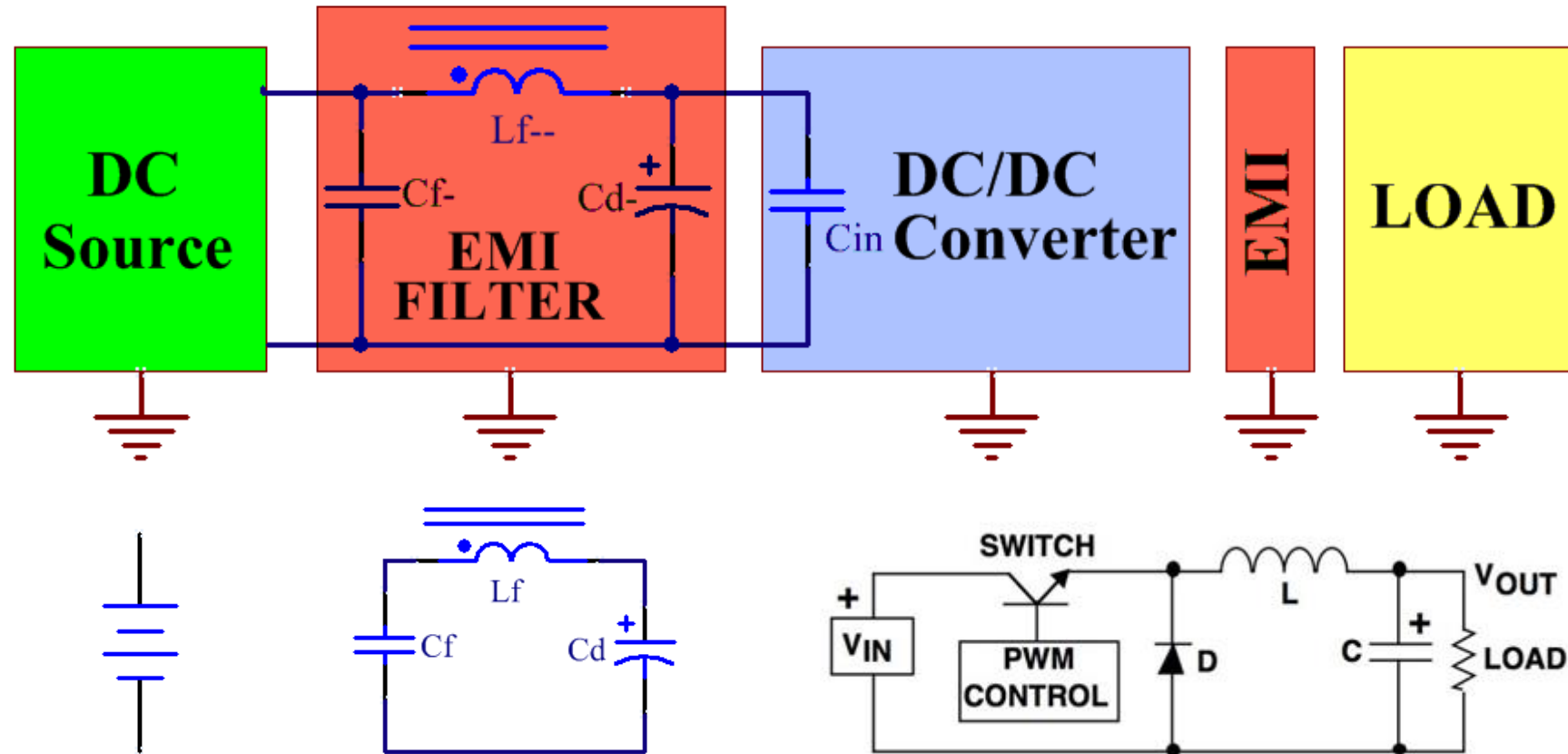


Calculate Required **Attenuation**

- Know input voltage, output voltage and ripple voltage
- Calculate required attenuations using formula
- E.g. to design an input filter for a 12v to 5v converter
 - **V_{ripple} = 0.5v, V_{max} = 7v → 13dB Attenuation(+)**


$$|Attn|_{dB} = 20 \text{ Log } \left(\frac{V_{ripple}}{1\mu V} \right) - V_{max}$$

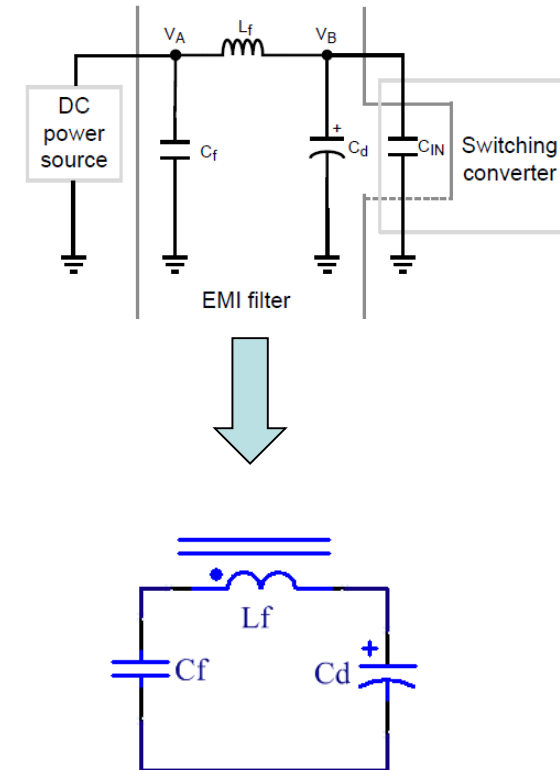* V_{max} is difference between V_{in} and V_{out} (differential noise)



Calculate C_f , L_f and C_d

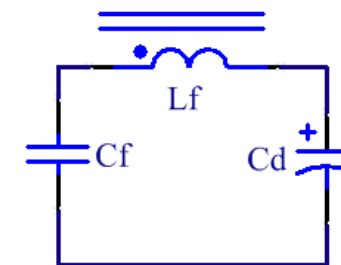- C_f = EMI Filter Capacitance (greater of C_{fa} or C_{fb} , 100nF)
- L_f = EMI Filter Inductance (key EMI resonance value, 5uH)
- C_d = Damping Capacitance (four times bigger than C_{in} , 330nF)




$$C_{fa} = \frac{C_{IN}}{C_{IN} L_f (2\pi f_s / 10)^2 - 1}$$

$$C_{fb} = \frac{1}{L_f} \left(\frac{10^{|Att|_{dB}/40}}{2\pi f_s} \right)^2$$



$$F_{osc} = \frac{1}{2\pi \sqrt{L C}}$$

$$L_F = \frac{1}{C (2\pi F)^2}$$

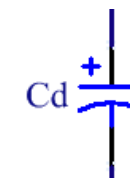

$$C_d \geq 4 \times C_{IN}$$

$$ESR_d \approx \sqrt{L_f / C_{IN}}$$


Lf uH	2xPi	Fs KHz	2PiF	Att dB	Attn/40	10^	Cf nF	Cd uF
5	6.28	500	3140	13	0.325	2.11	91	0.36
10	6.28	500	3140	13	0.325	2.11	45	0.18
100	6.28	500	3140	13	0.325	2.11	5	0.02

- DC/DC Converter Topologies – Buck, boost & SEPIC
- Causes of CM & DM Emissions – LT Spice
- Efficiency and Losses – Core, Copper and AC
- Criteria for selecting Inductor and Capacitor – DC Bias
- Practical Input Filter Design – LC Filter
- **REDEXPERT** – Interactive component selection

REDEXPERT

www.we-online.com/redexpert

REDEXPERT – Demystifying EMC

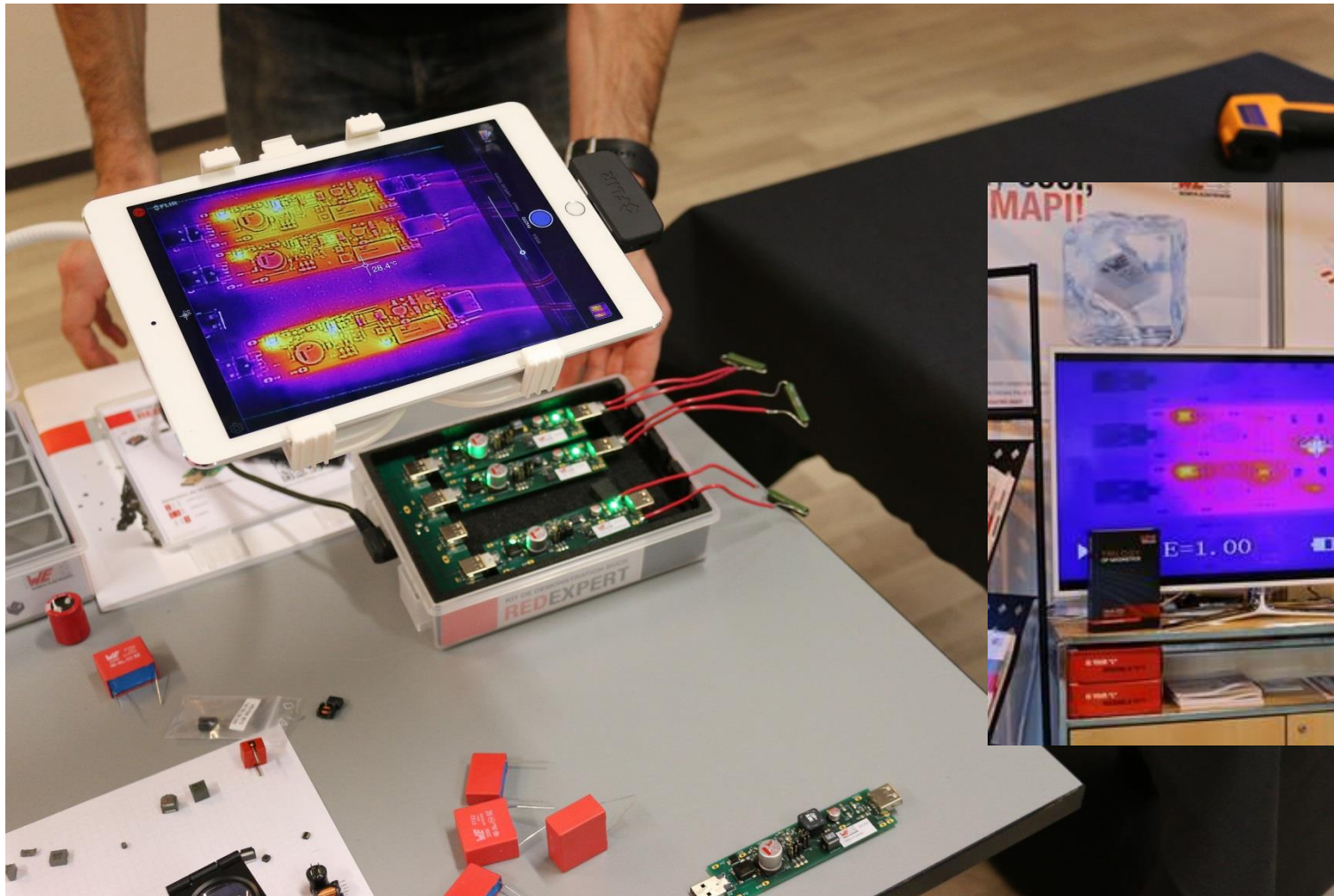

Buck Demo Kit for RED EXPERT


Test
Conditions

Switching frequency:

 200 kHz A B C	 1.6 MHz A B C
 450 kHz A B C	 1.8 MHz A B C
 700 kHz A B C	 2 MHz A B C
 900 kHz A B C	 2.2 MHz A B C

Inductor selection:

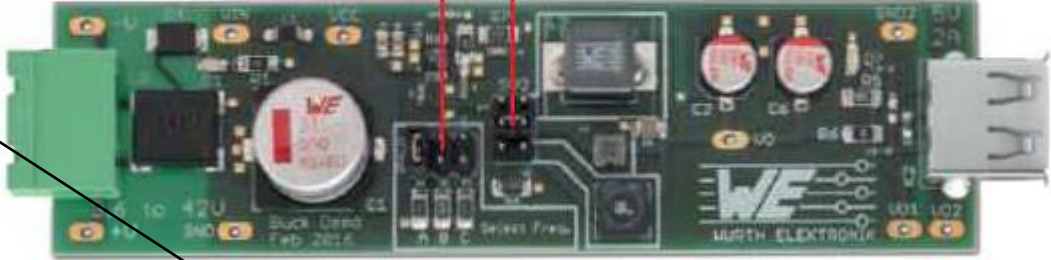-  4.7 µH WE-HCC 744 334 047 0
-  2.2 µH WE-MAPI 744 383 340 22
-  100 µH WE-PD 744 778 520



Inductor selection:

 10 Ω	 5 Ω
 0.5 A	 1.0 A
 3.33 Ω	 2.5 Ω
 1.5 A	 2.0 A

 Additional heatsink recommended for continuous use

Buck Demonstration Kit for RED EXPERT




TECHNICAL DATA:

f_{sw}	200 kHz ~ 2 MHz
V_{in}	4.5 V ~ 40 V
V_{out}	5 V
I_{out}	2 A / 3 A peak


Order Code 988 141
Version 1.0

Switching Frequency: **200KHz** vs **2MHz**


Ambient
SAT
22.9°C

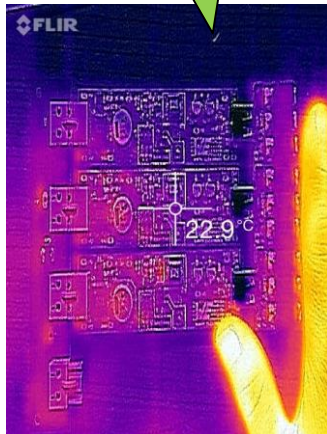

9Vin,
5Vo,
2.5W,
200KHz

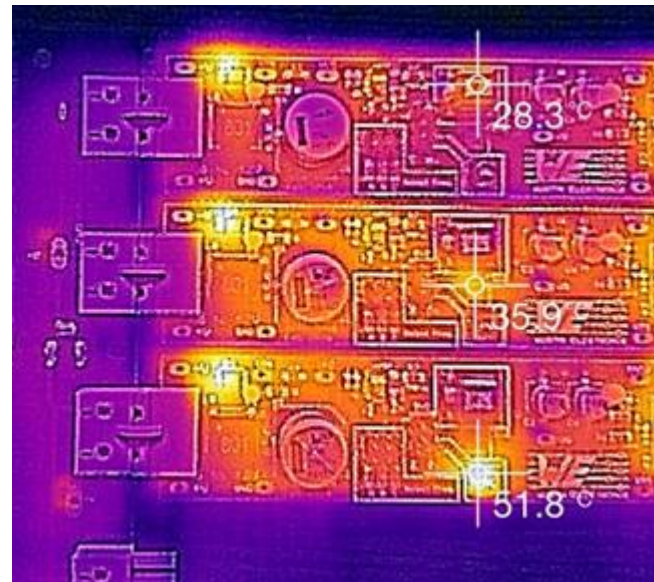

9Vin,
5Vo,
2.5W,
2MHz

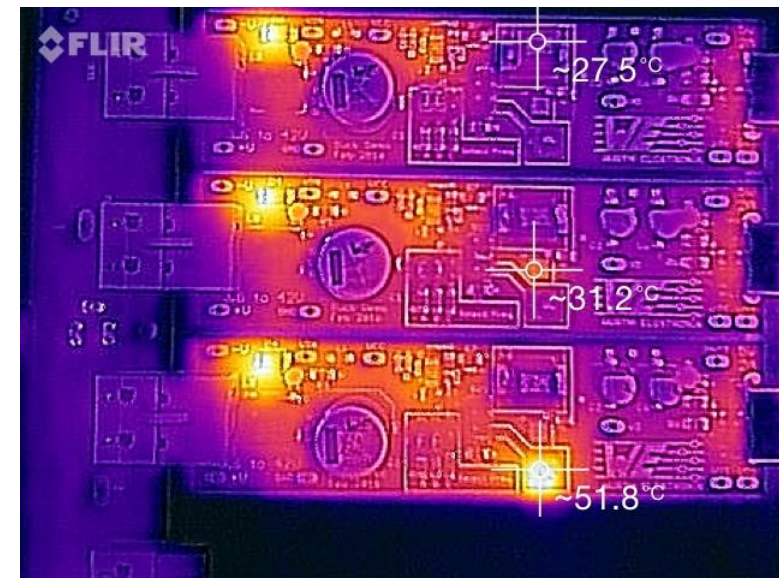

- <http://we-online.com/re/3bJFP7JE>

Filters: Order Code $\ni$ 7443340470, 74438334022, 744778520 $\times$ Type = Single $\times$

	Order Code	Series	Size	Spec	Type	L	L() @39...	R _{DC,typ}	I _R	I _{sat}	P _{AC}	P _{DC}	P _{TOT}	ΔT
✓	7443340470	WE-HCC	8070		Single	4.70 μ H	4.60 μ H	12.7 m Ω	7.50 A	8.00 A	64.6 mW	3.18 mW	67.8 mW	7.15 K
✓	74438334022	WE-MAPI	3012		Single	2.20 μ H	2.20 μ H	100 m Ω	1.80 A	5.00 A	74.6 mW	25.0 mW	99.6 mW	15.1 K
✓	744778520	WE-PD	6033		Single	100 μ H	99.0 μ H	950 m Ω	650 mA	500 mA	4.19 mW	238 mW	242 mW	26.3 K

Buck Converter $\times$

Reapply

PARAMETERS EDIT

Input	Output	Switch	Inductor	Diode
8.20 V 8.00-10.0 V	4.90 V 500 mA	200 kHz	40 % Single	0.30 V

DETAILS

I _{rms} ≥ 500 mA	I _{max} ≥ 600 mA	L _{opt} 50.5 μ H
-----------------------------------	-----------------------------------	----------------------------------

200KHz vs 2MHz

Buck Converter $\times$

Reapply

PARAMETERS EDIT

Input	Output	Switch	Inductor	Diode
8.20 V 8.00-10.0 V	4.90 V 500 mA	2 MHz	40 % Single	0.30 V

DETAILS

I _{rms} ≥ 500 mA	I _{max} ≥ 600 mA	L _{opt} 5.05 μ H
-----------------------------------	-----------------------------------	----------------------------------

Filters: Order Code $\ni$ 7443340470, 74438334022, 744778520 $\times$ Type = Single $\times$

	Order Code	Series	Size	Spec	Type	L	L() @39...	R _{DC,typ}	I _R	I _{sat}	P _{AC}	P _{DC}	P _{TOT}	ΔT
✓	7443340470	WE-HCC	8070		Single	4.70 μ H	4.60 μ H	12.7 m Ω	7.50 A	8.00 A	17.7 mW	3.18 mW	20.9 mW	2.70 K
✓	74438334022	WE-MAPI	3012		Single	2.20 μ H	2.20 μ H	100 m Ω	1.80 A	5.00 A	20.5 mW	25.0 mW	45.5 mW	7.90 K
✓	744778520	WE-PD	6033		Single	100 μ H	99.0 μ H	950 m Ω	650 mA	500 mA	537 μ W	238 mW	239 mW	26.1 K

User Interface



Würth Elektronik Group Sign in English

more than you expect

SELECTION TABLE

Power Inductors **REDEXPERT®**

- Converter
- Buck
- Boost
- SEPIC
- Losses

✓	Series	Order Code	Spec	Type	L	R _{DC,typ}	I _R	I _{sat}	Size	Length	Width	Height
✓	WE-MAPI	744383130068	PDF	Single	680 nH	101 mΩ	1.55 A	3.80 A	1610	1.6 mm	1.6 mm	0.90
✓	WE-MAPI	744383130082	PDF	Single	820 nH	115 mΩ	1.45 A	3.60 A	1610	1.6 mm	1.6 mm	0.90
✓	WE-MAPI	74438313010	PDF	Single	1.00 µH	127 mΩ	1.40 A	3.40 A	1610	1.6 mm	1.6 mm	0.90
✓	WE-MAPI	74438313012	PDF	Single	1.20 µH	140 mΩ	1.30 A	3.20 A	1610	1.6 mm	1.6 mm	0.90



Design Tools

744383130068
 WE-MAPI · 1610
 680 nH · 101 mΩ
 1.55 A · 3.80 A

Drop Order Codes in the bar to add
 Drag out buttons to delete them

STORAGE



Share
 Free Samples
 Tidy Up

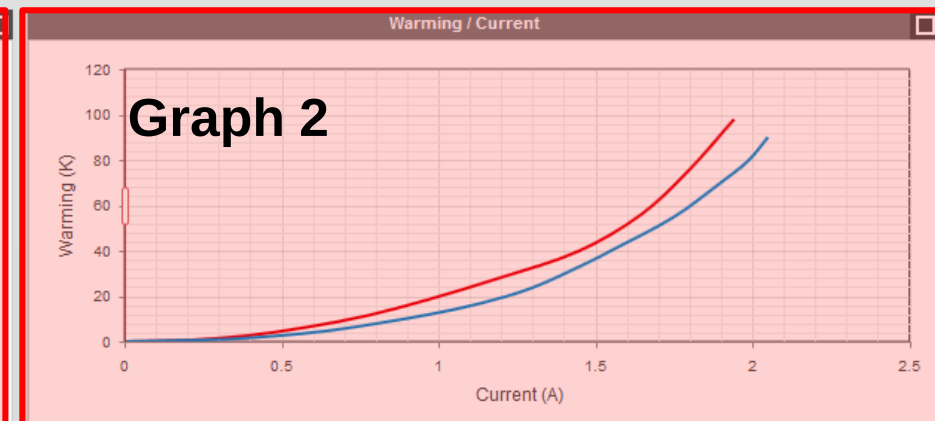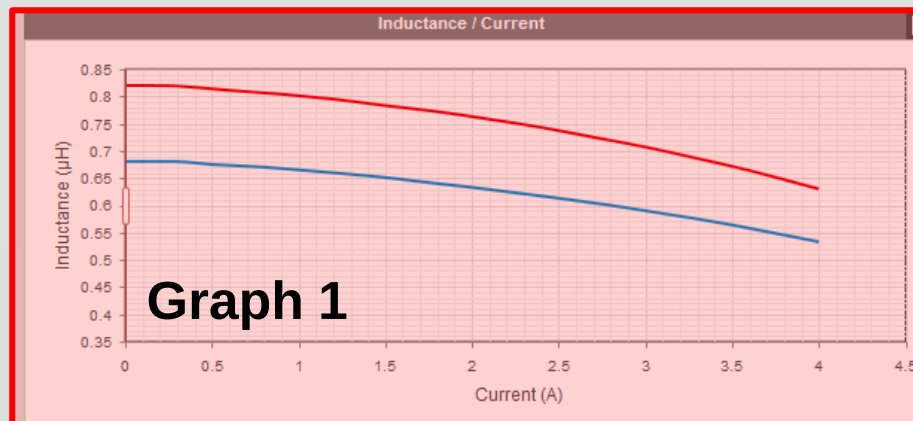

Contact | Imprint | Copyright © 2015 Würth Elektronik GmbH. All rights reserved.


World's Most Accurate AC Loss Model – Wave Signal

Würth AC Loss Model

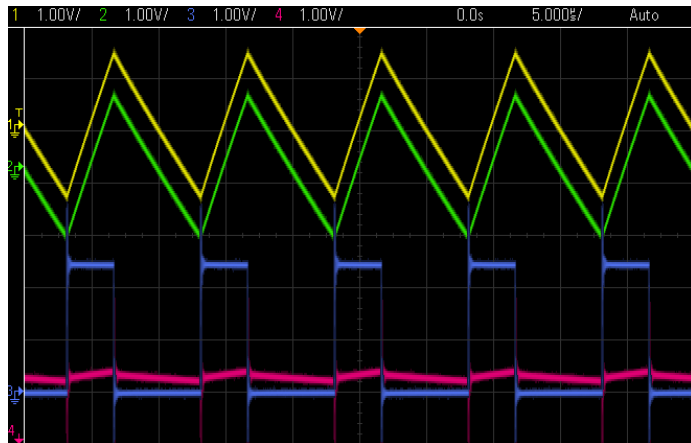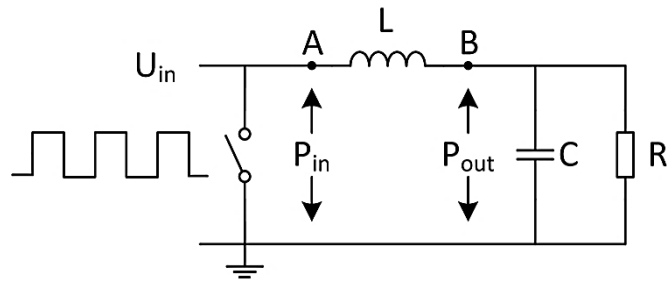

Simple Class-D Amplifier

Steinmetz Models

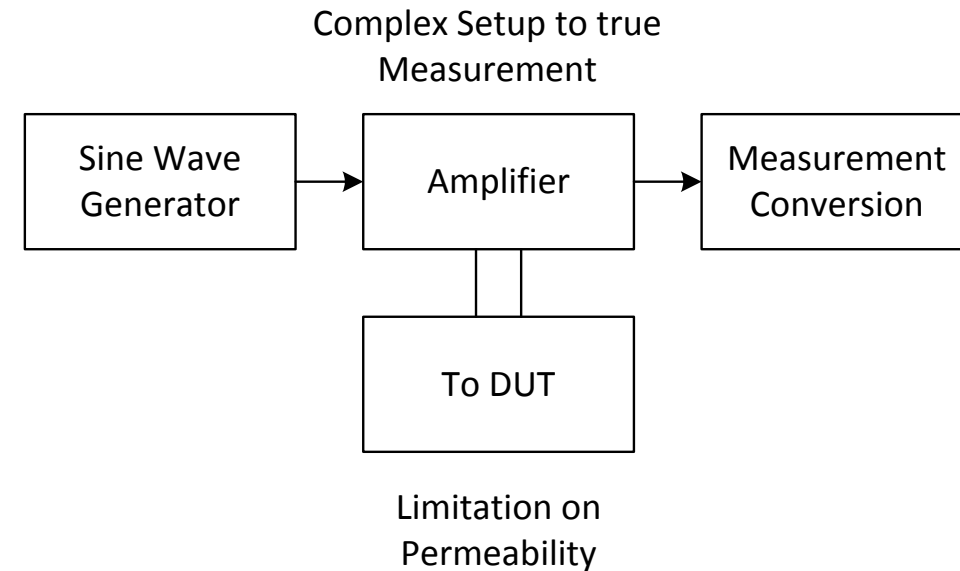


Complex Setup to Measure

World's Most Accurate AC Loss Model – **Signal Loop**

Würth AC Loss Model

$$P_{AC} = f(\Delta I, \text{freq}, DC, k1, k2)$$

➡ Core Loss & AC Wire Loss

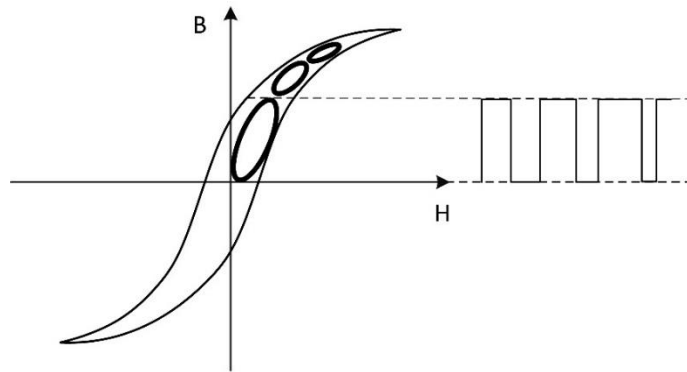

Point of Operation Approach
 ➡ Triangular current form


Steinmetz Models

$$P_V = K \cdot f^\alpha \cdot \Delta B^\beta$$

$$P_V = K \cdot f^{\alpha-1} \cdot \Delta B^\beta \times f^r$$

$$P_V = K \cdot f_{eq}^\alpha \cdot \Delta B^\beta$$


➡ Core Loss Only

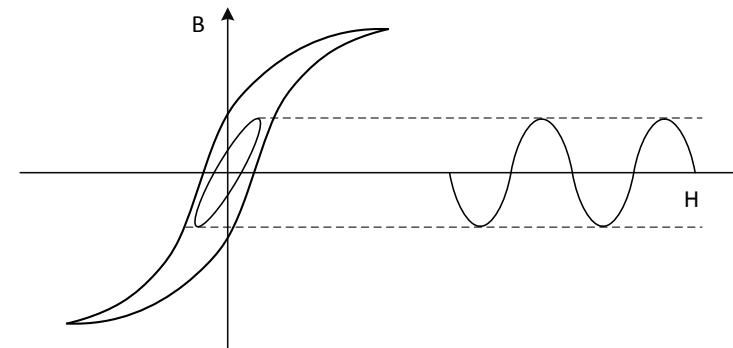

Major Loop Approach
 ➡ only sine wave


World's Most Accurate AC Loss Model – Duty Cycle

Würth AC Loss Model

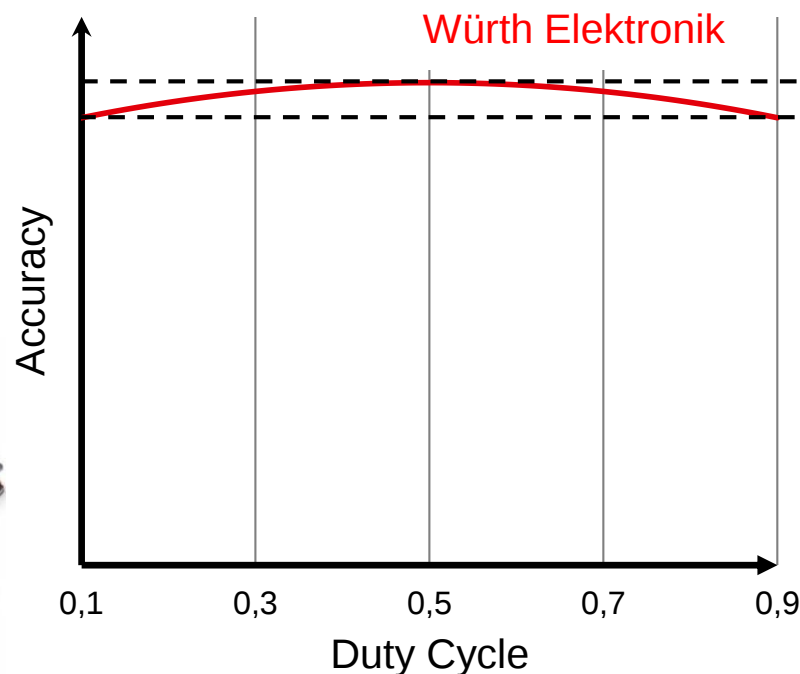


**Highest Accuracy
over wide DC range**

Steinmetz Models

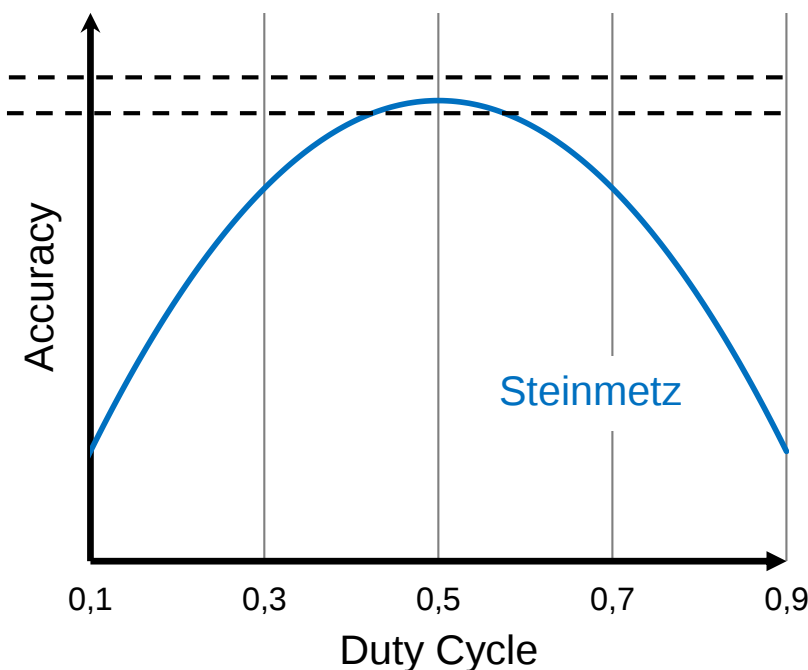

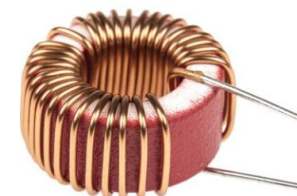**Acceptable Accuracy at 50%,
even worse for other DC**



World's Most Accurate **AC Loss Model**

Würth AC Loss Model:

- Based on real time application set up and measurements
- A pulsating input voltage is applied over the real inductor
- The input and output power is measured
- This process is repeated over wide range of parameters
incl. variation of peak flux density swing to produce our own empirical data
- This empirical data is used to create the equation for Würth AC Loss Model

Advantages:

- Accurate calculation of losses for any given Duty Cycle
- Accurate over wide range of frequency (10 kHz to 10 MHz)
- Considers even small change in core material and winding structure

All Inclusive – Full On Board **Dc/Dc Modules**



OR

Wanted!
Easy Power & EMI solution:
Magl³C

Keep It Simple

& Let the MAGIC Begin

MAGI3C Buck Boost

Thank you

Any Questions

