

Würth Electronics (UK) Ltd



Practical EMI Filter Design Considerations – Part 2

19th September 2017

Presented by

Mohamed AlAlami
Field Application Engineer - UK

Agenda


- **DC/DC Converter Topologies**
- **Inductor and Capacitor Selection Parameters**
- **Efficiency and Losses**
- **REDEXPERT**
- **Practical DC/DC Converter Input Filter Design Considerations**



DC/DC CONVERTER TOPOLOGIES

DC to DC Converter Topologies


■ DC/DC converter topologies

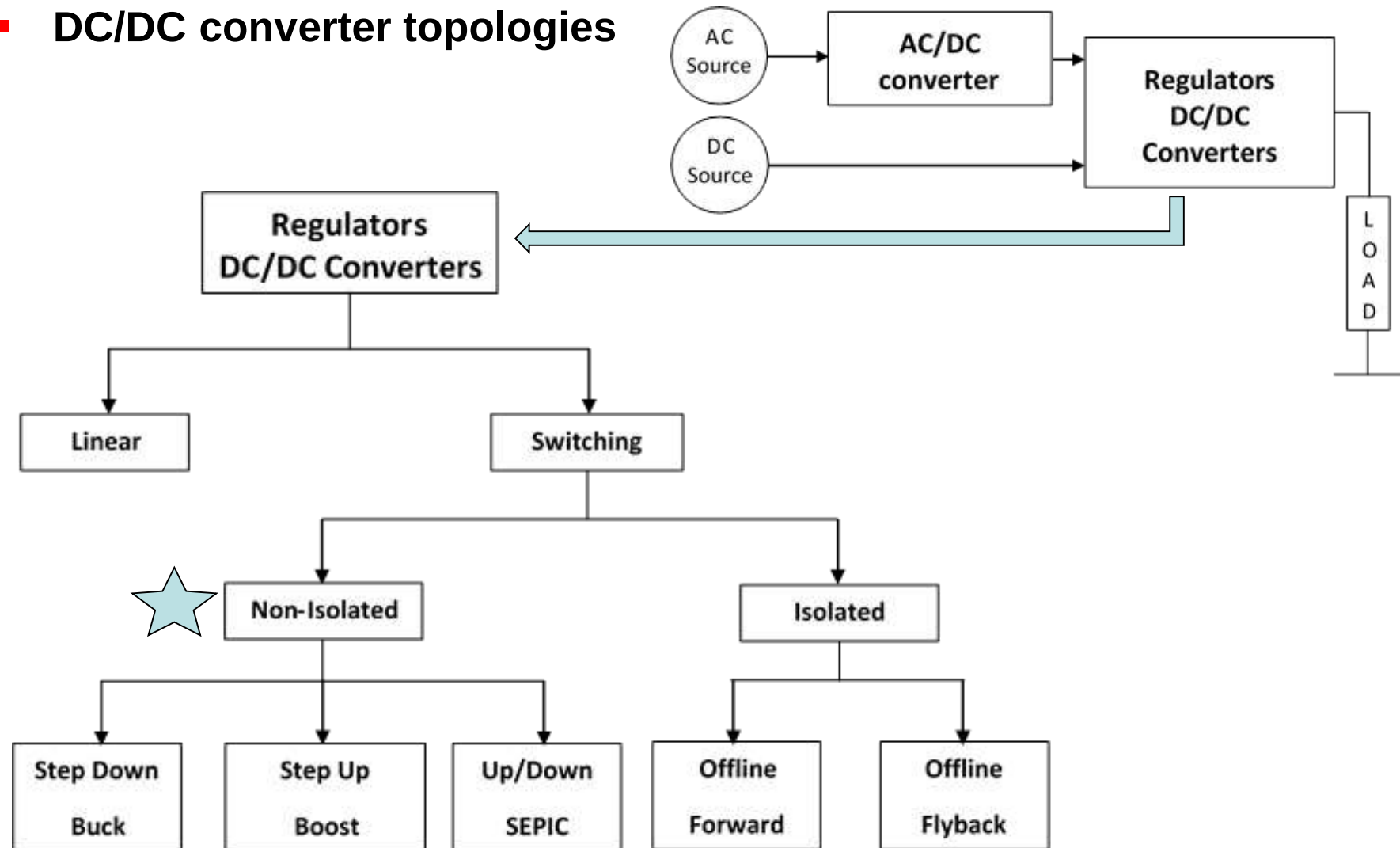

The Buck Converter

■ The Buck Converter (Step Down)

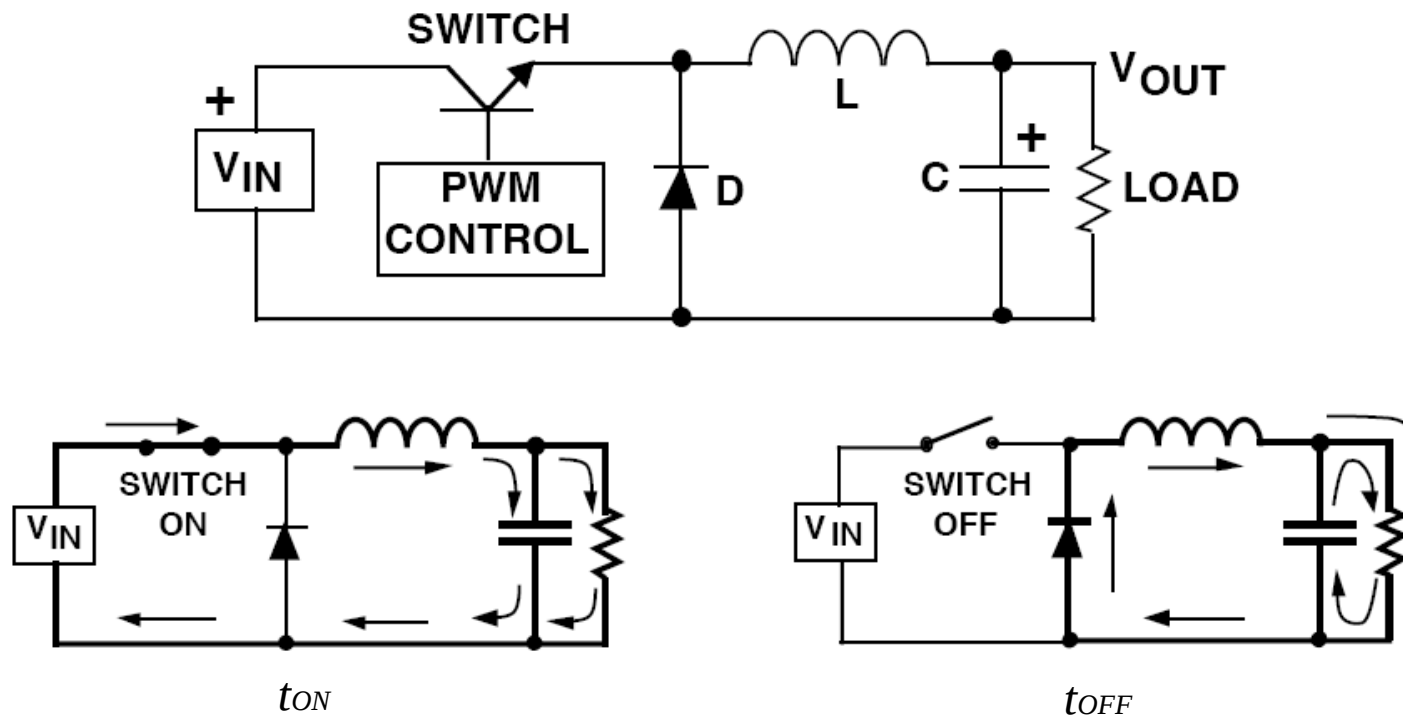
- Converts a DC voltage to a lower DC voltage with the same polarity
- Continuous and discontinuous conduction modes (CCM and DCM)



The Buck Converter

■ Effects of ripple current (ΔI_L):

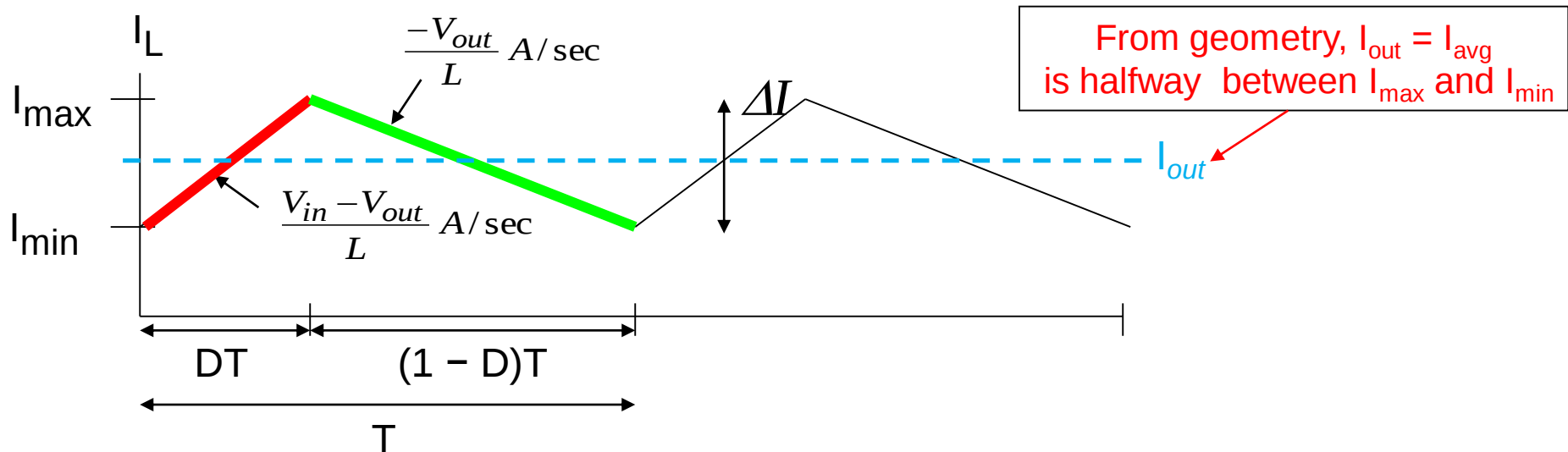
$$\Delta I = \frac{V_{in} - V_{out}}{L} \times D \times T$$



- CCM operation
- Output voltage ripple (with the ESR of C_{out})
- Core losses in the inductor
- Emissions

The Buck Converter

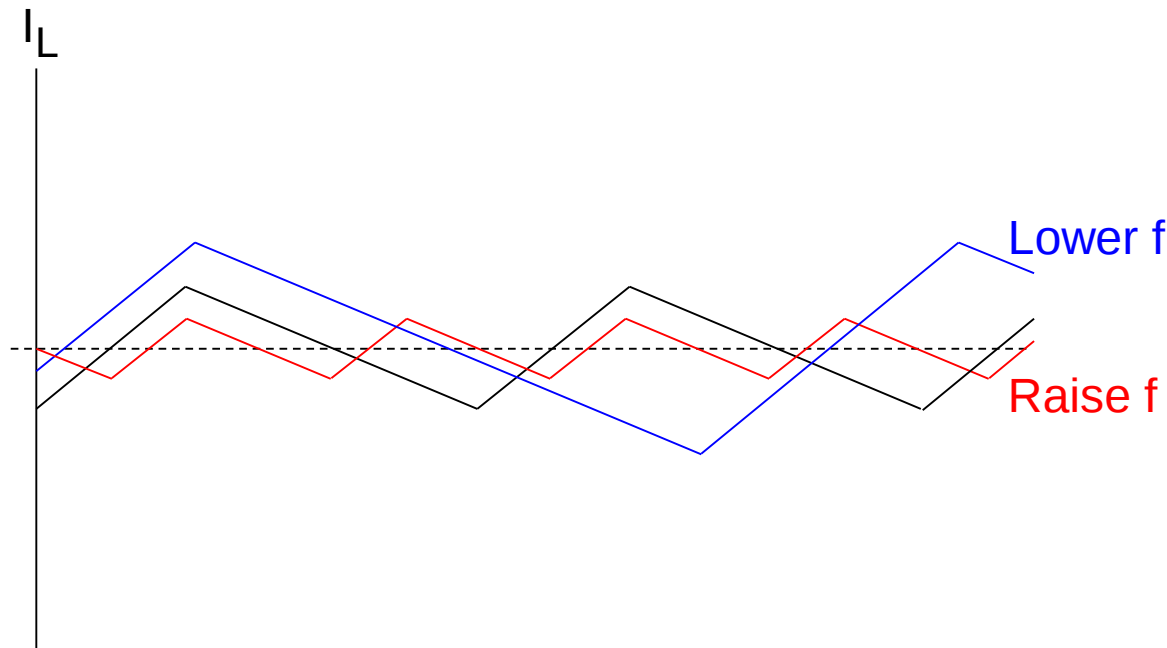
- Effects of changing switching frequency (f_s):



- Slope of I_L unchanged
- Lowering f_s increases ΔI and can move the circuit towards DCM

The Buck Converter

■ Effects of changing inductance (L):

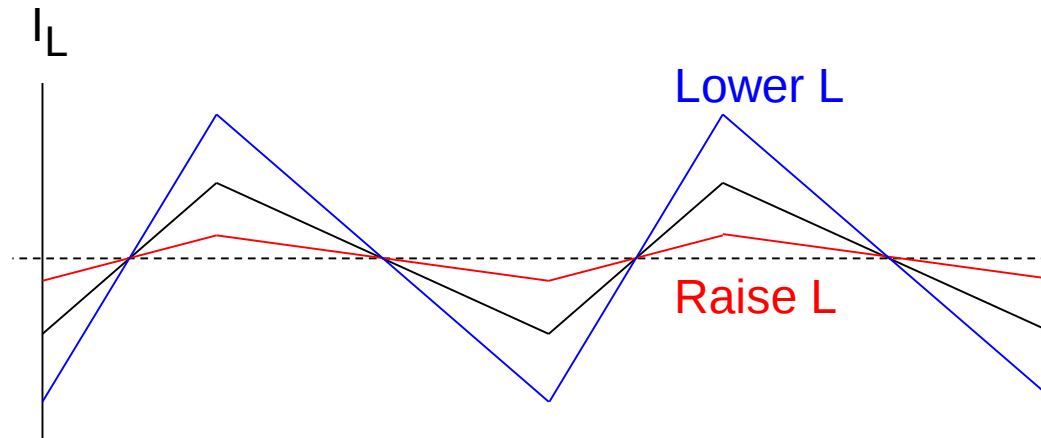

- Slope of I_L changed
- Lowering L increases ΔI and can move the circuit towards DCM

The Buck Converter

■ Calculating inductance value (L):

$$L = \frac{(V_{in} - V_{out})}{\Delta I} \times D \times T$$

Re-write as ➡


$$L = \frac{V_{out} \cdot (1 - D)}{f_{switch} \cdot r \cdot I_{out}}$$

where r is the percentage ripple of the output load current.

■ Critical inductance value ($L_{critical}$):

- At Boundary of CCM/DCM ($\Delta I = 2I_{out}$)
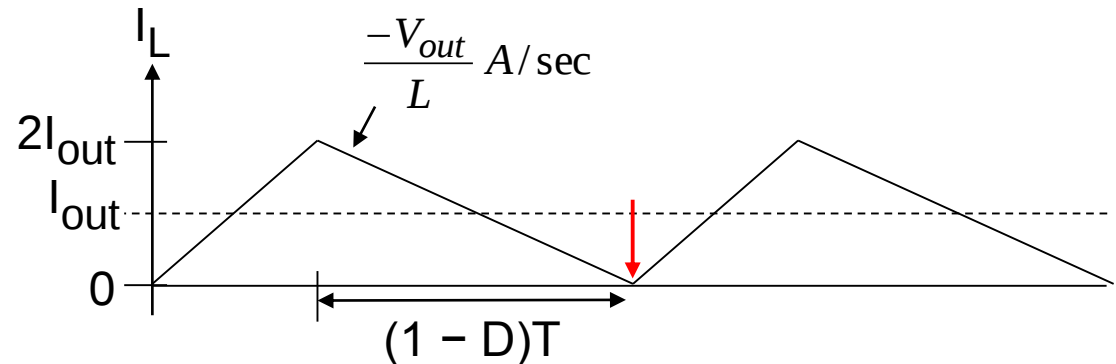
$$L_{Critical} > \frac{V_{out} (1 - D_{min})}{2I_{out_min} \cdot f_{switch}}$$



The Buck Converter


■ Calculating capacitance value (C):

$$C = \frac{\Delta I}{8 \cdot f_s \cdot \Delta V_{out}}$$

where ΔV_{out} is the specified maximum output voltage ripple.

Remember:
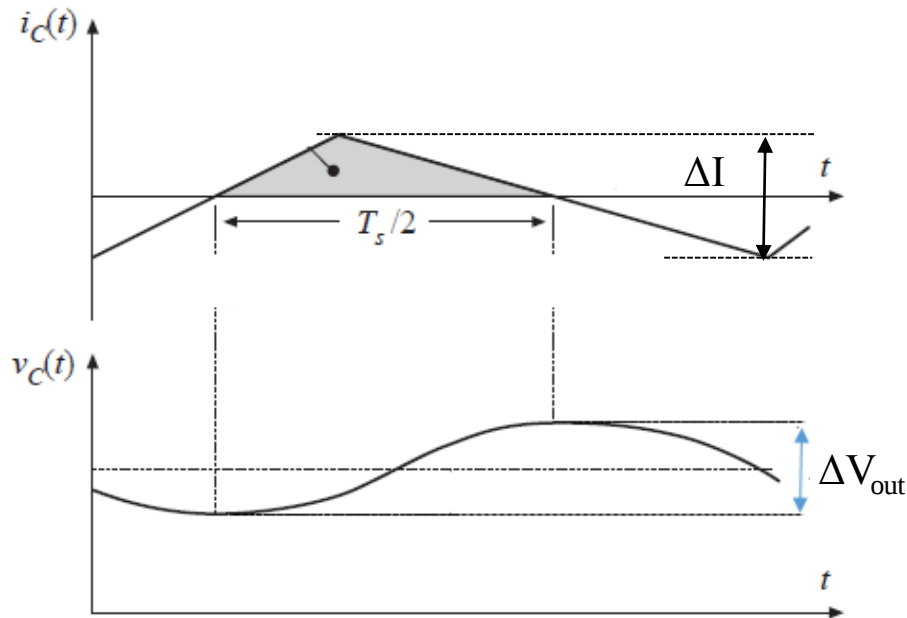
$$ESR \ll \frac{\Delta V_{out}}{\Delta I}$$




■ Considering Dynamic response

The Boost Converter

■ The Boost Converter (Step Up)

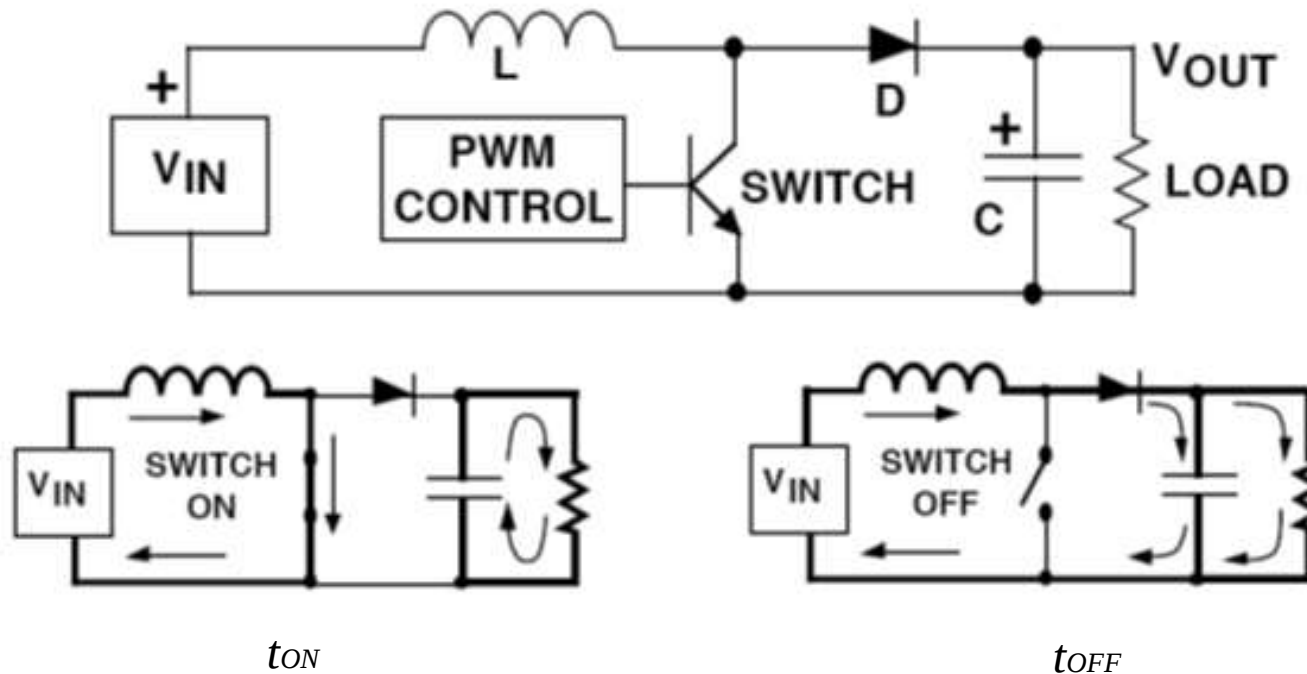
- Converts a DC voltage to a higher DC voltage with the same polarity
- Continuous and discontinuous conduction modes (CCM and DCM)



The Boost Converter

■ Effects of ripple current (ΔI_L):
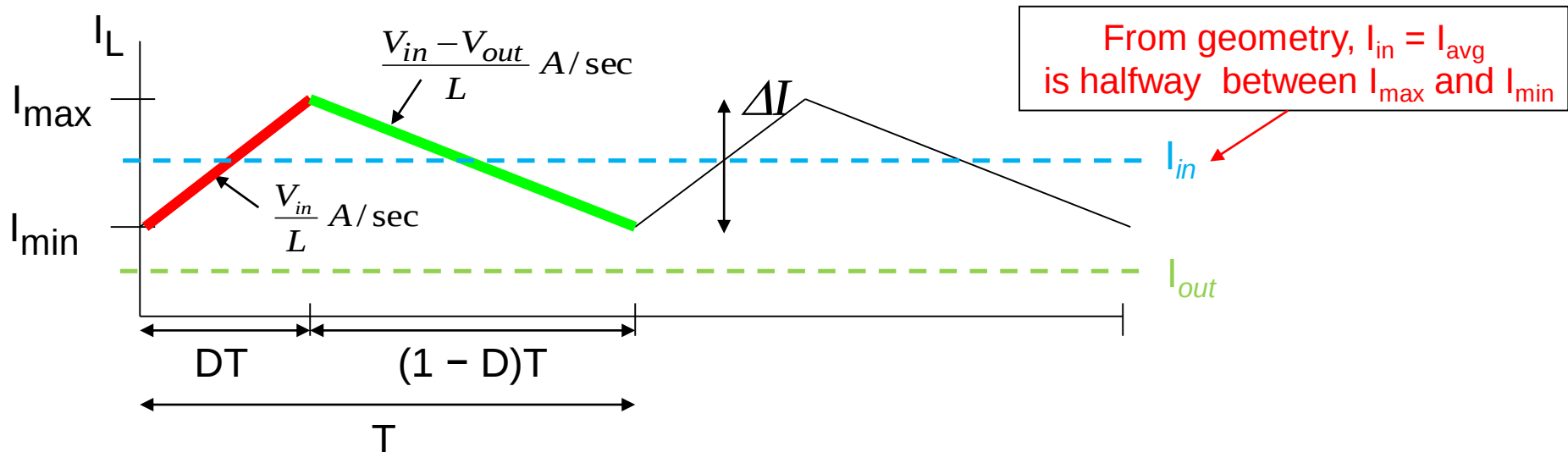
$$\Delta I = \frac{V_{in}}{L} \times D \times T$$



- CCM operation (as with the Buck)
- Output voltage ripple (with the ESR of C_{out})
- Core losses in the inductor
- Emissions

The Boost Converter

■ Calculating inductance value (L):

$$L = \frac{V_{in}}{\Delta I} \times D \times T$$

Re-write as ➡


$$L = \frac{D \cdot V_{out} \cdot (1 - D)^2}{f_{switch} \cdot r \cdot I_{out}}$$

where r is the percentage ripple of the input inductor current.

■ Critical inductance value ($L_{critical}$):

- At Boundary of CCM/DCM ($\Delta I = 2I_{in}$ and $D = 0.33$)



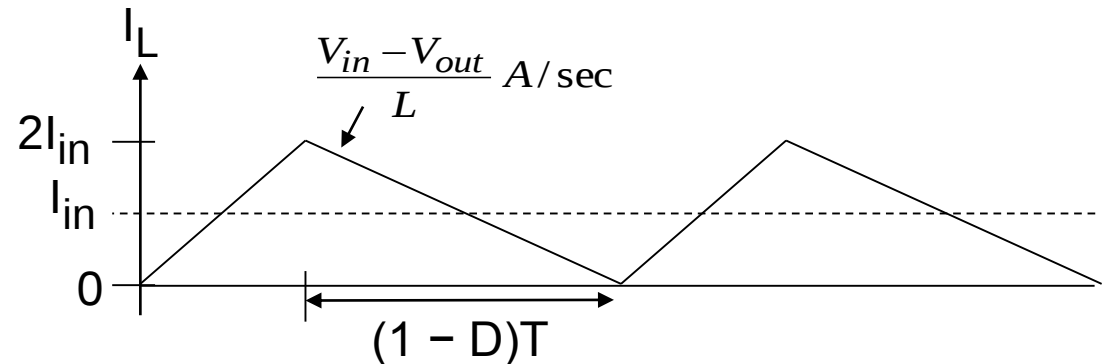
$$L_{Critical} > \frac{V_{out} \cdot D_{0.33} \cdot (1 - D_{0.33})^2}{2I_{out_min} \cdot f_{switch}}$$



The SEPIC Converter


■ The SEPIC Converter (Buck-Boost)

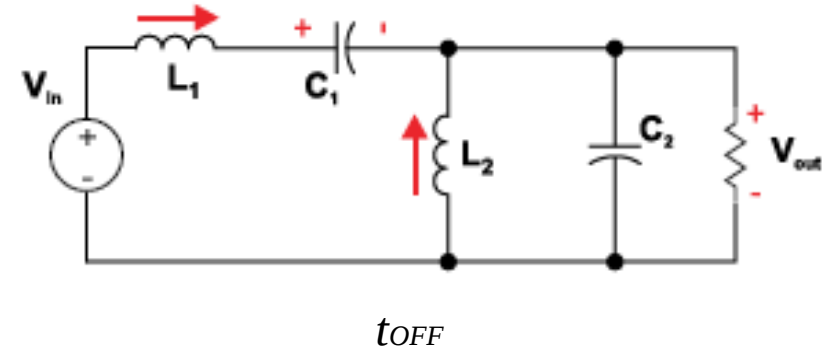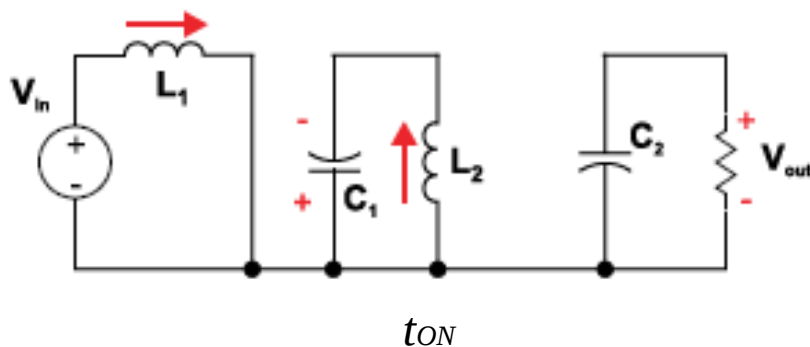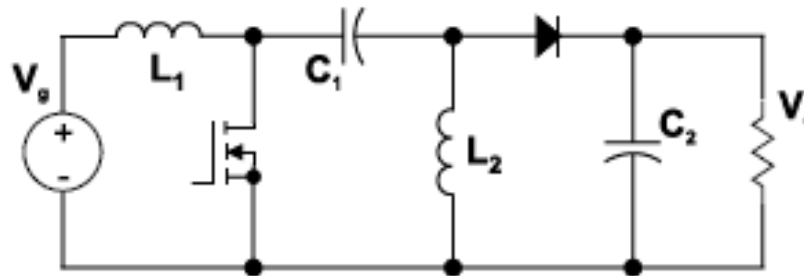- Single Ended Primary Inductance Converter
- Converts a DC voltage to a lower or higher DC voltage with the same polarity



The SEPIC Converter

■ Single Inductors vs a Coupled Inductor

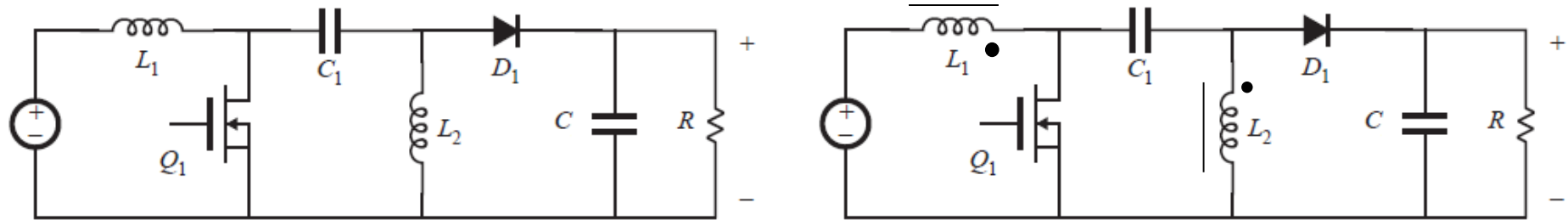


- A coupled inductor is often selected due to:
 - Lower inductance requirement compared to using two single inductors (half).
 - Reduced component count,
 - Improved efficiency,
 - Reduced circuit area
 - Less cost
 - Input ripple current cancellation (resulting in smaller input capacitor and simpler EMI input filter)



INDUCTOR AND CAPACITOR SELECTION PARAMETERS

Inductor Selection Parameters




■ Power Inductor Categories:

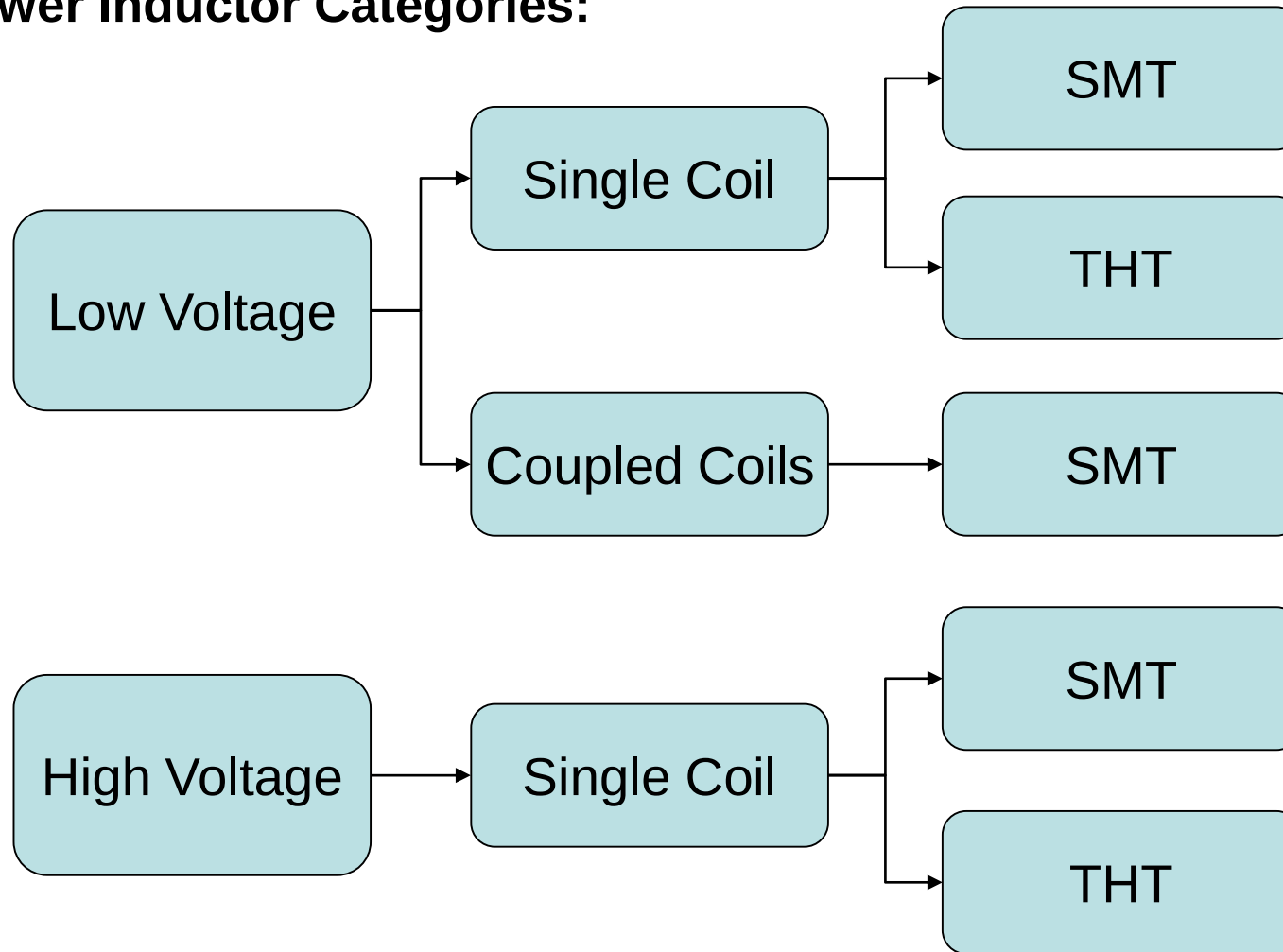

Inductor Selection Parameters



■ Inductor Catalogue Parameters:

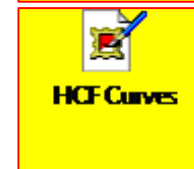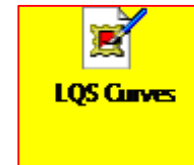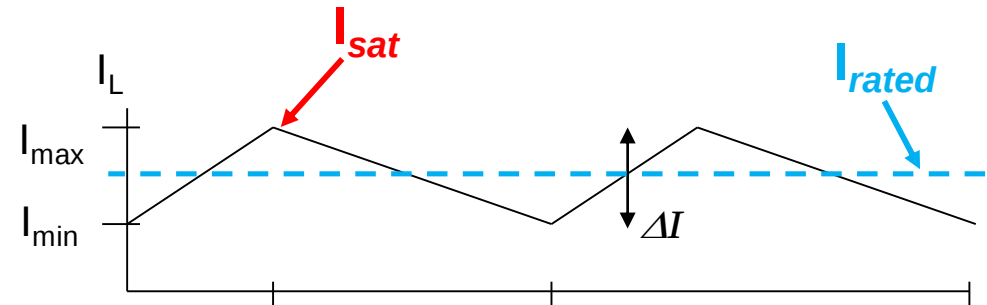- Rated Current
- Saturation Current
- R_{DC}
- Resonant Frequency/Q
- Impedance vs Frequency Curve
- Inductance vs Current Curve
- Temperature rise vs Current Curve



Inductor Selection Parameters

■ Saturation Current

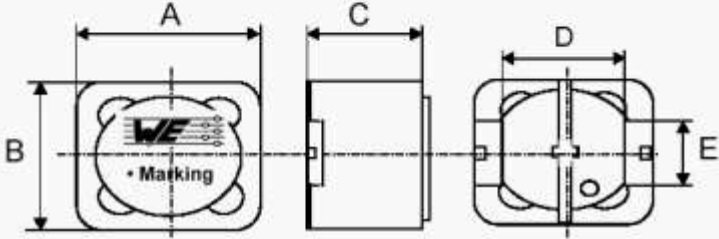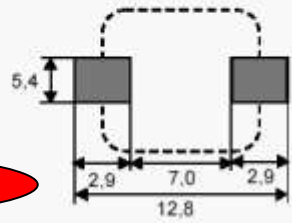Spezifikation für Freigabe / specification for release					
Kunde / customer : _____					
Artikelnummer / part number : 7447709001/LF					
Bezeichnung : SPEICHERDROSSEL WE-PD					
description : POWER-CHOKE WE-PD					
 					
DATUM / DATE : 2004-06-03					
A Mechanische Abmessungen / dimensions:			Typ XXL		
			A	12,0 ± 0,5	mm
			B	12,0 ± 0,5	mm
			C	10,0 max.	mm
			D	7,6 ref	mm
			E	5,0 ref	mm
			F		mm
● = Start of winding Marking = Inductance code					
B Elektrische Eigenschaften / electrical properties:			C Lötpad / soldering spec.:		
Eigenschaften / properties	Testbedingungen / test conditions		Wert / value	Einheit / unit	tol.
Induktivität / inductance	1 kHz / 0,25V	L_N	1,0	μH	±20%
DC-Widerstand / DC-resistance	@ 20°C	$R_{DC \text{ typ}}$	3,86	m Ω	typ.
DC-Widerstand / DC-resistance	@ 20°C	$R_{DC \text{ max}}$	5,60	m Ω	max.
Nennstrom / rated current	$\Delta T = 10 \text{ K}$	I_{DC}	15,00	A	max.
Sättigungsstrom / saturation current	$ \Delta L/L < 10\%$	I_{sat}	25,00	A	typ.
Eigenres.-Frequenz / self-res.-frequency		SRF	120,0	MHz	typ.
					

Inductor Selection Parameters

=> *Print in the data sheet and in the catalogue, drop of the inductance value*

Spezifikation für Freigabe / specification for release

Kunde / customer : _____
 Artikelnummer / part number : 7447709001/LF
 Bezeichnung : SPEICHERDROSSEL WE-PD
 description : POWER-CHOKE WE-PD

LEAD FREE
 WÜRTH ELEKTRONIK

DATUM / DATE : 2004-06-03

A Mechanische Abmessungen / dimensions

Typ XXL		
A	12,0 ± 0,5	mm
B	12,0 ± 0,5	mm
C	10,0 max.	mm
D	7,6 ref	mm
E	5,0 ref	mm
F		mm



Electrical Parameters

Parameter	Value	Unit
Inductance @ 1 kHz / 0,25V	L_N	1,0
DC Resistance @ 20°C	$R_{DC\ typ}$	3,86
DC Resistance @ 20°C	$R_{DC\ max}$	5,60
DC Current	I_{DC}	12,00
Inductance Tolerance	$ \Delta L/L < 10\%$	
Saturation Current	I_{sat}	25,00
Self-Resonant Frequency	SRF	

C Lötpad / soldering spec.:

[mm]


max. 7,0
 typ. 2,9
 typ. 12,8

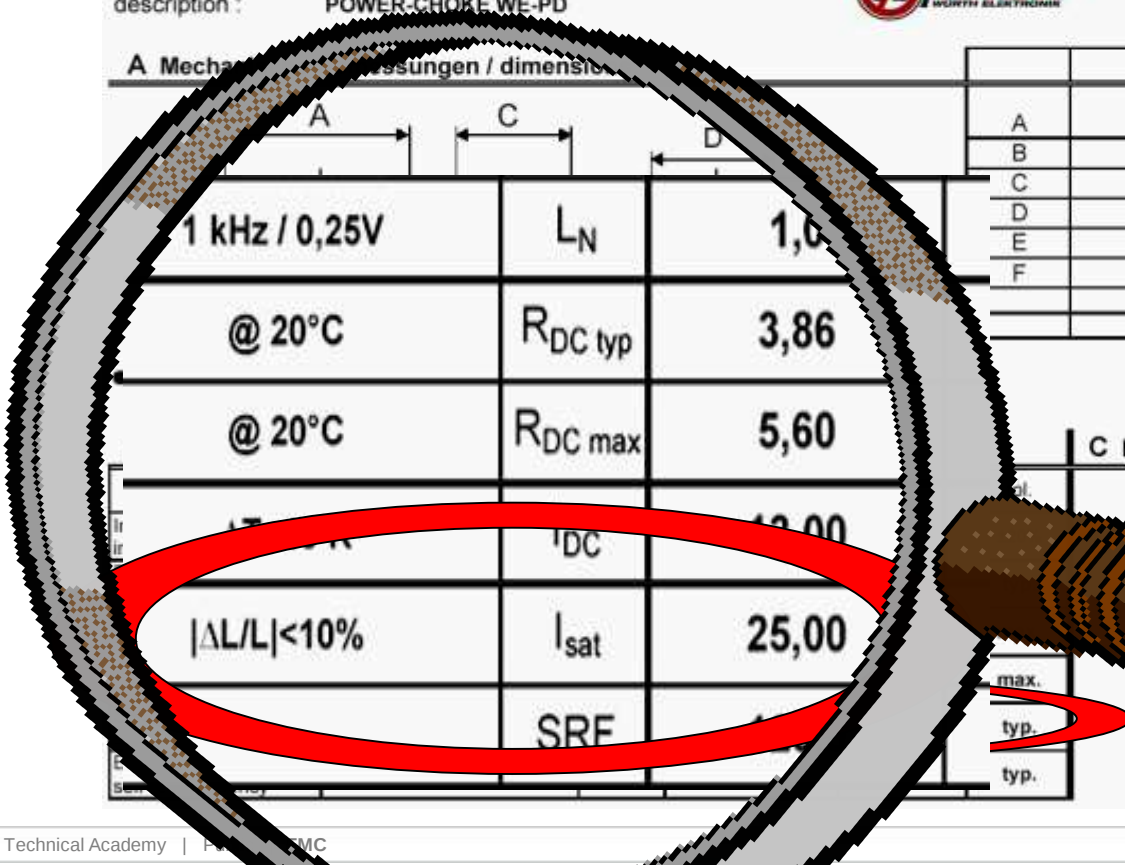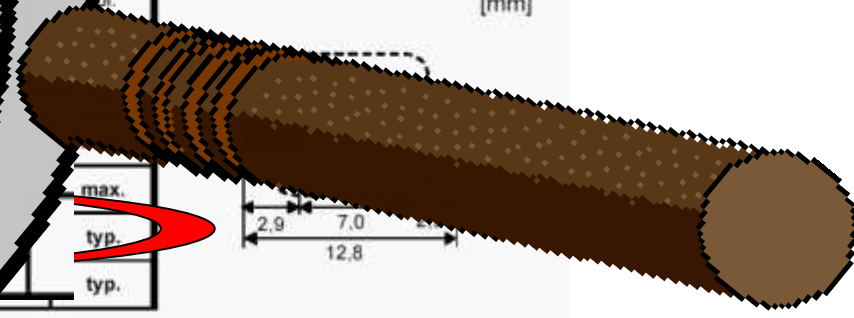Inductor Selection Parameters

■ Saturation Current

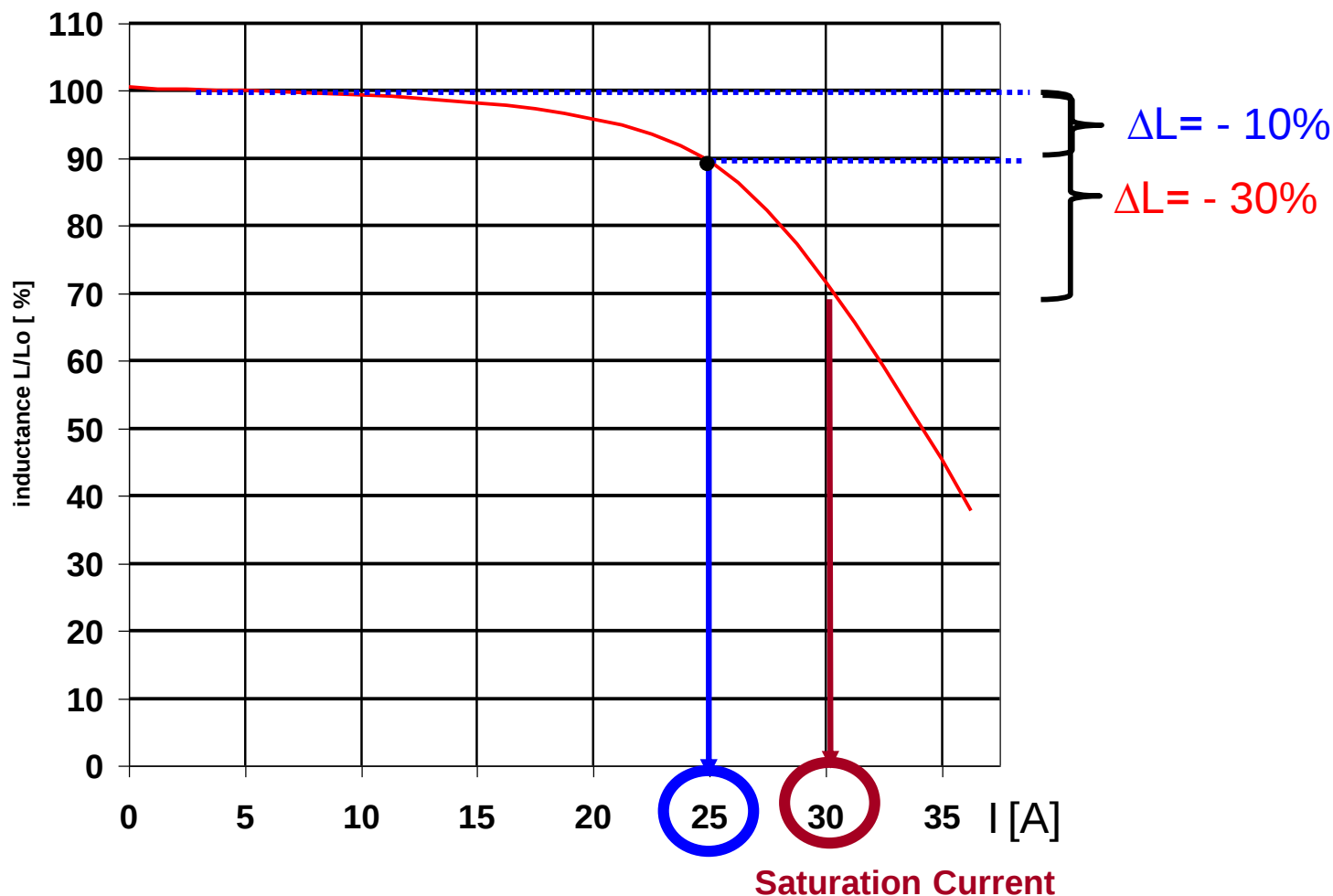Definition
 Würth Elektronik:
 e.g. WE-PD




$I_{sat} = 25$ A

$I_{sat} = 30$ A


- the saturation current always refers to a certain inductance drop

Inductor Selection Parameters

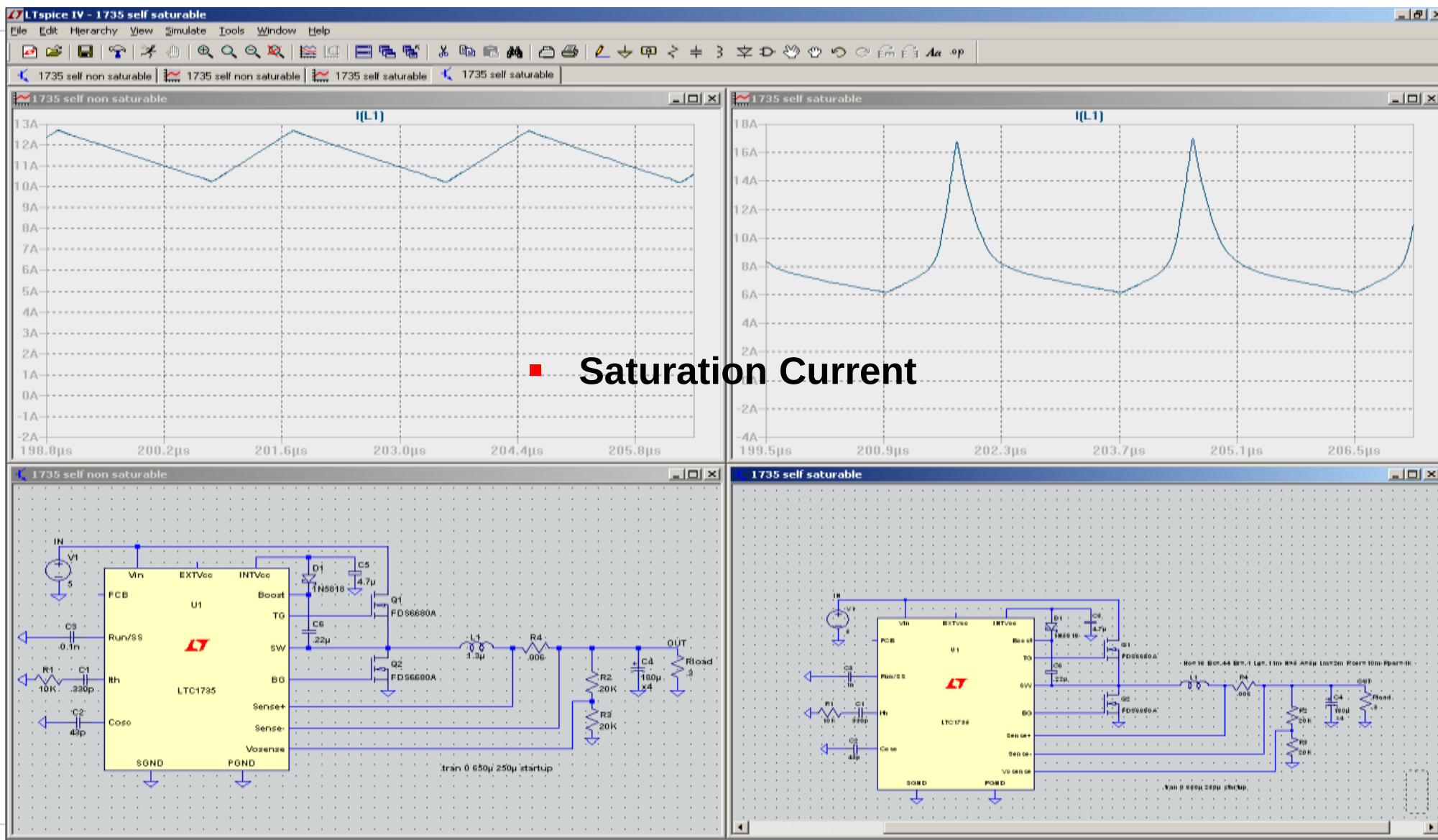

Inductor Selection Parameters

■ Saturation Current vs material

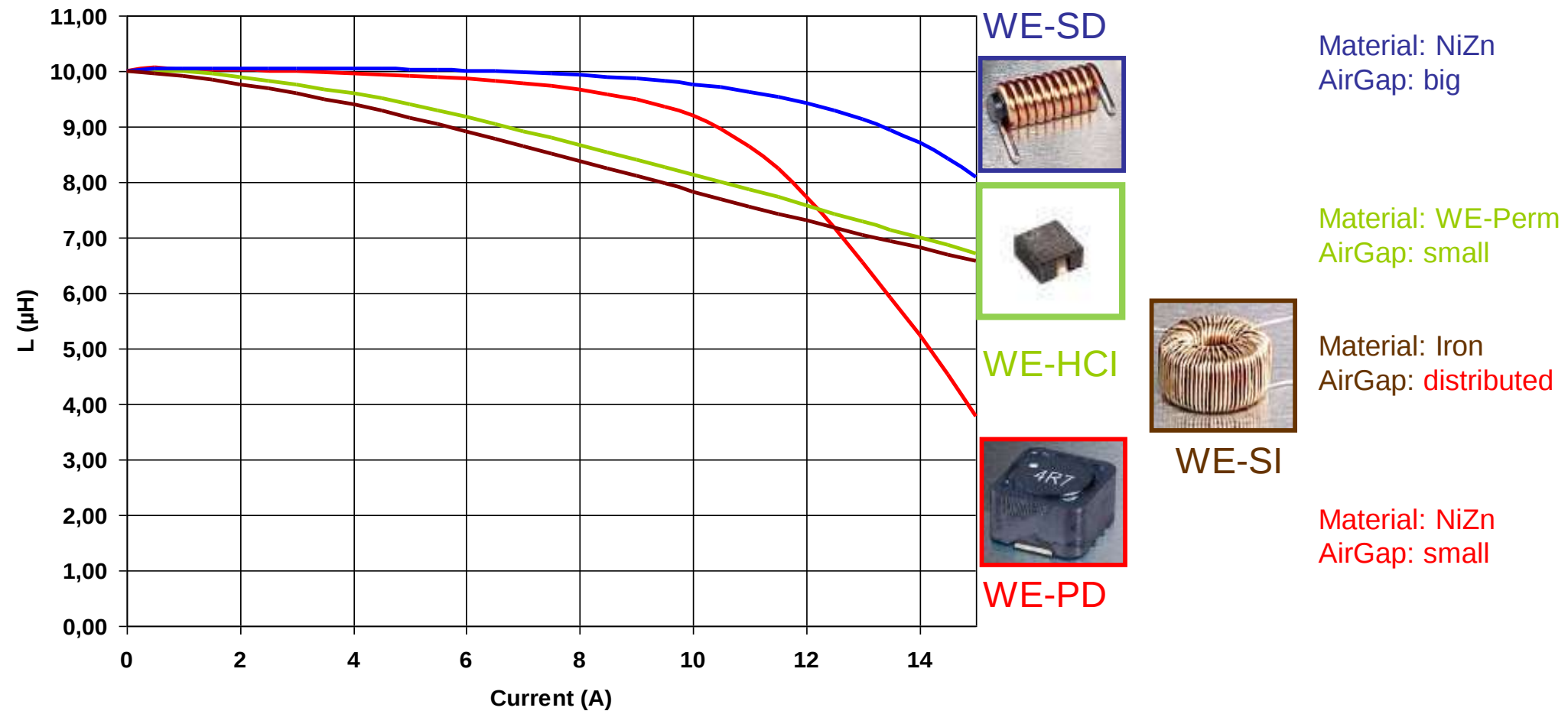

Inductor Selection Parameters

■ Rated Current

=> **Increase temperature with a DC current**

[Demo](#)


Spezifikation für Freigabe / specification for release

Kunde / customer : _____
 Artikelnummer / part number : **7447709001/LF**
 Bezeichnung : **SPEICHERDROSSEL WE-PD**
 description : **POWER-CHOKE WE-PD**

WE
WÜRTH ELEKTRONIK

DATUM / DATE : 2004-06-03

A Mechanische Abmessungen / dimensions:

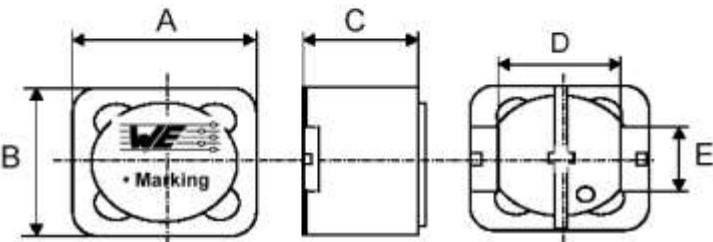

Typ XXL		
A	12,0 ± 0,5	mm
B	12,0 ± 0,5	mm
C	10,0 max.	mm
D	7,6 ref	mm
E	5,0 ref	mm
F		mm


● = Start of winding Marking = Inductance code

DC-Widerstand / DC-resistance	@ 20°C	R _{DC} max	5,60	mΩ
Nennstrom / rated current	ΔT=40 K	I _{DC}	13,00	A
Sättigungsstrom / saturation current	I _{sat} @ I _{DC} 400%	I _{sat}	25,00	A

Inductor Selection Parameters

■ Rated Current – De-rating

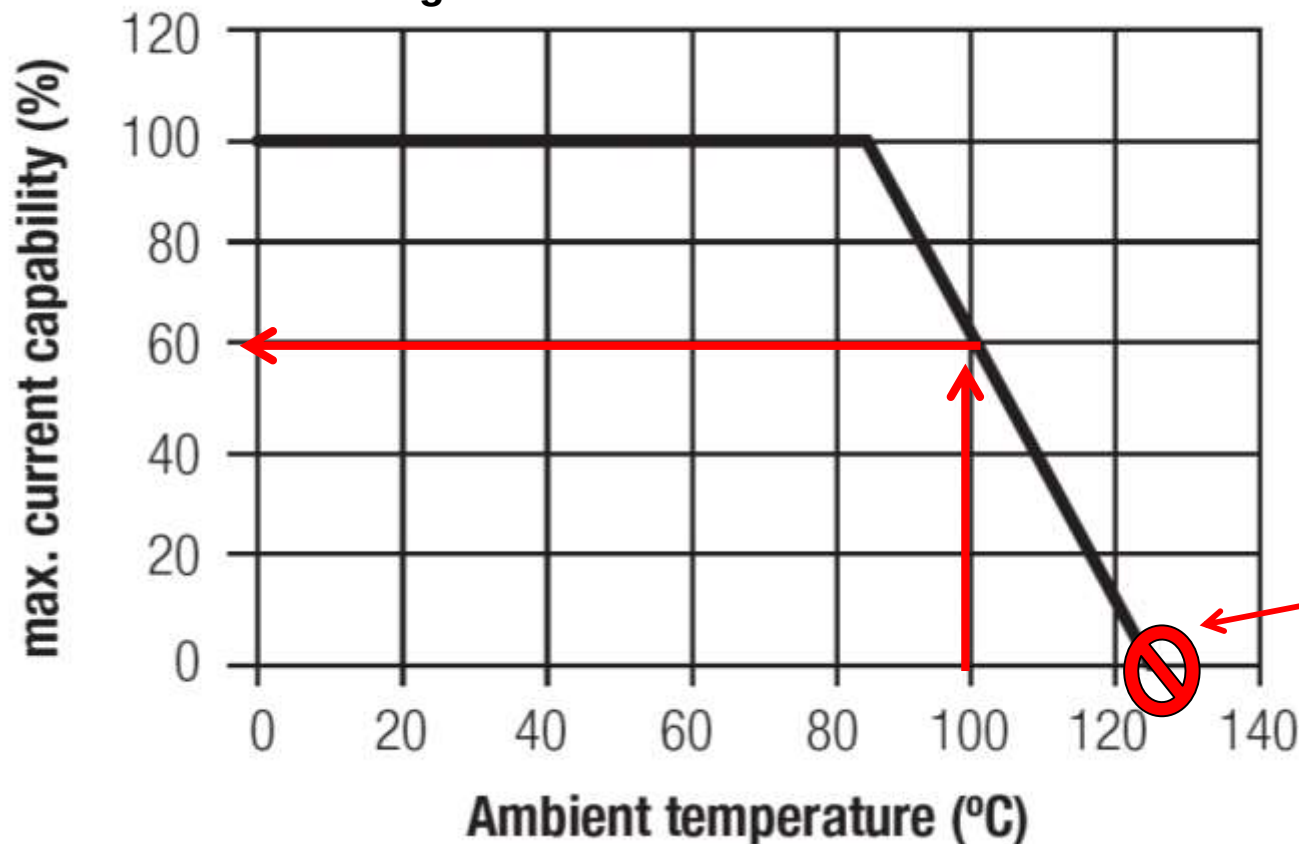At 100°C ambient Temp. only 60% of the rated current can be used
Derating of 40 %




The max operating temperature of the inductor is 125°C

Can be higher 155°C, like PDF series

Capacitor Selection Parameters



■ Capacitor Categories:

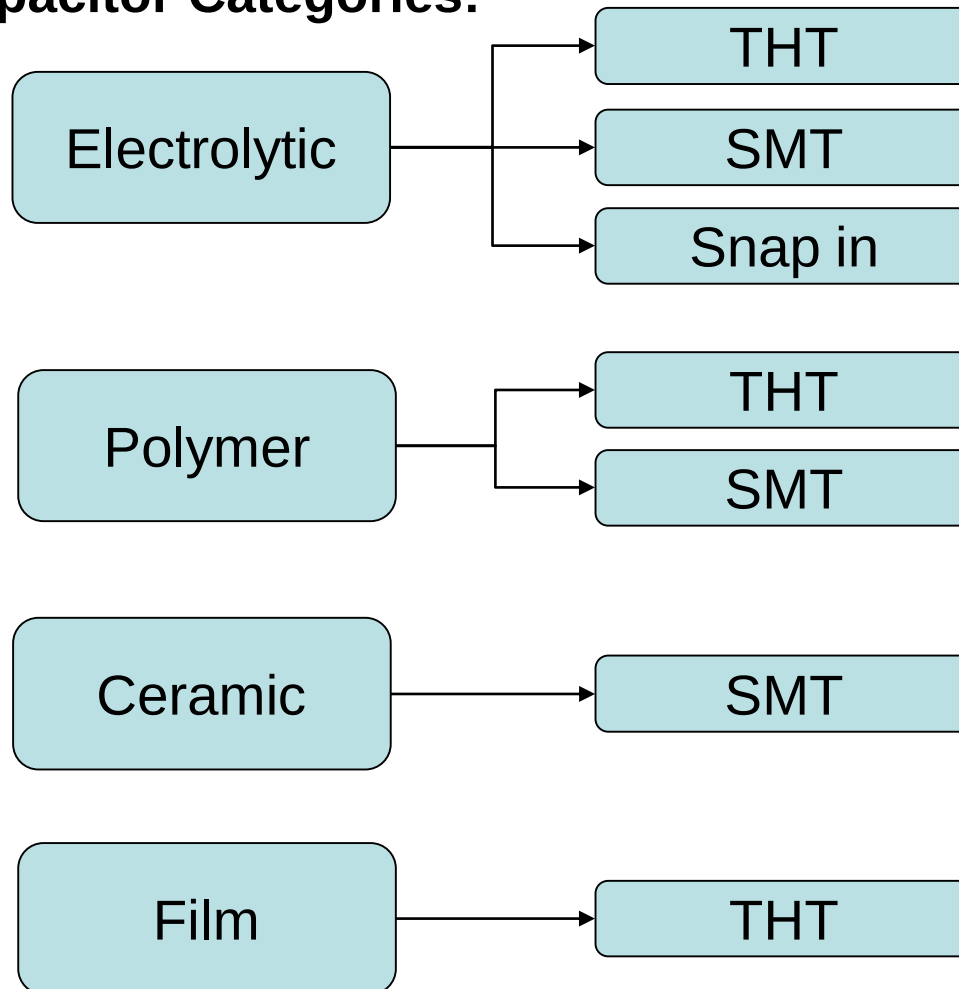

Electrolytic &
Polymer




MLCC & FILM

Capacitor Selection Parameters

- **Capacitor Catalogue Parameters:**
 - Voltage Rating
 - Ripple Current (rms)
 - Leakage current
 - Dissipation Factor
 - Expected Life
 - MLCC Capacitance vs Temperature Curve
 - MLCC Capacitance vs Voltage Curve
 - MLCC Capacitance vs time Curve
 - MLCC Class 1 and 2



Expected Life

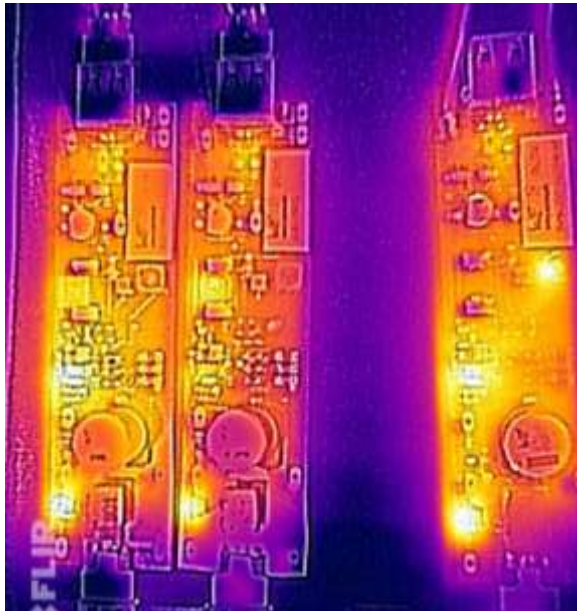

EFFICIENCY & LOSSES

Efficiency - Importance

- Advantages
 - „green design“
 - sustainable products
 - less cooling efforts
 - cost savings
 - high power density
 - size shrinks


A small efficiency increase

greatly reduce losses !!

No Fan – No bulky heat sink

INDUCTOR LOSSES

T1 = 58°C T2 = 69°C T3 = 50°C

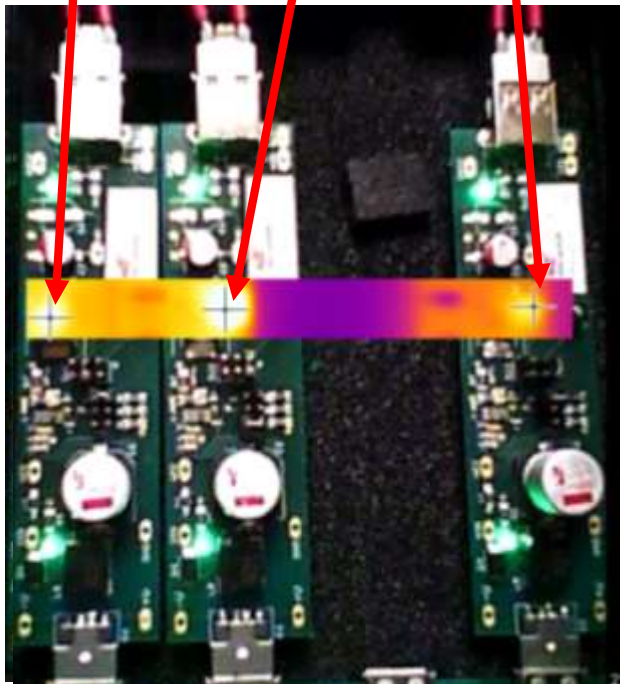

Self Heating of the inductor
can be estimate

INDUCTOR LOSSES

$$P_{total} = P_{core} + P_{copper}$$

Core losses:

Hysteresis losses

Eddy current losses


Copper losses:

DC losses – depending on DCR

AC losses – dep. on winding structure

→ Skin-Effect

→ Proximity-Effect

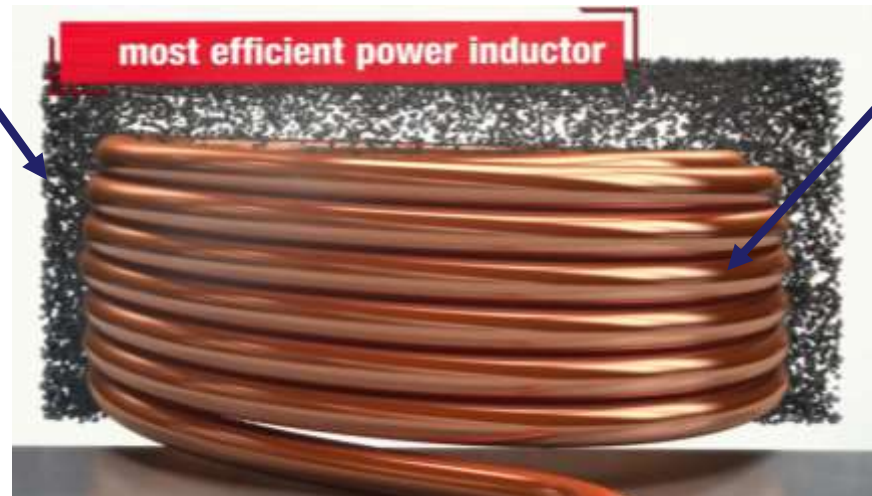


INDUCTOR LOSSES : Copper DC losses



$$P_{cu} = R_{DC} * I_{RMS}^2$$

$$R_{DC} = \rho * \frac{l}{A}$$

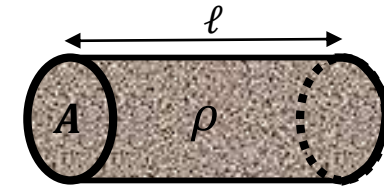


$$\rho = 1,78 * 10^{-2} \frac{\Omega \cdot mm^2}{m}$$

$$R_{DC} \downarrow \Rightarrow P_{cu} \downarrow$$




- ρ : Resistivity of copper
- l : Length of wire
- A : Cross Sectional area

Optimization

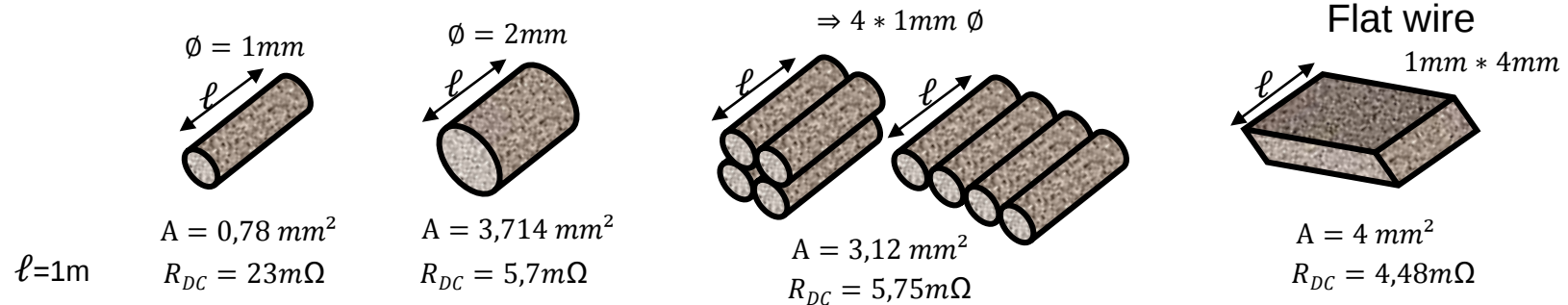


INDUCTOR LOSSES : Copper AC losses

Eddy Currents in Wire

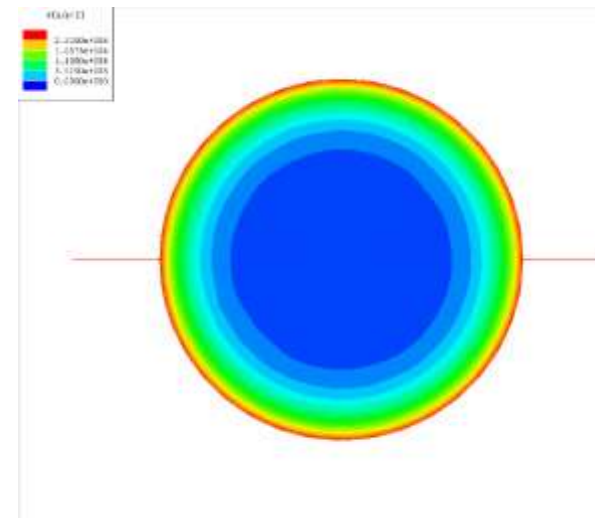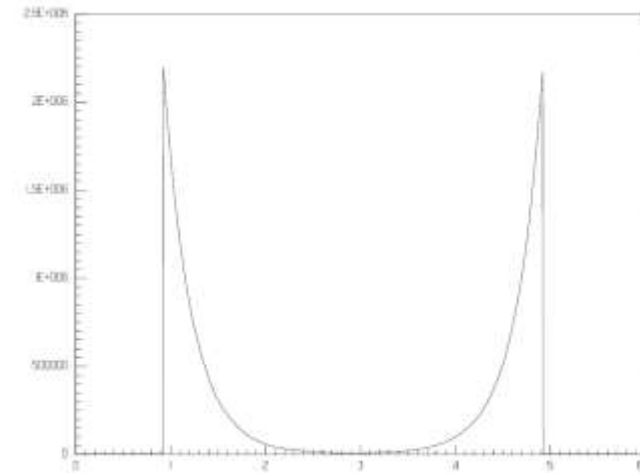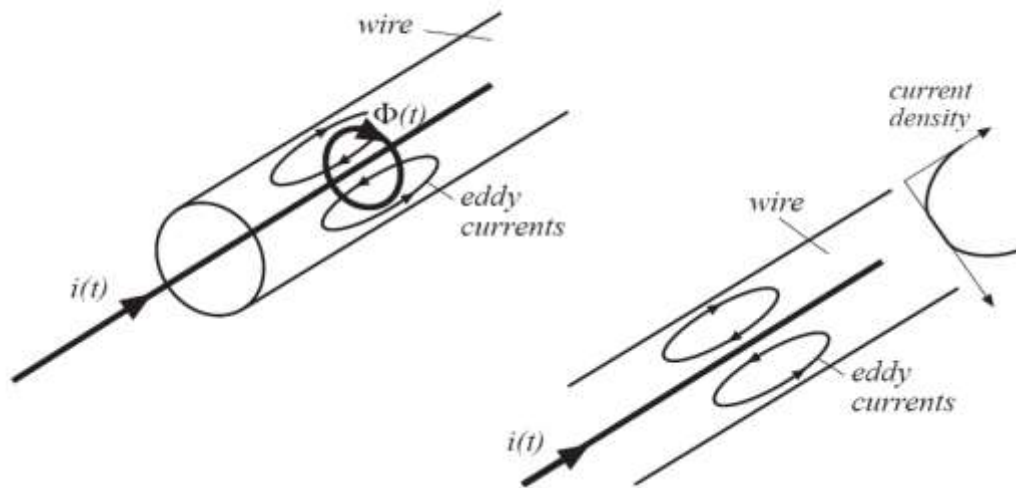

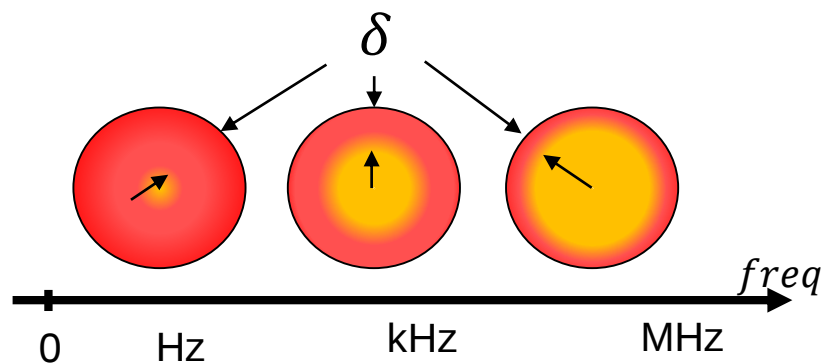INDUCTOR LOSSES : Copper AC losses, Skin effect



$$\delta = \sqrt{\frac{2 * \rho}{\omega * \mu}} \text{ mm}$$

δ = skin depth

ρ = resistivity

ω = angular frequency $2\pi f$

μ = permeability


$$\delta = \frac{76}{\sqrt{f}} \text{ mm} @ 100^\circ\text{C}$$

For Copper


$\delta @ 50\text{Hz} = 9.38 \text{ mm}$

$\delta @ 10\text{kHz} = 0.66 \text{ mm}$

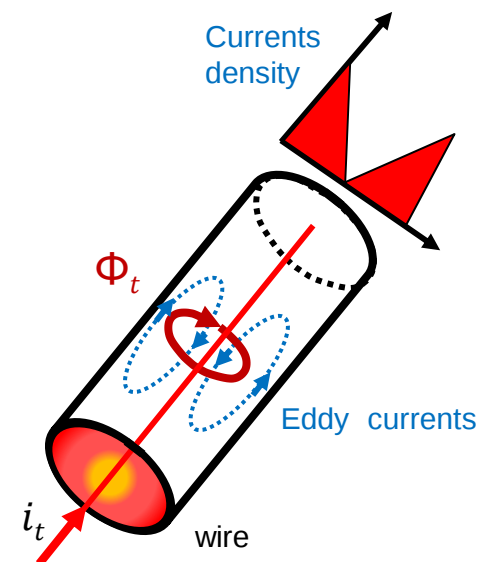$\delta @ 100\text{kHz} = 0.22 \text{ mm}$



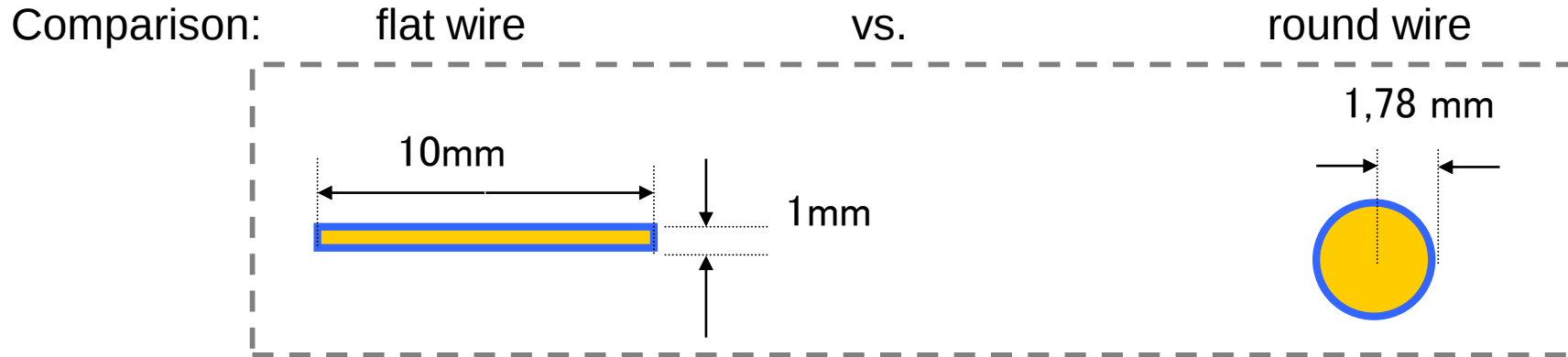INDUCTOR LOSSES : Copper AC losses, Skin effect



cross section of both wires is 10mm^2

BUT: flatwire has much more bigger surface

Flat wire surface : 22mm / round wire 11,18mm

$$S_{\text{FLAT}} = 1,96 \times S_{\text{RUND}}$$

AND: high frequency currents only use the surface


→ Skin effect



Flat wire has a higher surface,
thus less copper losses at higher frequencies !



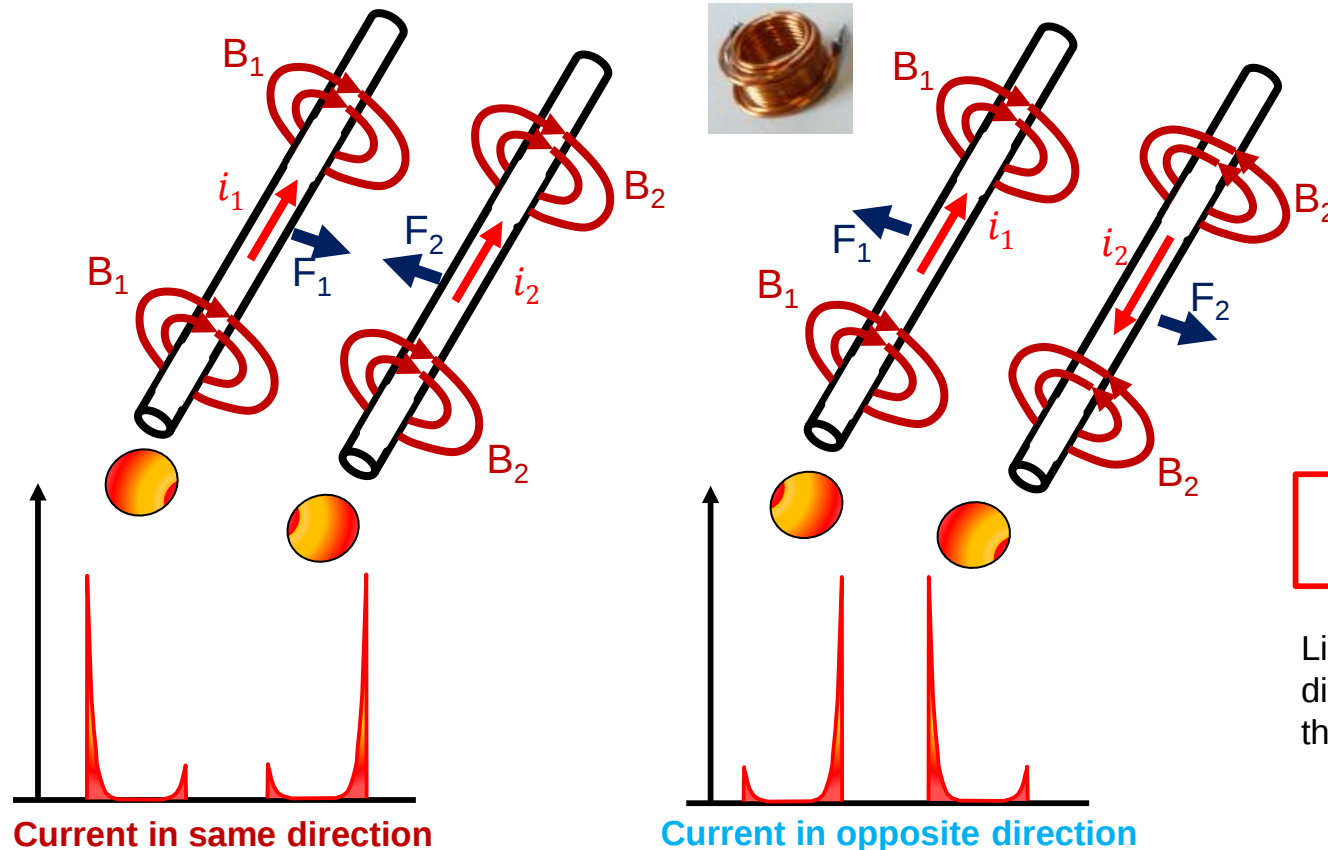INDUCTOR LOSSES : Copper AC losses, Proximity effect



$$f \uparrow \Rightarrow R_{AC} \uparrow$$

Like the skin effect, the distribution of current inside the wire is reduced



- Proximity Effect creates more loss than Skin Effect
- Approximate Calculations
 - Dowell's curves for simple geometries
 - Bruce Carsten or Charles Sullivan for more in-depth

INDUCTOR LOSSES : Core losses


- Steinmetz formula

$$P_{core} = K \cdot f^a \cdot B^b$$

Error factor

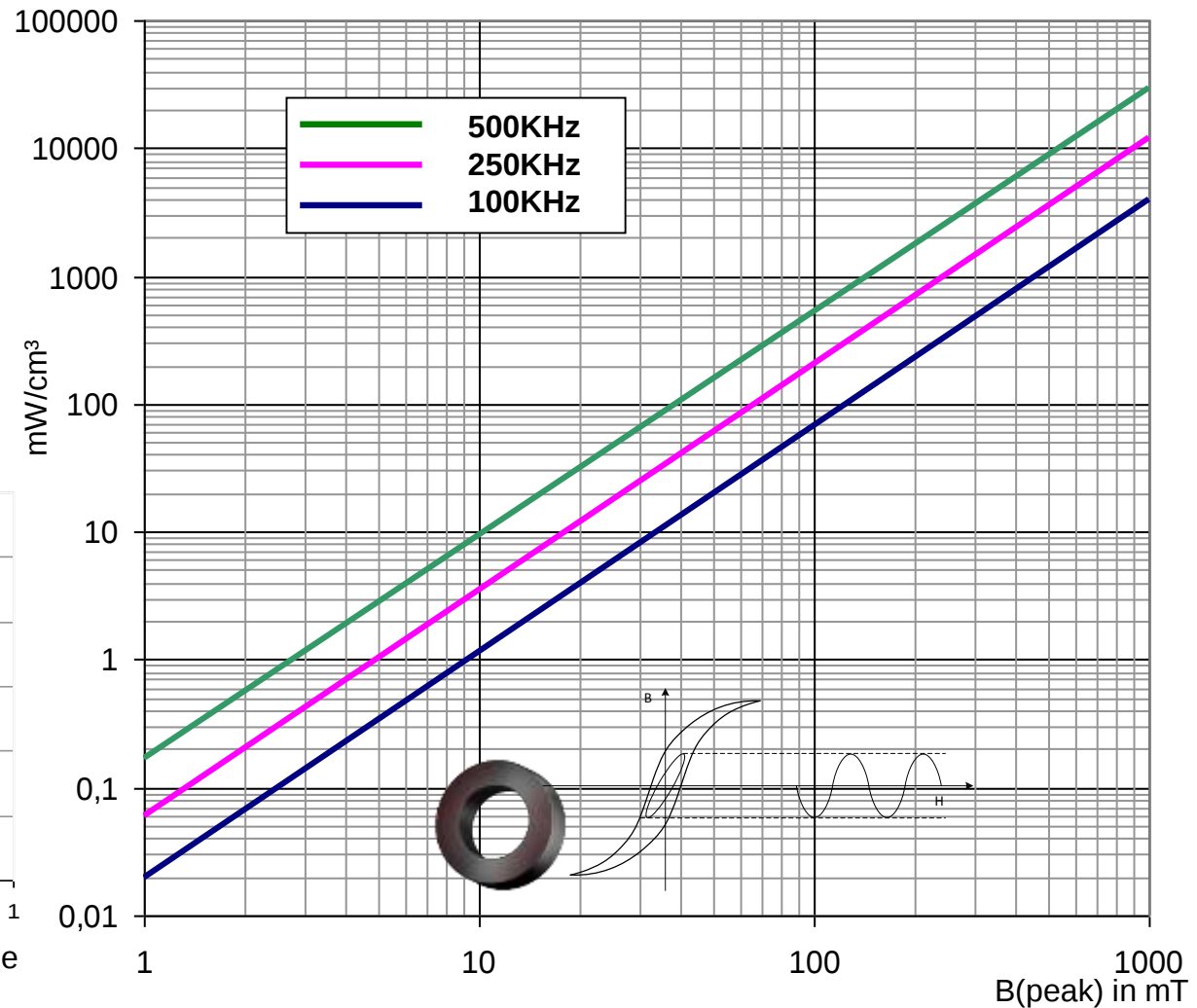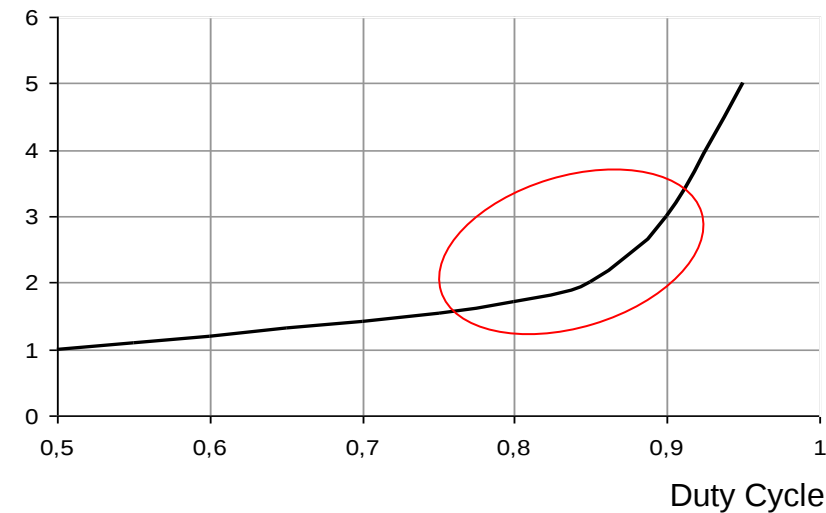

REDEXPERT – The missing link

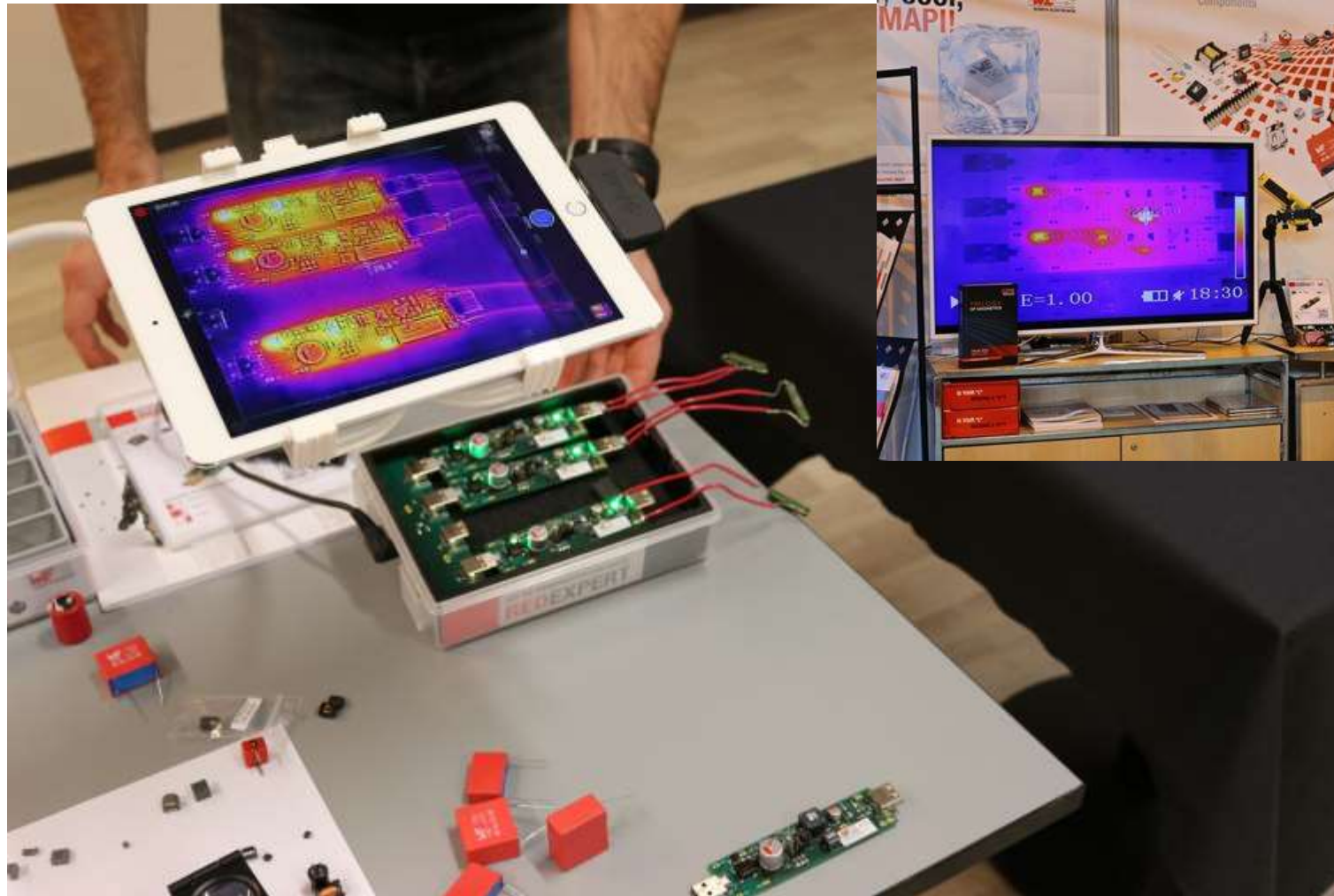



REDEXPERT

REDEXPERT



Power Inductors

REDEXPERT

World's most accurate AC loss model

The losses determined with REDEXPERT are based on real time DCDC measurements with its typical current and voltage waveforms. Besides all core and winding losses they do also consider losses in the air gap.

▶ Calculate the AC losses



User Interface



Würth Elektronik Group

Sign in

English ▾

more than you expect

SELECTION TABLE

Power Inductors **REDEXPERT®** ▾

100 / 2082 items

✓	Series	Order Code	Spec	Type	L	R _{DC,typ}	I _R	I _{sat}	Size	Length	Width	Height
✓	WE-MAPI	744383130068	PDF	Single	680 nH	101 mΩ	1.55 A	3.80 A	1610	1.6 mm	1.6 mm	0.90
✓	WE-MAPI	744383130082	PDF	Single	820 nH	115 mΩ	1.45 A	3.60 A	1610	1.6 mm	1.6 mm	0.90
✓	WE-MAPI	74438313010	PDF	Single	1.00 µH	127 mΩ	1.40 A	3.40 A	1610	1.6 mm	1.6 mm	0.90
✓	WE-MAPI	74438313012	PDF	Single	1.20 µH	140 mΩ	1.30 A	3.20 A	1610	1.6 mm	1.6 mm	0.90

Design Tools

STORAGE

744383130068

WE-MAPI · 1610
680 nH · 101 mΩ
1.55 A · 3.80 A

Drop Order Codes



in the bar to add

Drag out buttons
to delete them

Share



Free Samples

Tidy Up

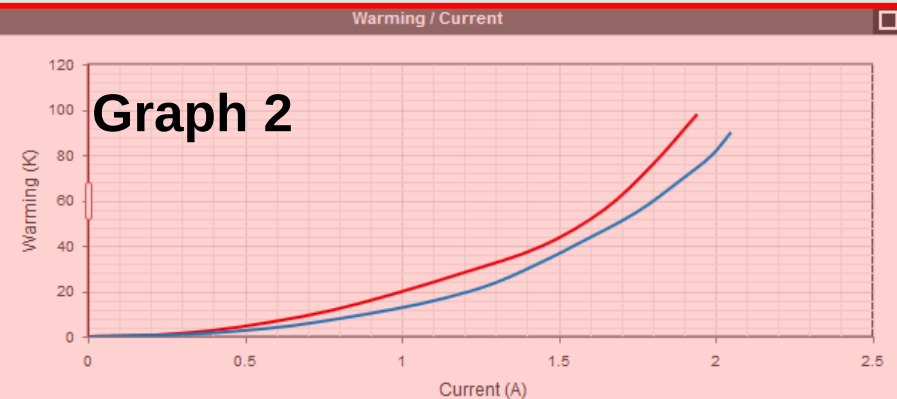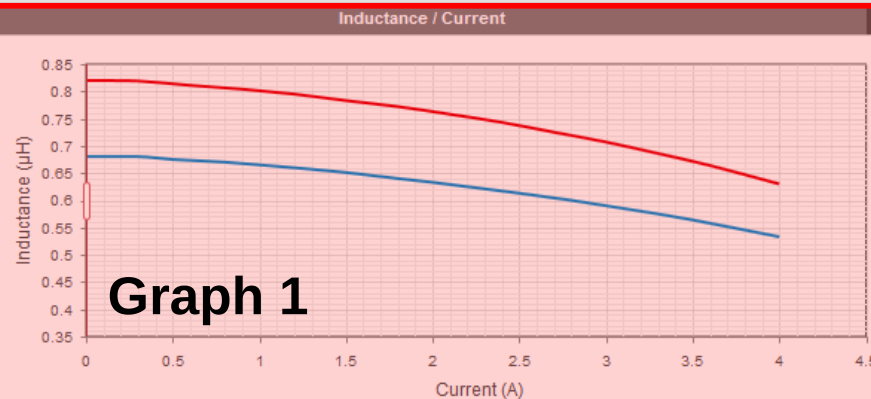


World's Most Accurate AC Loss Model

Würth AC Loss Model

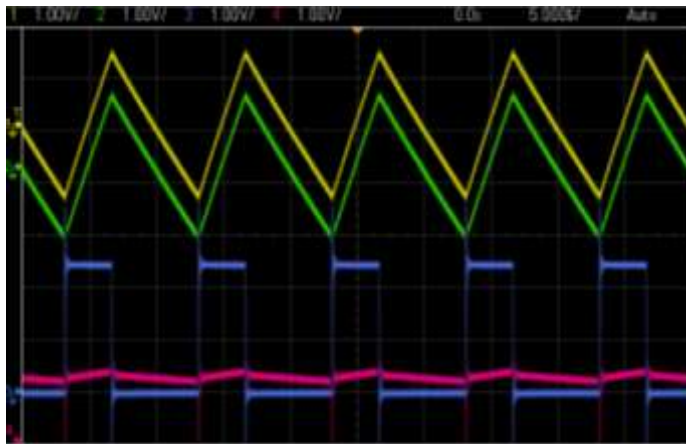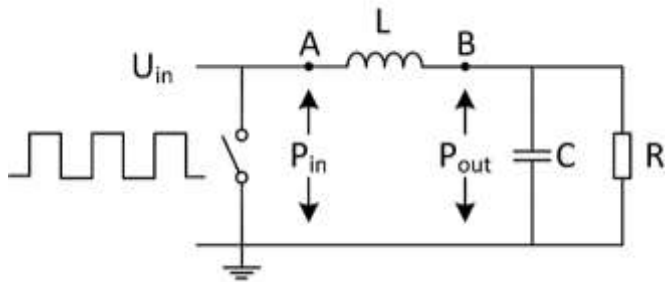

Simple Class-D Amplifier

Steinmetz Models

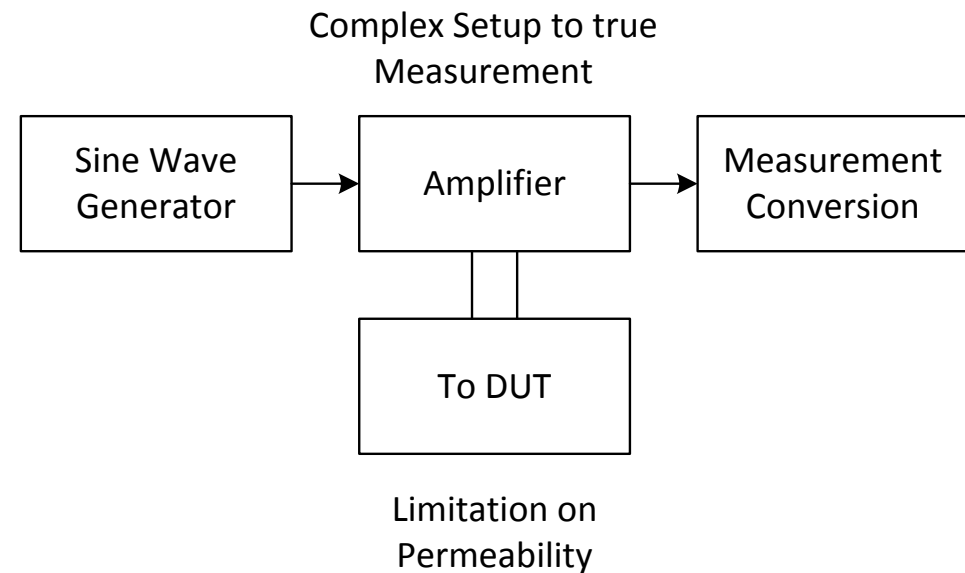

Complex Setup to Measure

World's Most Accurate AC Loss Model

Würth AC Loss Model:

- Based on real time application set up and measurements
- A pulsating input voltage is applied over the Inductor
- The input and output power is measured
- This process is repeated over wide range of parameters incl. variation of peak flux density swing to produce our own empirical data
- This empirical data is used to create the equation for Würth AC Loss Model

Advantages:


- Accurate calculation of losses for any given Duty Cycle
- Accurate over wide range of frequency (10 kHz to 10 MHz)
- Considers even small change in core material and winding structure

World's Most Accurate AC Loss Model

Würth AC Loss Model

$$P_{AC} = f (\Delta I, \text{freq}, DC, k1, k2)$$

➡ Core Loss & AC Wire Loss

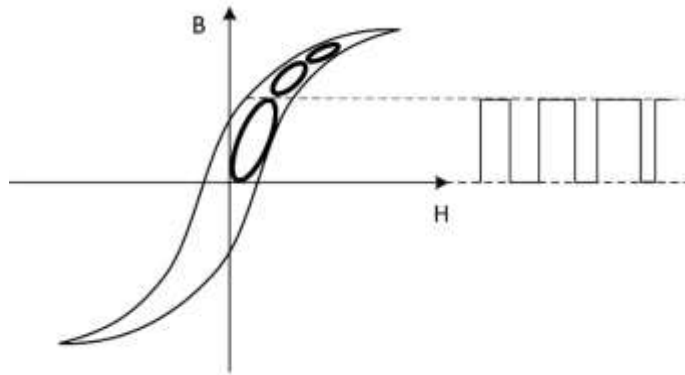

➡ Point of Operation Approach
triangular current form


Steinmetz Models

$$P_V = K \cdot f^\alpha \cdot \Delta B^\beta$$

$$P_V = K \cdot f^{\alpha-1} \cdot \Delta B^\beta \times f^r$$

$$P_V = K \cdot f_{eq}^\alpha \cdot \Delta B^\beta$$


➡ Core Loss Only

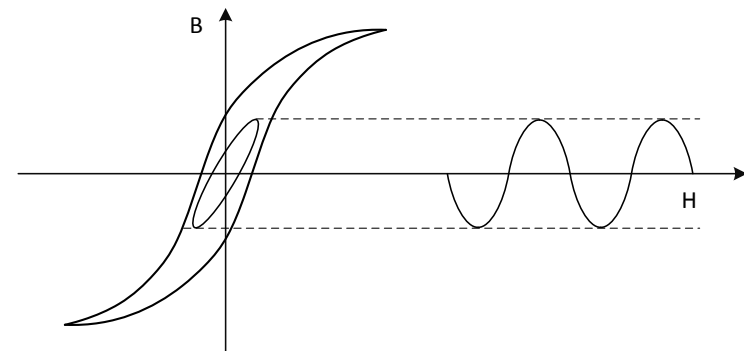

➡ Major Loop Approach
only sine wave


World's Most Accurate AC Loss Model

Würth AC Loss Model

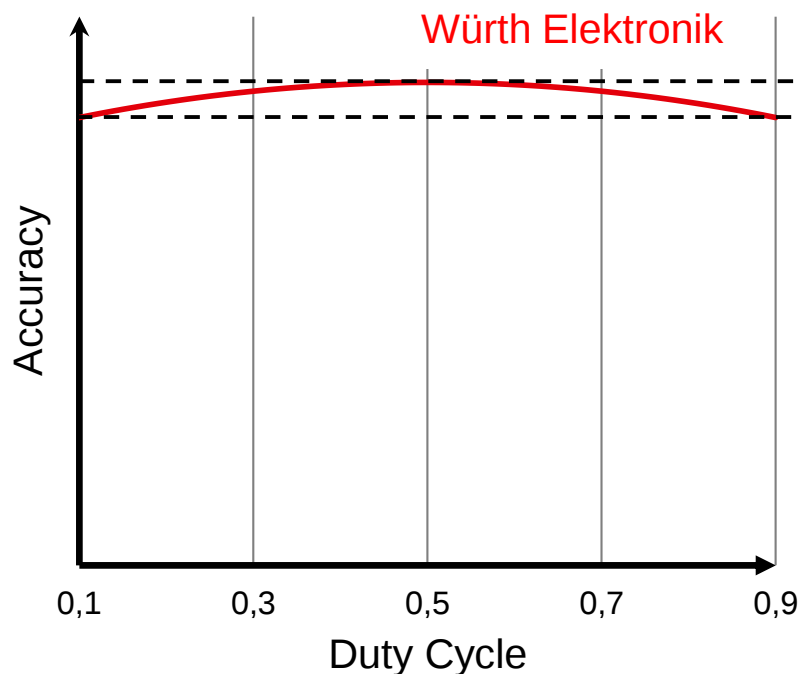

**Highest Accuracy
over wide DC range**

Steinmetz Models

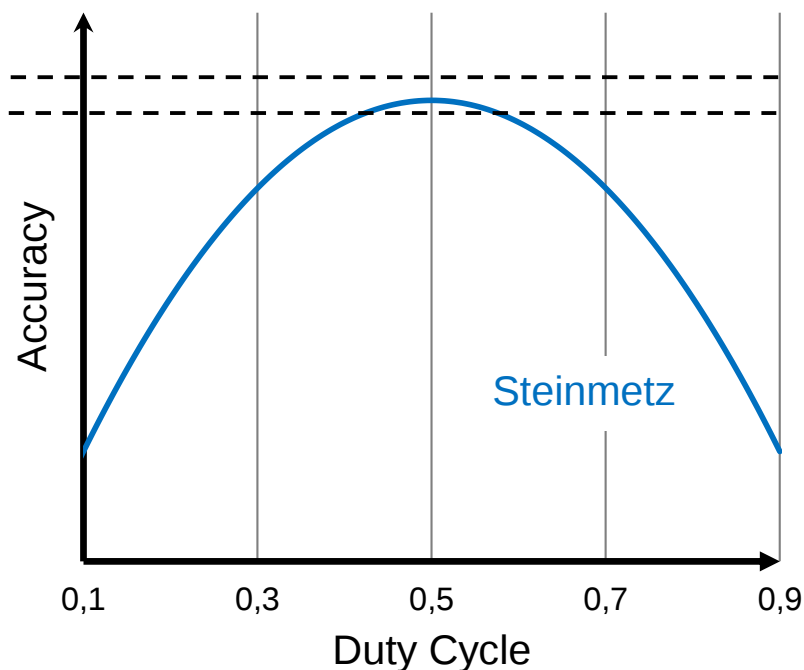

**Acceptable Accuracy at 50%,
even worse for other DC**

REDEXPERT

<https://www.we-online.com/redexpert/#/module/1>

www.we-online.com/redexpert

- <http://we-online.com/re/3bJFP7JE>

Buck Demo Kit for REDEXPERT



A photograph of the Buck Demonstration Kit for RED EXPERT. It is a green printed circuit board (PCB) populated with various electronic components including a large electrolytic capacitor, several smaller capacitors, resistors, and integrated circuits. A USB-A connector is visible on one end, and a green multi-pin connector is on the other. The Würth Elektronik logo is printed on the board.

Buck Demonstration Kit for **RED**EXPERT


TECHNICAL DATA:

f_{sw}	200 kHz ~ 2 MHz
V_{in}	4.5 V ~ 40 V
V_{out}	5 V
I_{out}	2 A / 3 A peak

Order Code 988 141
Version 1.0

Buck Demo Kit for REDEXPERT

Test Conditions

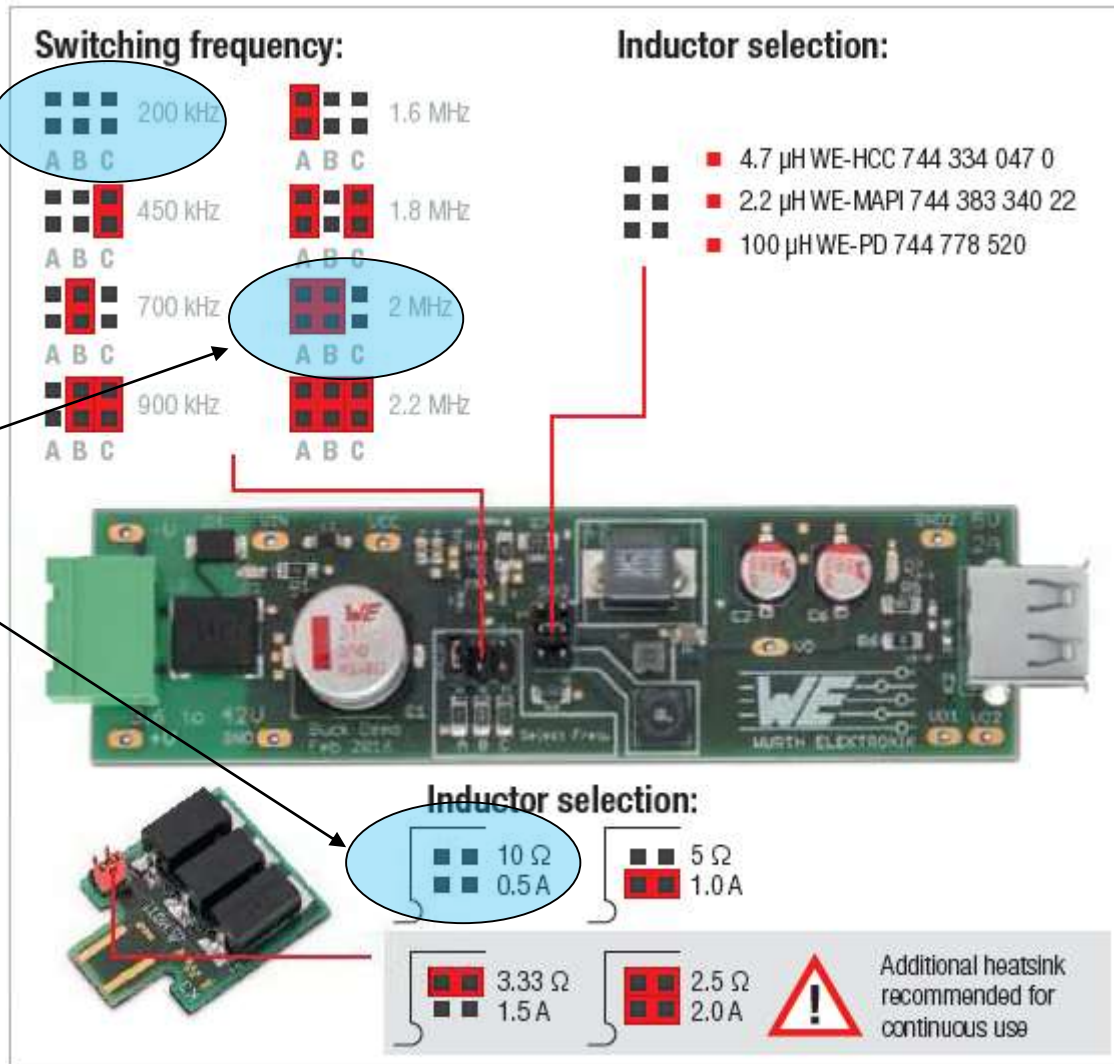


Switching Frequency: 200KHz vs 2MHz


Ambient
SAT
22.9°C



9Vin,
5Vo,
2.5W,
200KHz

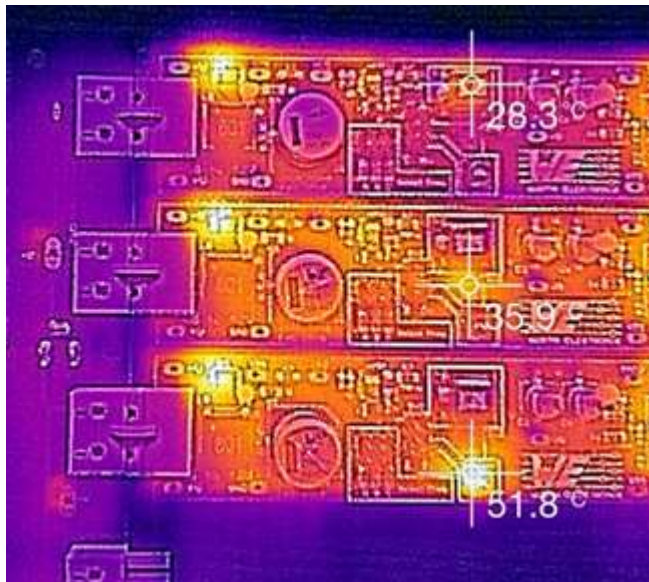

9Vin,
5Vo,
2.5W,
2MHz

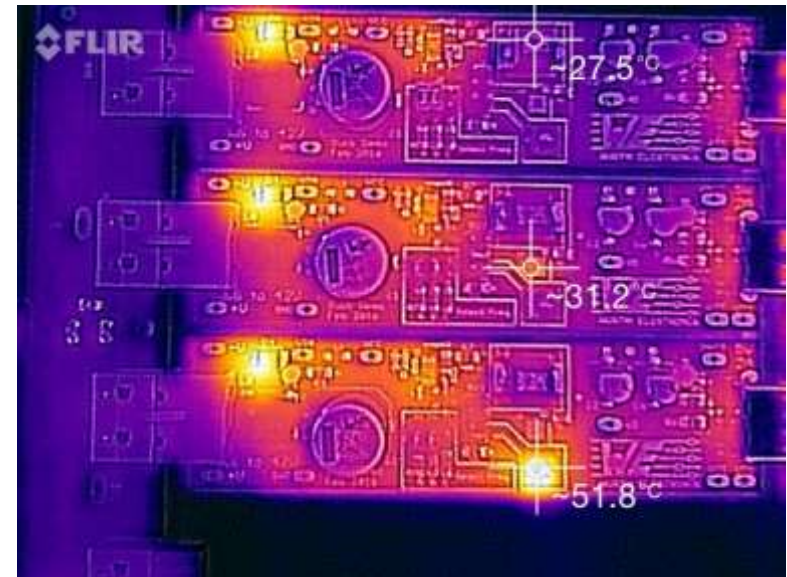

REDEXPERT



- <http://we-online.com/re/3bJFP7JE>

Filters: Order Code $\ni$ 7443340470, 74438334022, 744778520 $\times$ Type = Single $\times$														
	Order Code	Series	Size	Spec	Type	L	L() @39...	R _{DC,typ}	I _R	I _{sat}	P _{AC}	P _{DC}	P _{TOT}	ΔT
✓	7443340470	WE-HCC	8070		Single	4.70 μ H	4.60 μ H	12.7 m Ω	7.50 A	8.00 A	64.6 mW	3.18 mW	67.8 mW	7.15 K
✓	74438334022	WE-MAPI	3012		Single	2.20 μ H	2.20 μ H	100 m Ω	1.80 A	5.00 A	74.6 mW	25.0 mW	99.6 mW	15.1 K
✓	744778520	WE-PD	6033		Single	100 μ H	99.0 μ H	950 m Ω	650 mA	500 mA	4.19 mW	238 mW	242 mW	26.3 K

Buck Converter $\times$				
Reapply				
PARAMETERS				EDIT
Input	Output	Switch	Inductor	Diode
8.20 V 8.00-10.0 V	4.90 V 500 mA	200 kHz	40 % Single	0.30 V
DETAILS				
I _{rms} ≥ 500 mA	I _{max} ≥ 600 mA	L _{opt} 50.5 μ H		


200KHz vs 2MHz

Buck Converter $\times$				
Reapply				
PARAMETERS				EDIT
Input	Output	Switch	Inductor	Diode
8.20 V 8.00-10.0 V	4.90 V 500 mA	2 MHz	40 % Single	0.30 V
DETAILS				
I _{rms} ≥ 500 mA	I _{max} ≥ 600 mA	L _{opt} 5.05 μ H		

Filters: Order Code $\ni$ 7443340470, 74438334022, 744778520 $\times$ Type = Single $\times$														
	Order Code	Series	Size	Spec	Type	L	L() @39...	R _{DC,typ}	I _R	I _{sat}	P _{AC}	P _{DC}	P _{TOT}	ΔT
✓	7443340470	WE-HCC	8070		Single	4.70 μ H	4.60 μ H	12.7 m Ω	7.50 A	8.00 A	17.7 mW	3.18 mW	20.9 mW	2.70 K
✓	74438334022	WE-MAPI	3012		Single	2.20 μ H	2.20 μ H	100 m Ω	1.80 A	5.00 A	20.5 mW	25.0 mW	45.5 mW	7.90 K
✓	744778520	WE-PD	6033		Single	100 μ H	99.0 μ H	950 m Ω	650 mA	500 mA	537 μ W	238 mW	239 mW	26.1 K

PRACTICAL DC TO DC CONVERTER INPUT FILTER DESIGN CONSIDERATIONS




Oscillation At Converter Input

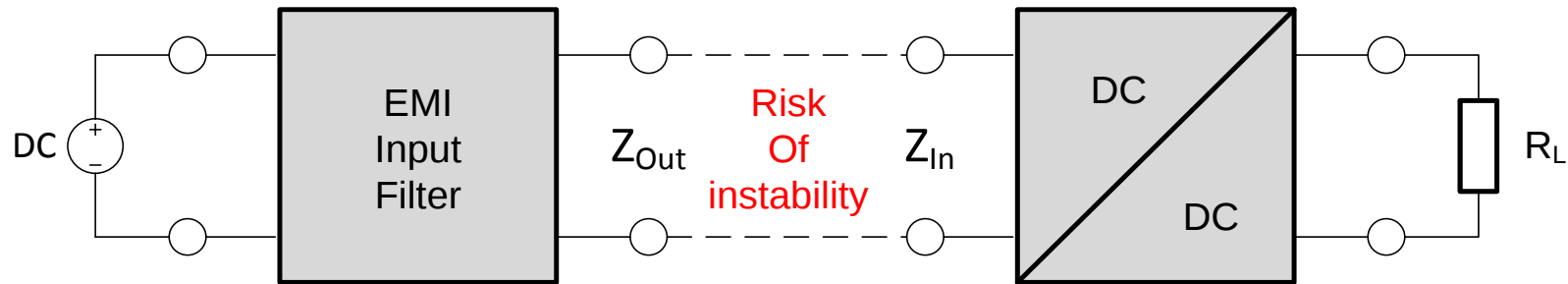

- Adding an input EMI filter to converter input can cause oscillation at converter input
- Problem could arise : the converter no longer meets response specification and may even become unstable!!! Why????

(DC) Input Impedance Of Converter (an explanation)

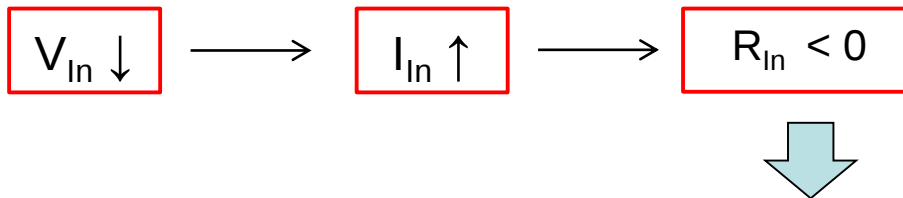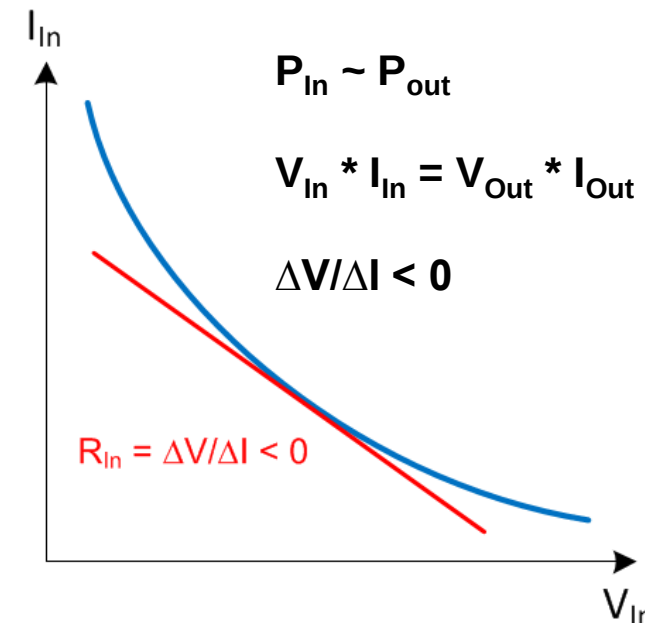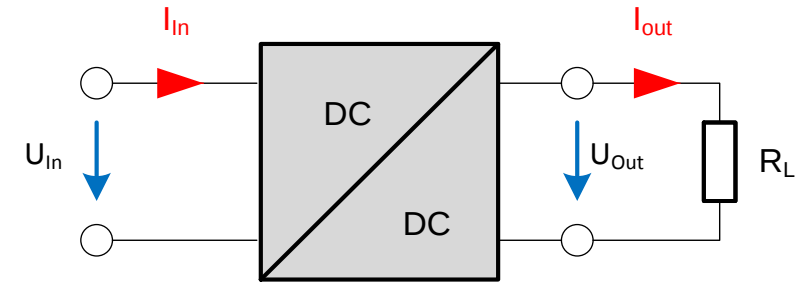
- Input and output power of converter is near the same (efficiency drop)
- Under stable conditions output power is constant
- If the input voltage falls, the input current increases
- Voltage-current line has a negative slope




NEGATIVE DC INPUT RESISTANCE

What could happen?

- Simplified model

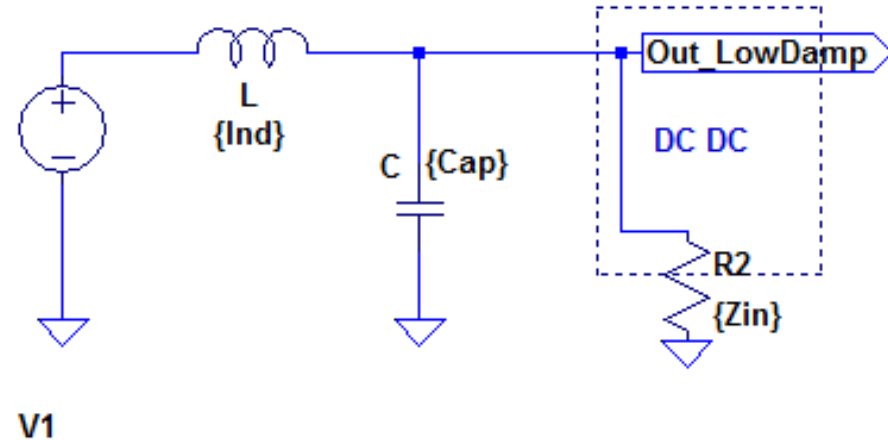

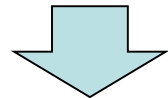- R_L : Rdc of the inductor
- ESR: serie resistance of the capacitor
- Input impedance of the buck converter (looking negative – see previous slide)





- This is a LC filter loaded by a negative resistance!!!!
- NICE WAY TO CREATE OSCILLATORS

LTspice



Damping Input Filter

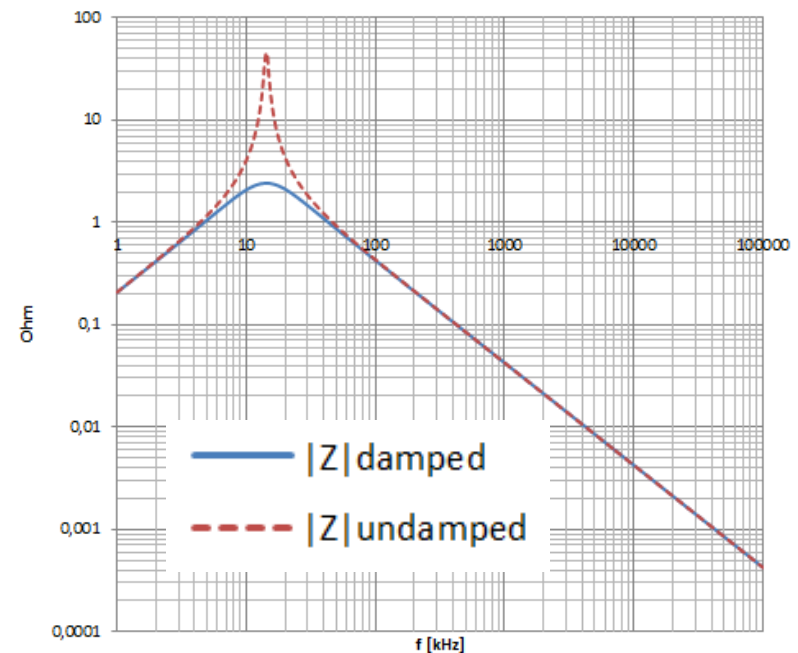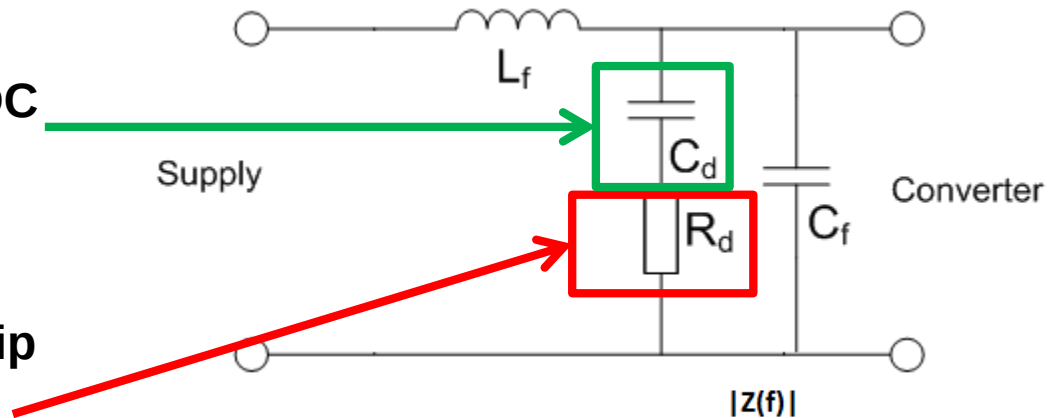- Damping capacitor C_d blocks DC current
- Damping resistor R_d reduces dip magnitude of filter at resonant frequency f_0




Calculating Input Filter Components values

Gain-Bandwidth product:

Give the right filter cutoff freq to have the attenuation required with the choosed filter topology (order)

$$f_{co} = f_{sw} \cdot 10^{\left(\frac{-A_{db}}{n \cdot 20}\right)}$$

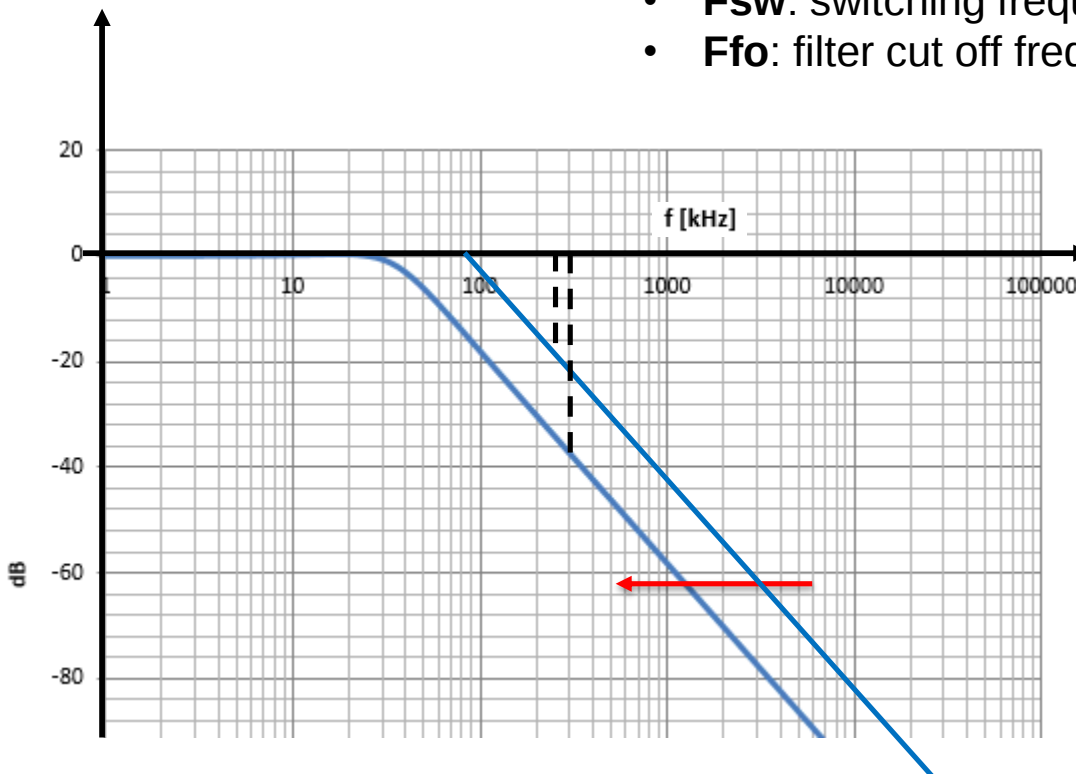- **Adb**: attenuation required
- **n**: filter order
- **Fsw**: switching frequency
- **Ffo**: filter cut off frequency



Our design:
 Adb: 32 dbuV
 2nd order filter
 Fsw: 150kHz




F_{0calc} : 23,77kHz

Calculating Input Filter Components values

Selection of the L and C value:

Different values for L and C occurs. In our design we can choose as follows:

C	2,2	uF
L	27	uH

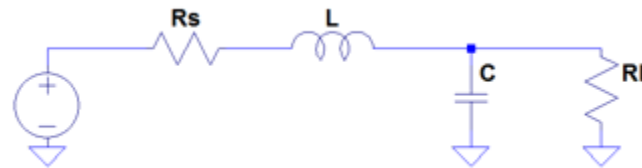


Overshoot

In order to have

$$f_0 = \frac{1}{2 \cdot \pi \cdot \sqrt{L \cdot C}} \approx 21\text{kHz}$$

(20,65kHz calculated)

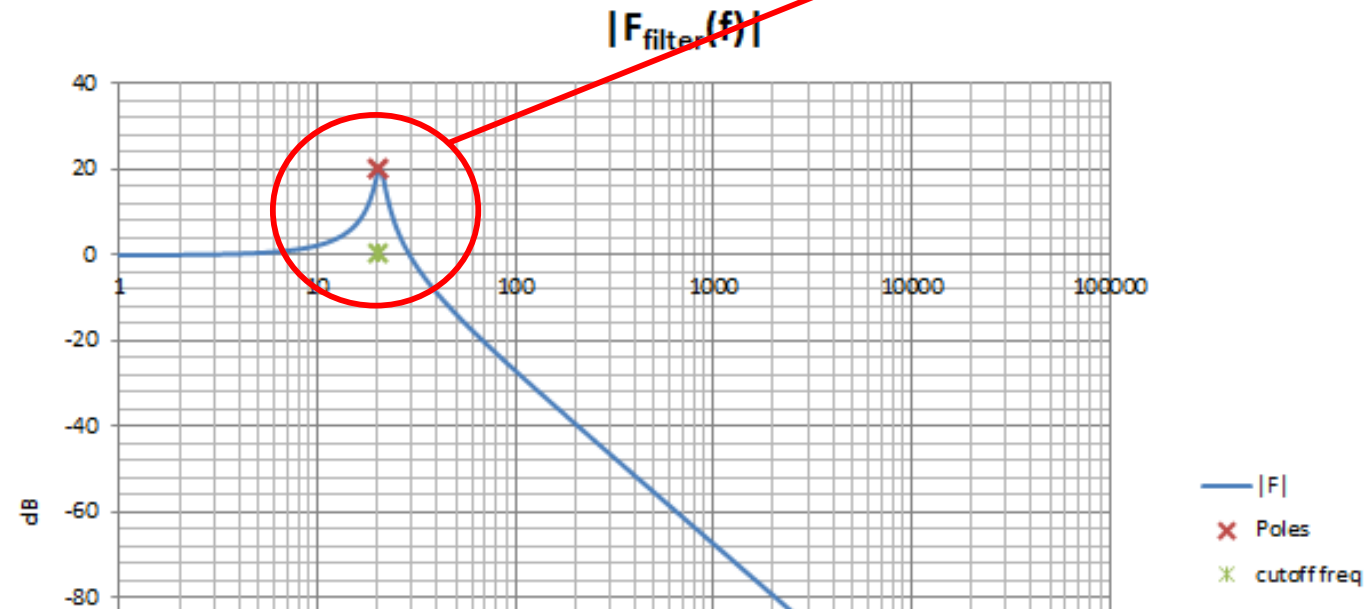

Calculating Input Filter Components values*

1) Calculate damping capacitor


$$C_d = n \cdot C_f \quad \text{with } n = 4 \text{ or } 6$$

2) Calculate damping Resistor

$$R_d = \sqrt{\frac{L_f}{C_f} \frac{(n+1)}{2n}} \sqrt{\frac{2n^2(4+n)}{(2+n)(4+3n)}}$$

Keeping the same values of undamped filter, we can add an R_d and a C_d as follows:

R_d	3,57548	Ω
C_d	8,8	μF
C	2,2	μF
L	27	μH
n	4	


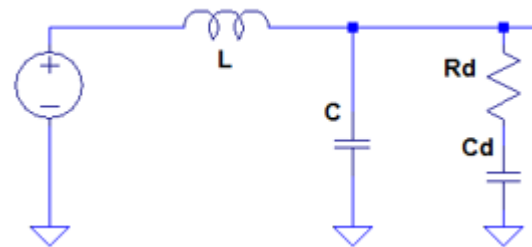


*See Input Filter Design for Switching Power Supplies, Michele Sclocchi – National App Note 2010



Calculating Input Filter Components values

 $|Z(f)|$


Damping the filter:

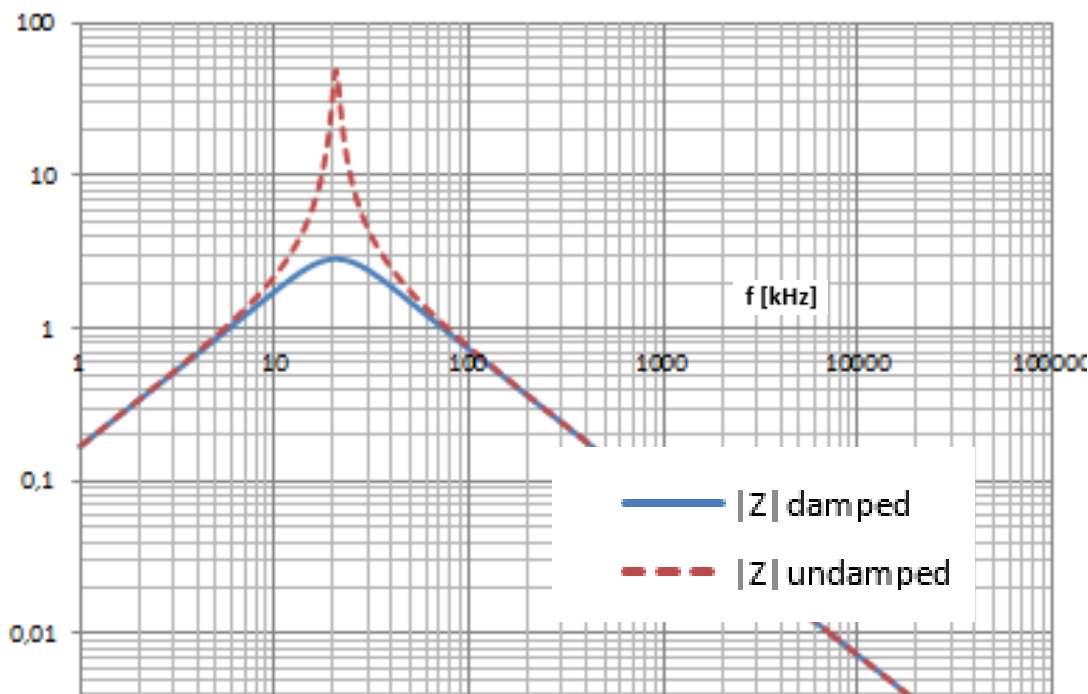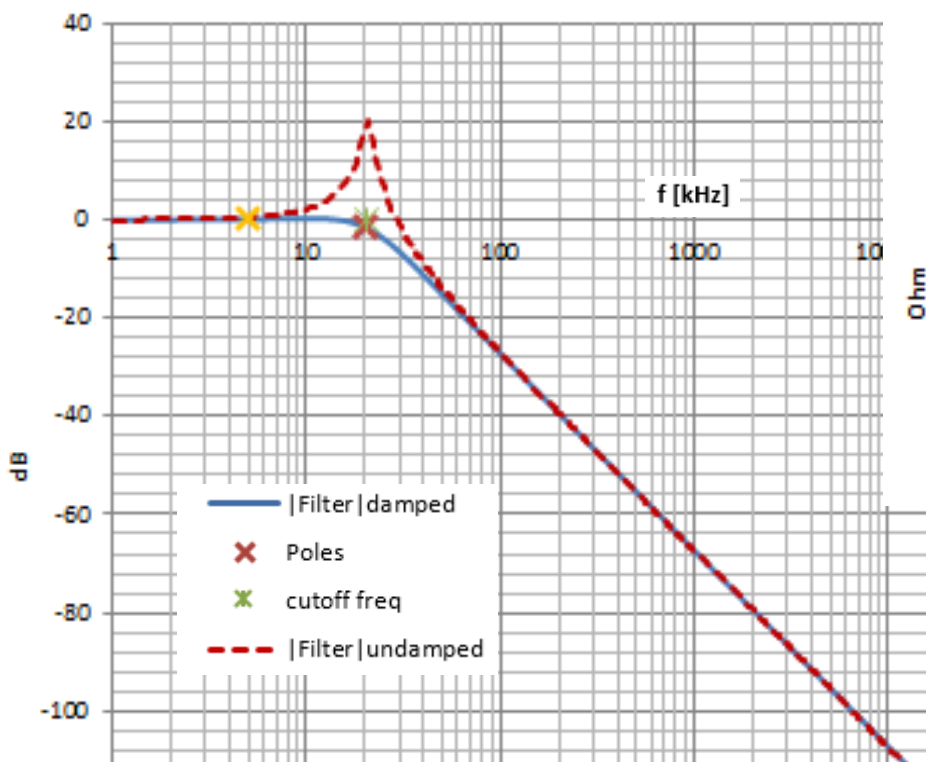 $|F_{\text{filter}}(f)|$


Check using LT Spice Simulation

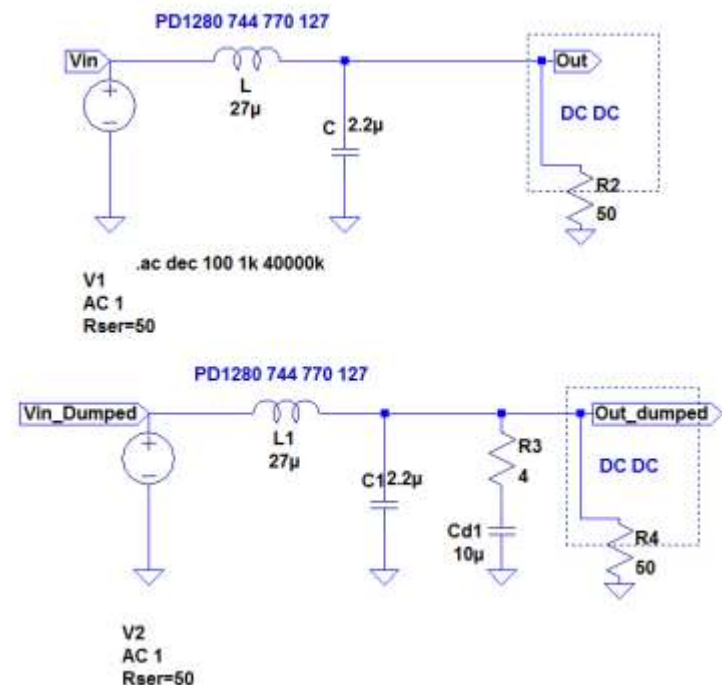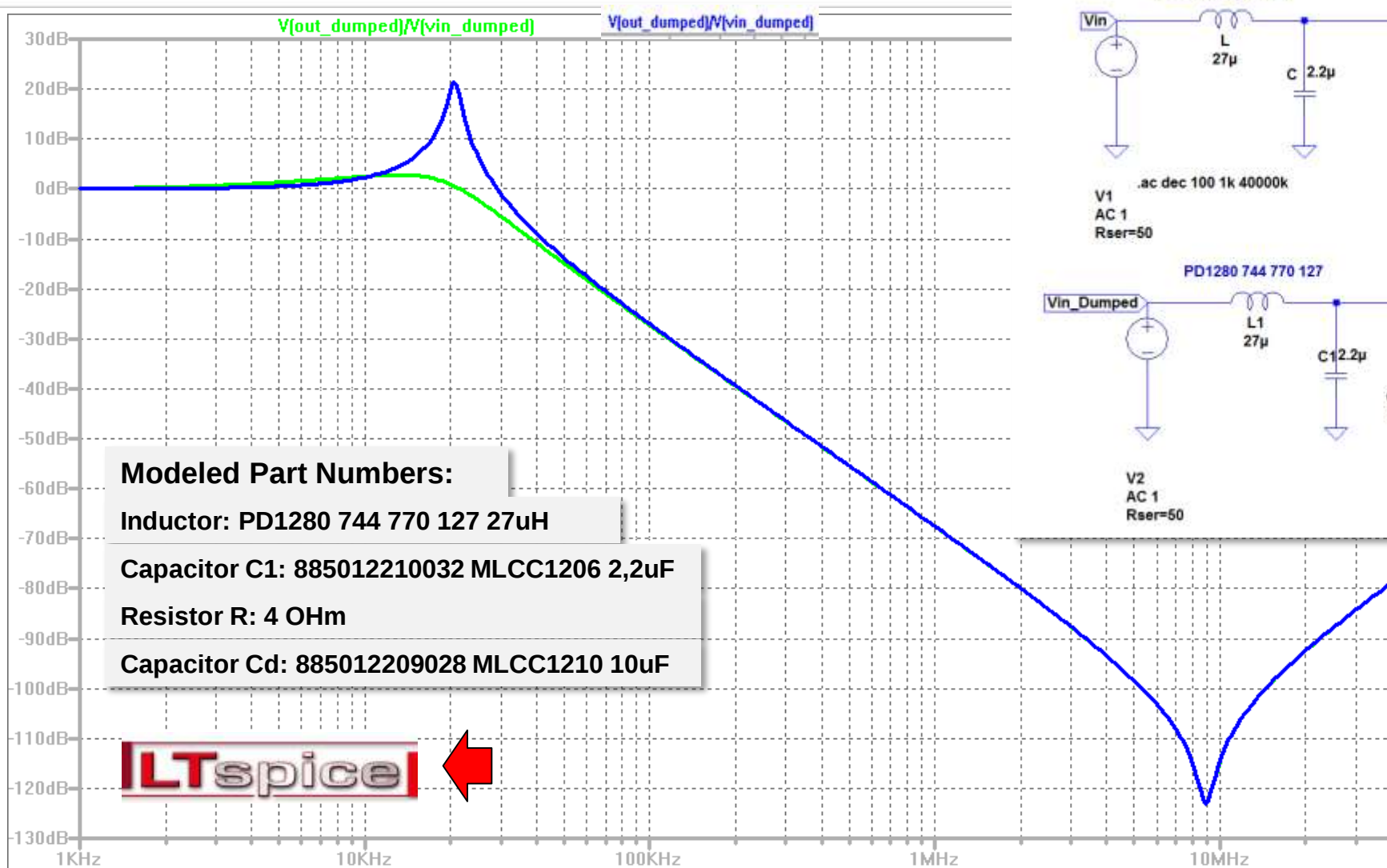

SEPIC Converter Example

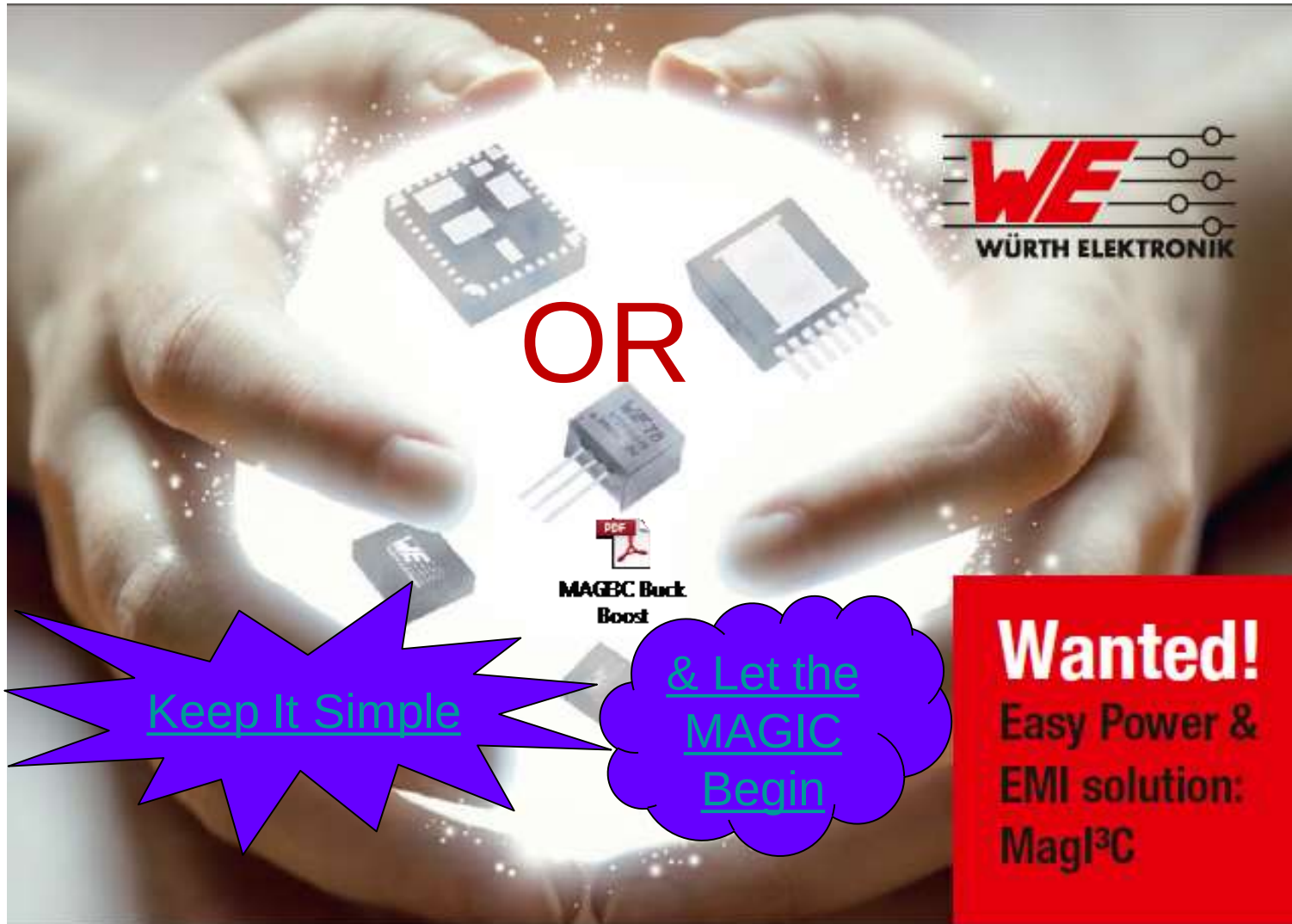

OR

MAGEC Buck Boost

Keep It Simple

& Let the MAGIC Begin

Wanted!
Easy Power & EMI solution:
MagI³C

Thank you

Any Questions

