

We need to
talk about
GROUND



[Follow this link to watch on
YouTube](#)

James Pawson - Unit 3 Compliance

@ Rohde & Schwarz “Demystifying EMC” 2020 

Unit 3 Compliance



Full Pre-Compliance Laboratory


EMC Problem Solving

Design Review

Consultancy

Enviro + Vibration



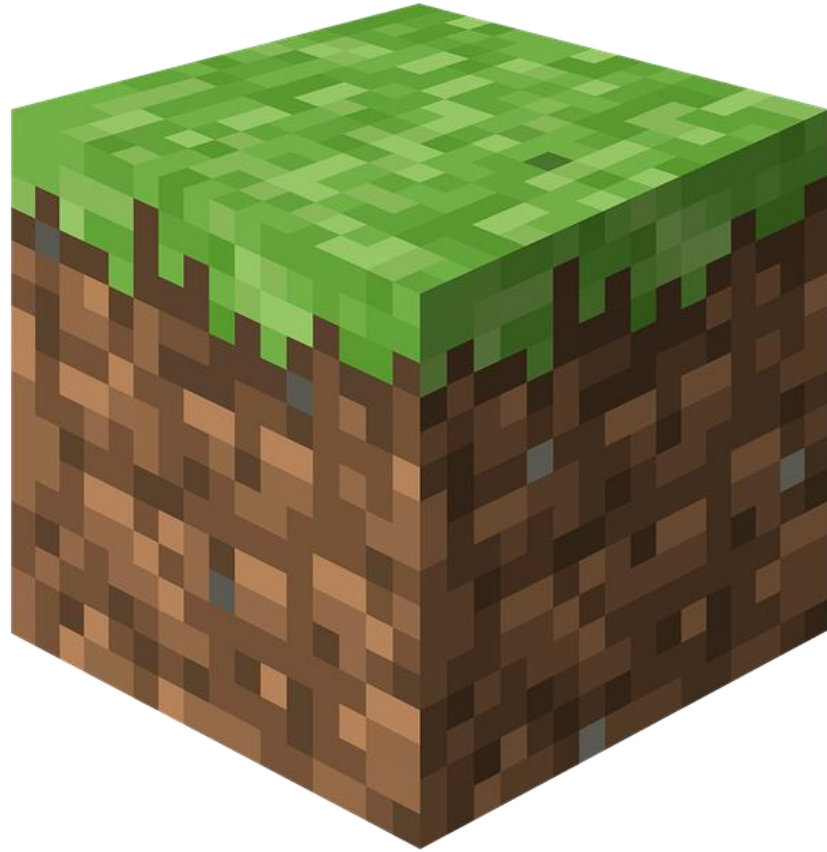





A lack of clarity




Grounds = 1

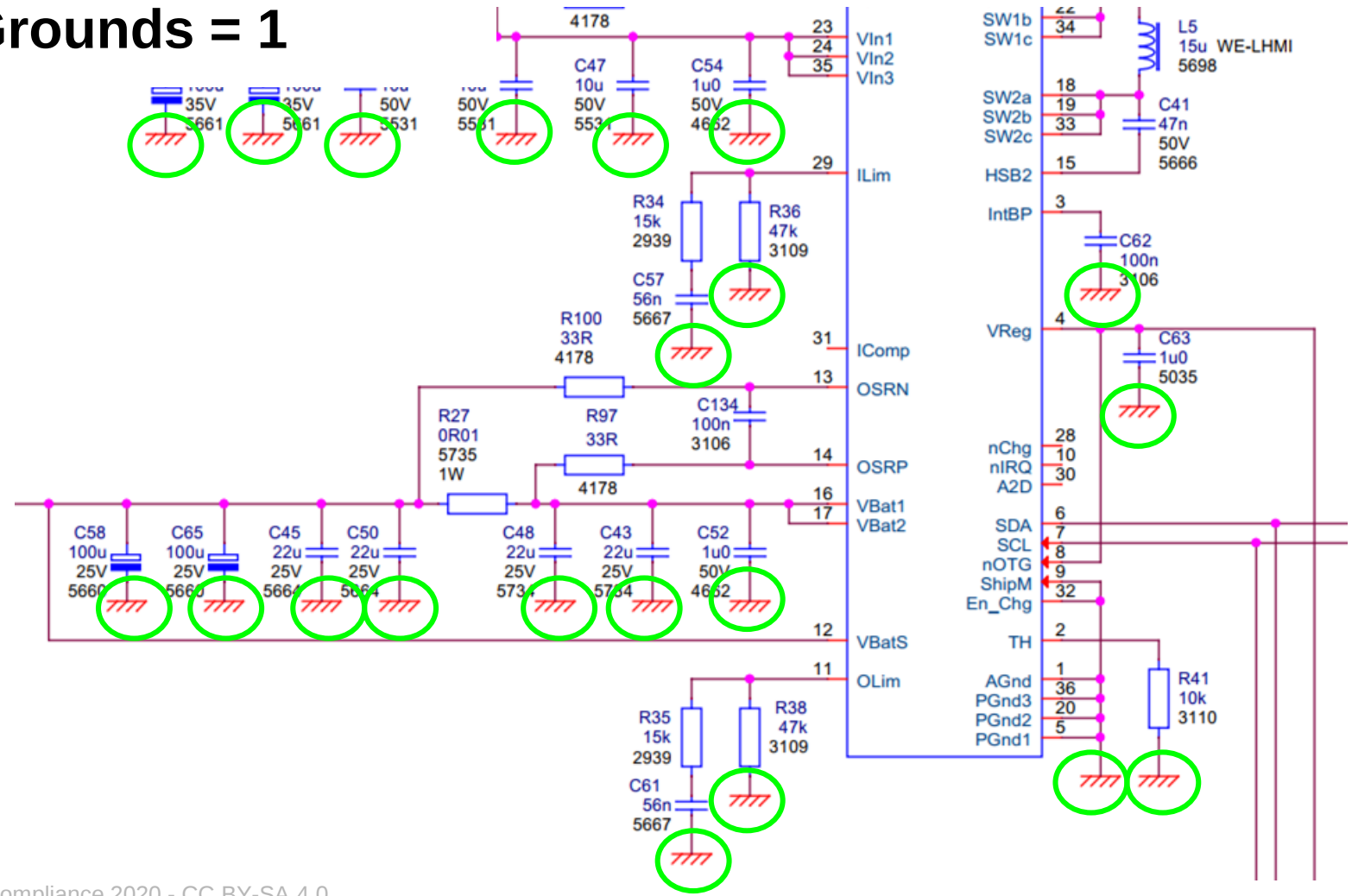


Grounds = 2

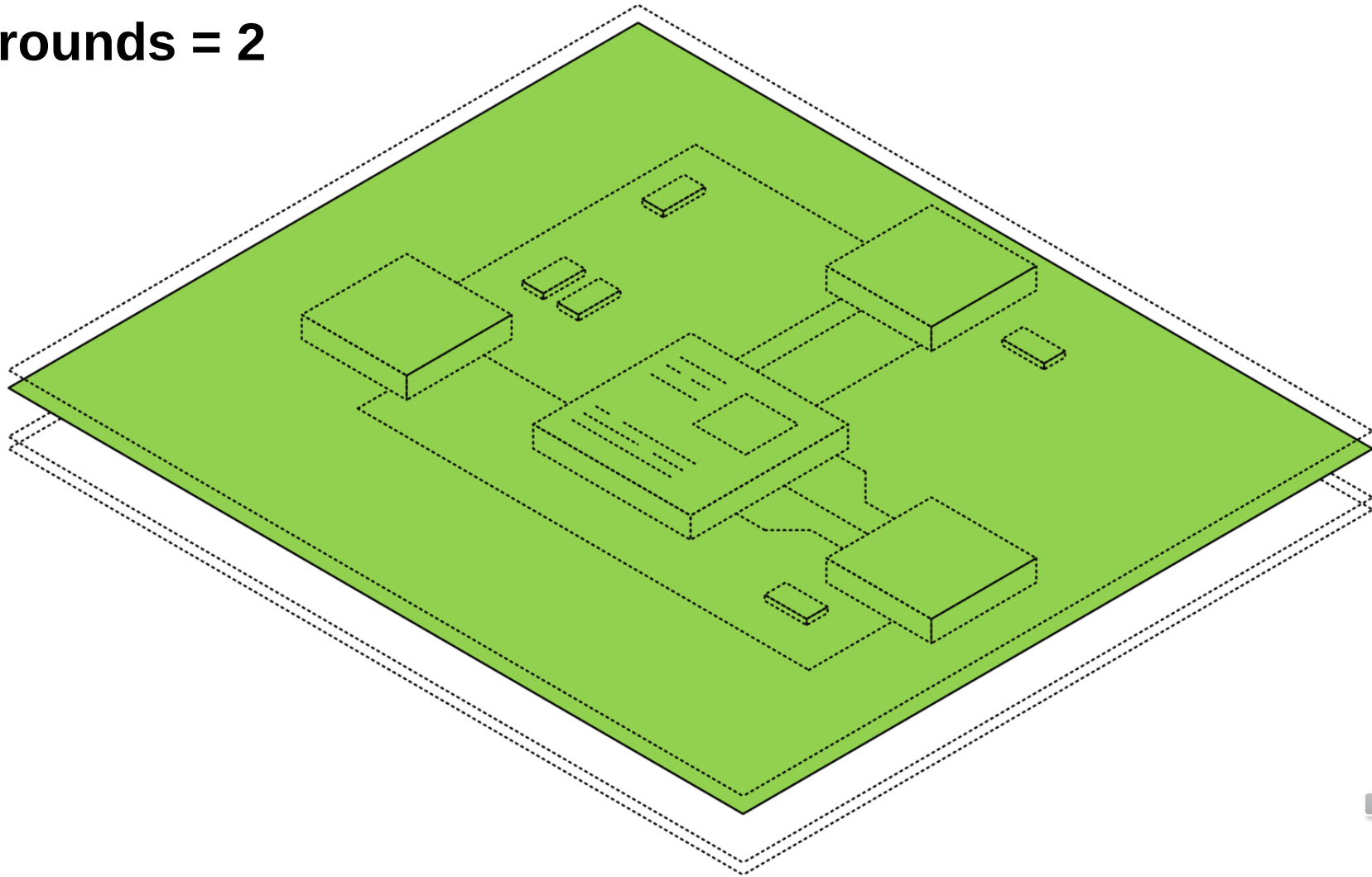


Grounds = 5

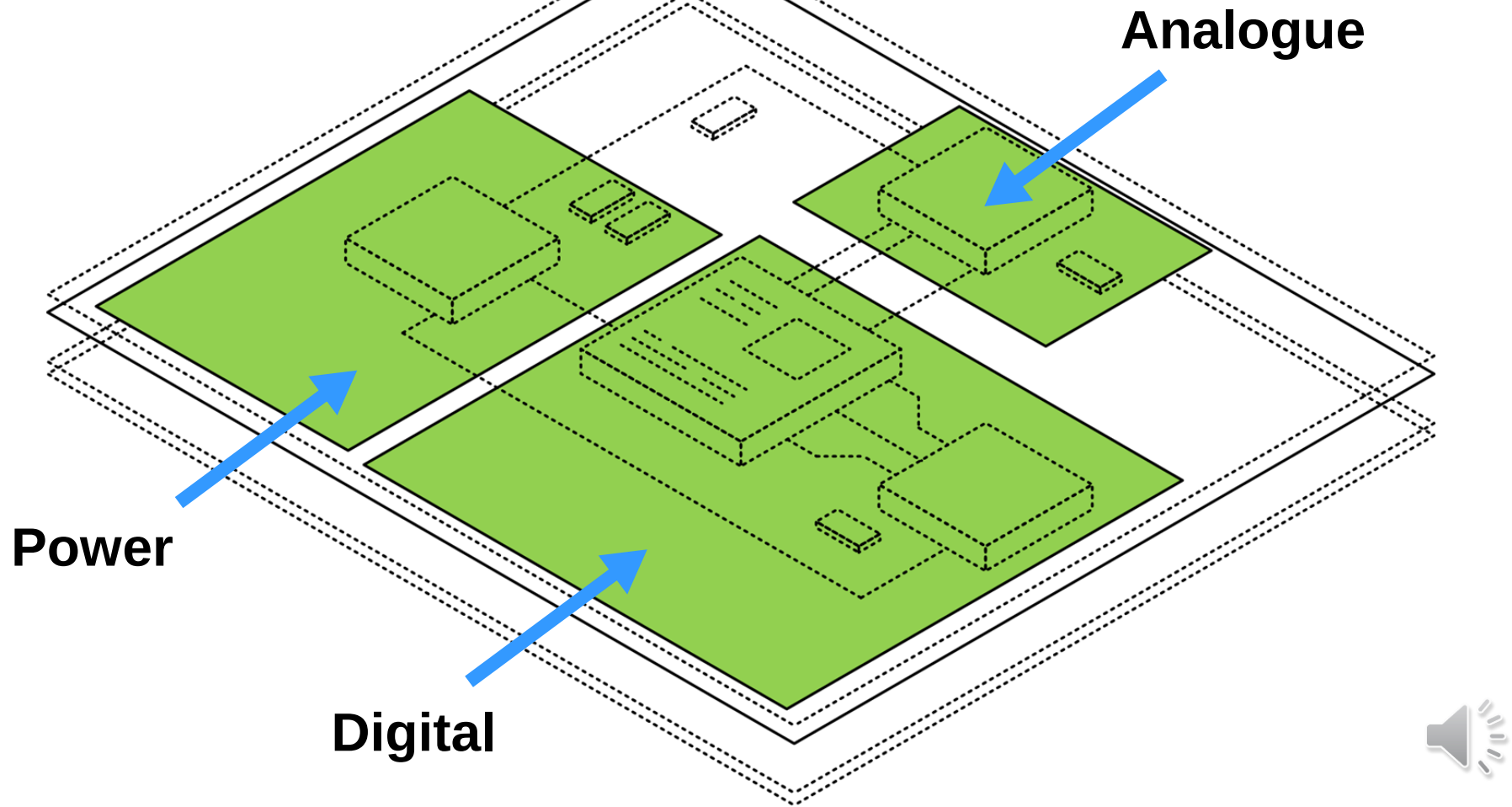


Grounds = 6

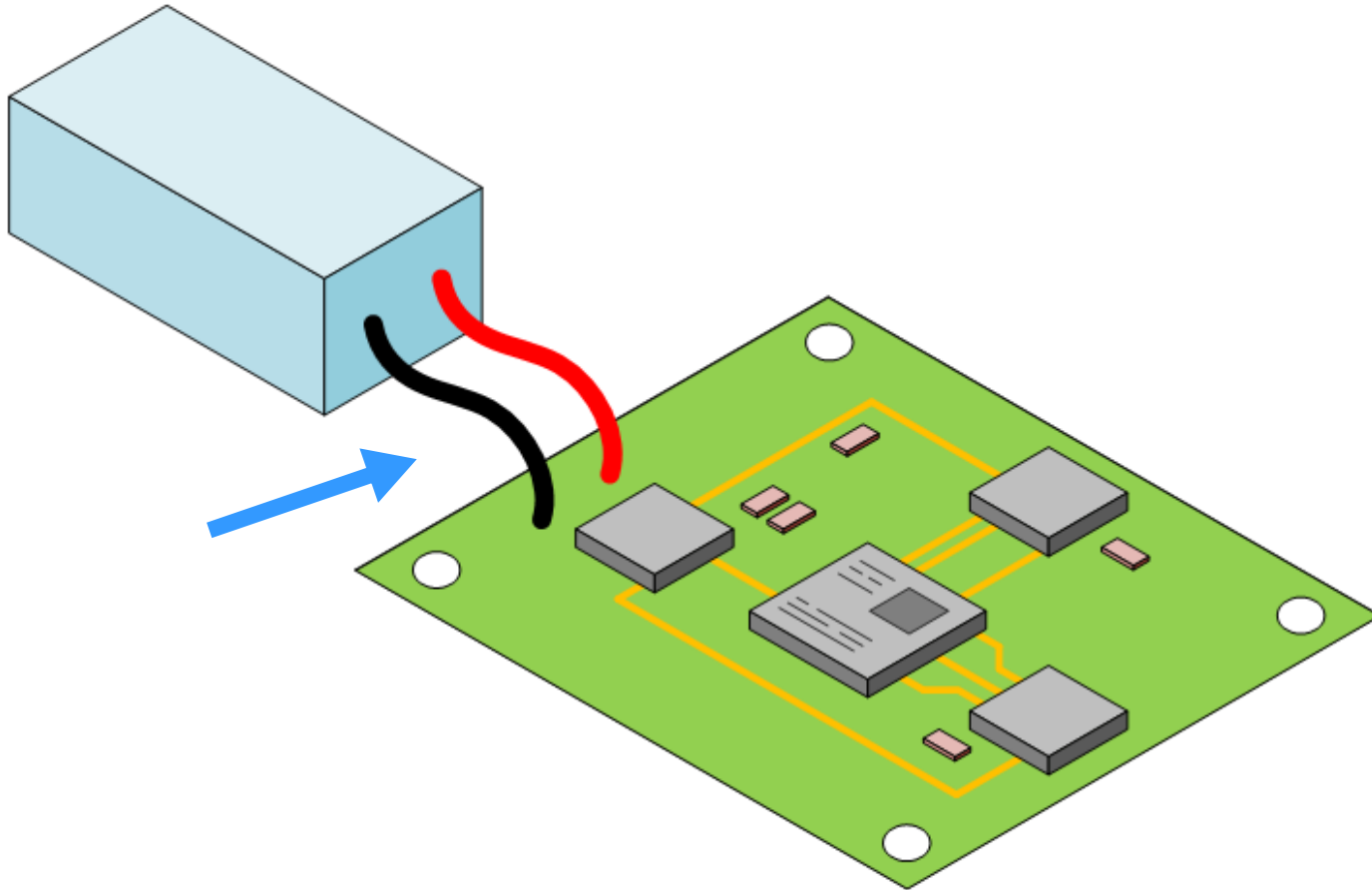


Grounds = 7

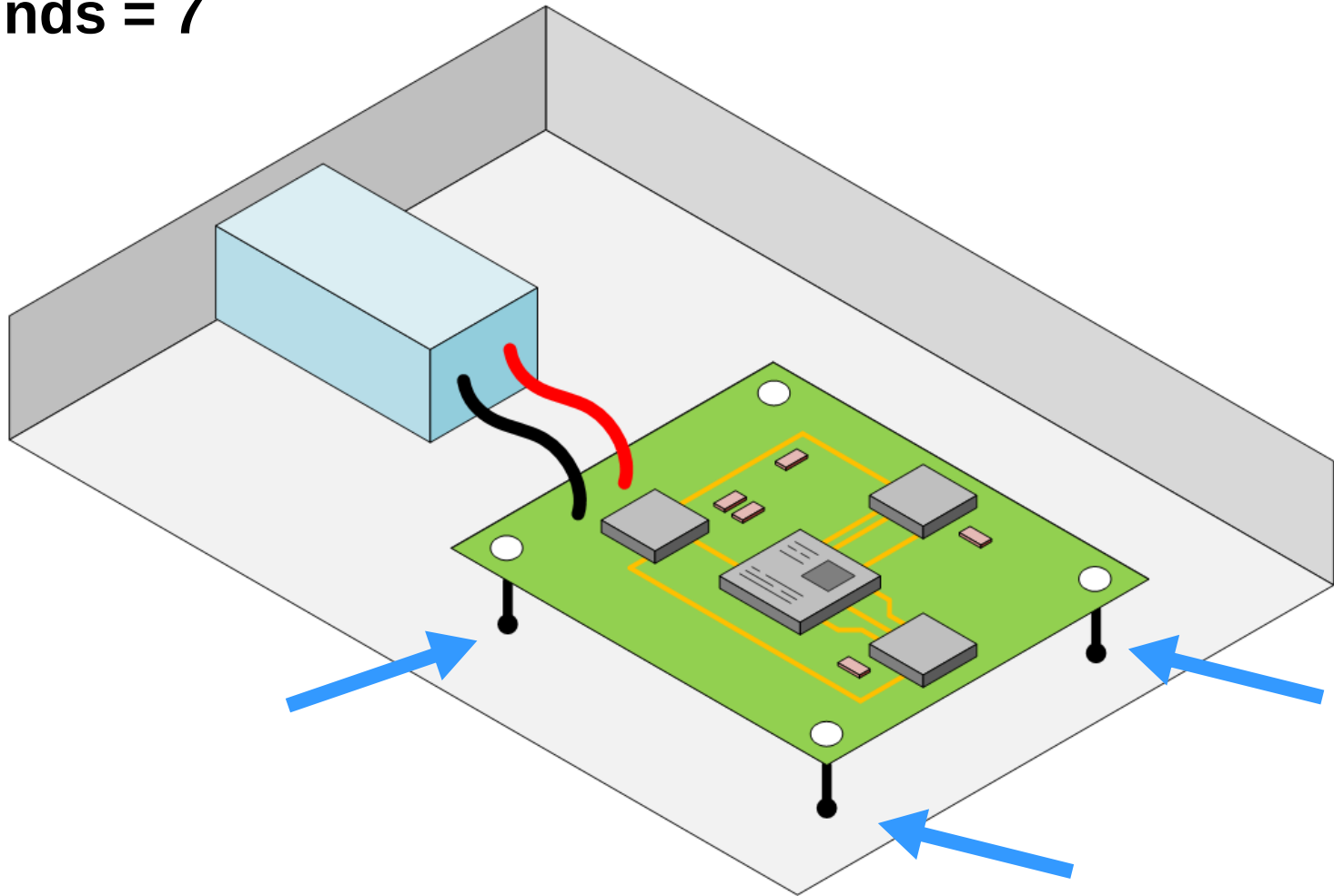


Grounds = 9

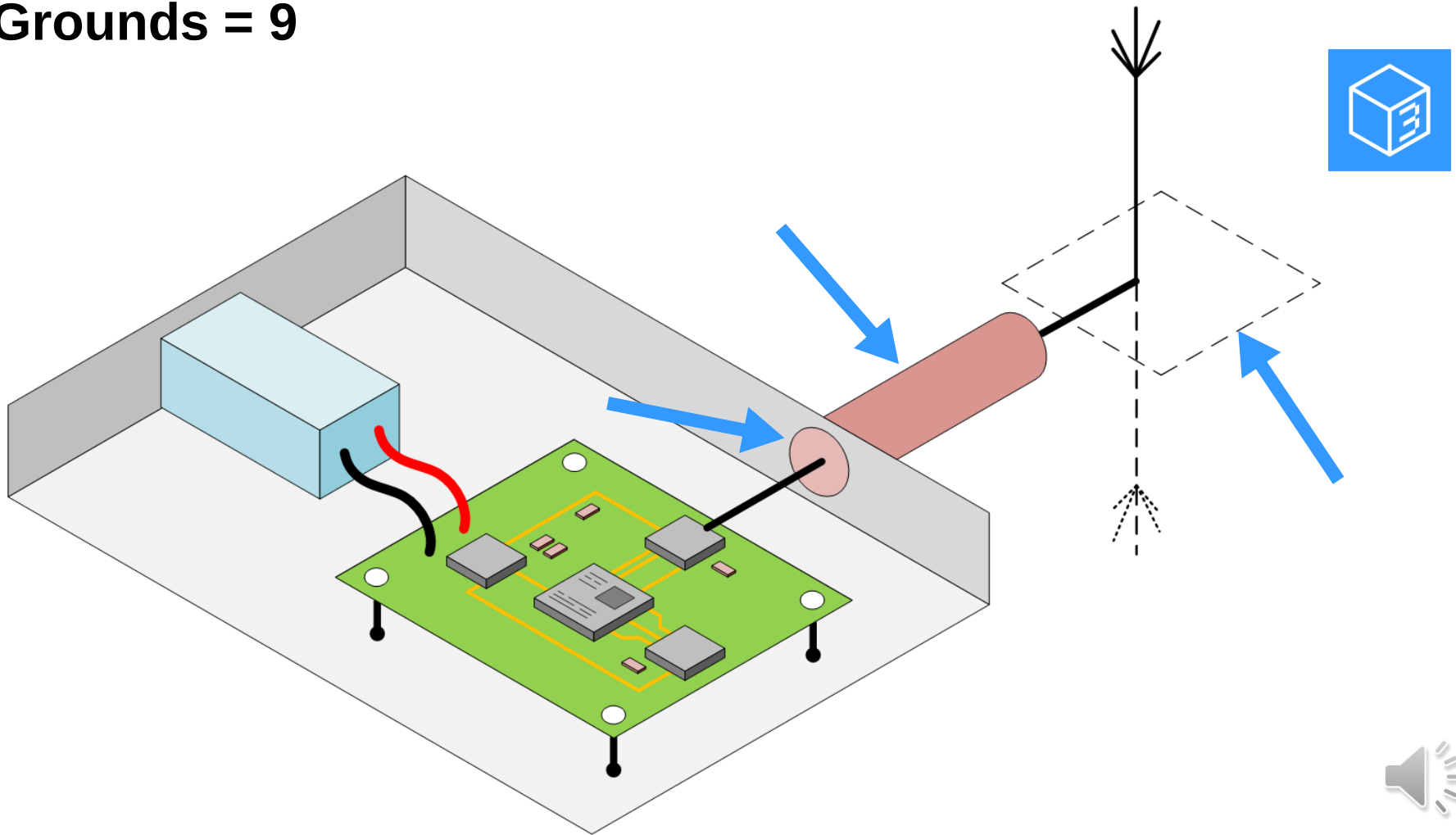


Grounds = 11

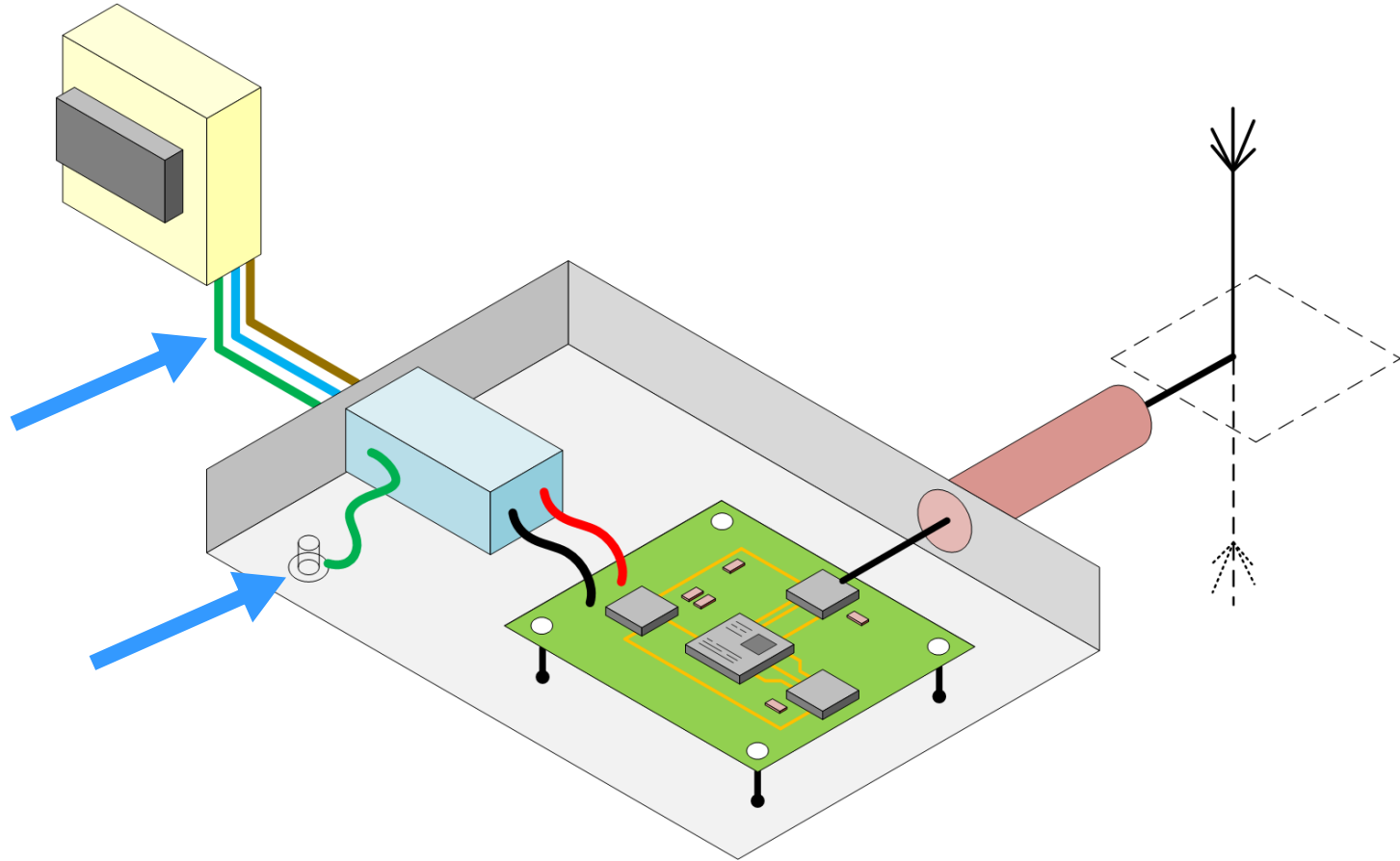


Grounds = 13

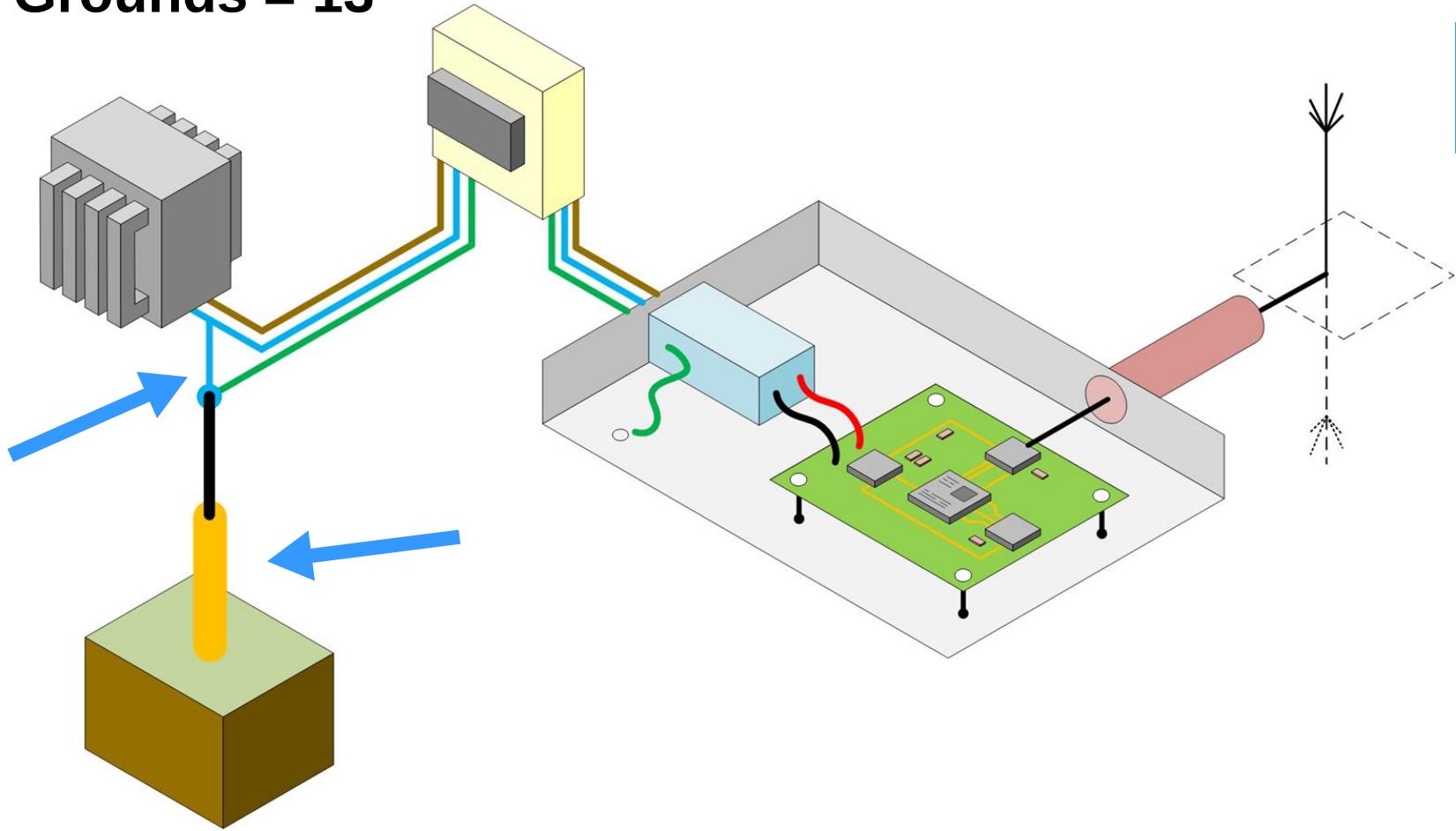

Grounds = 15

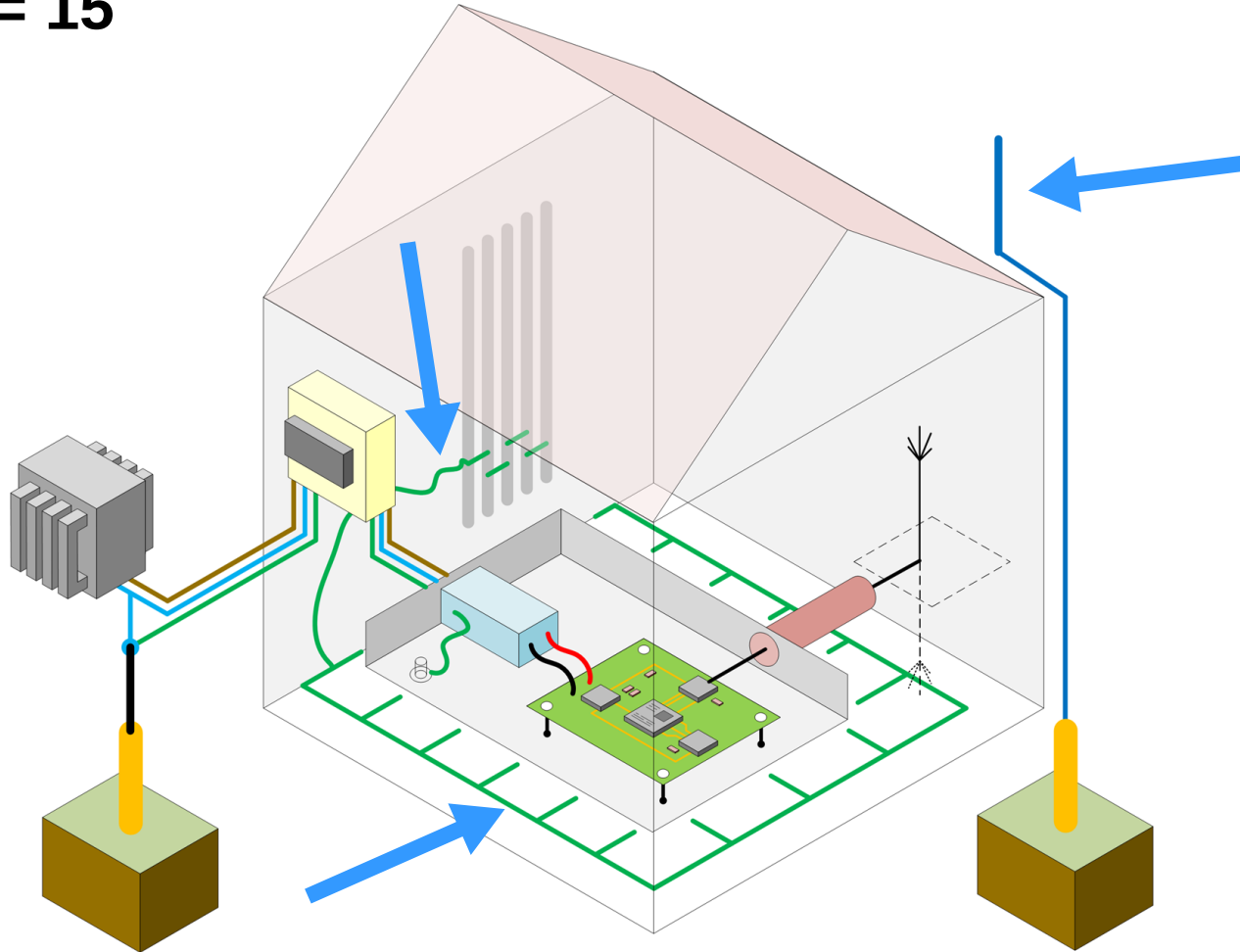

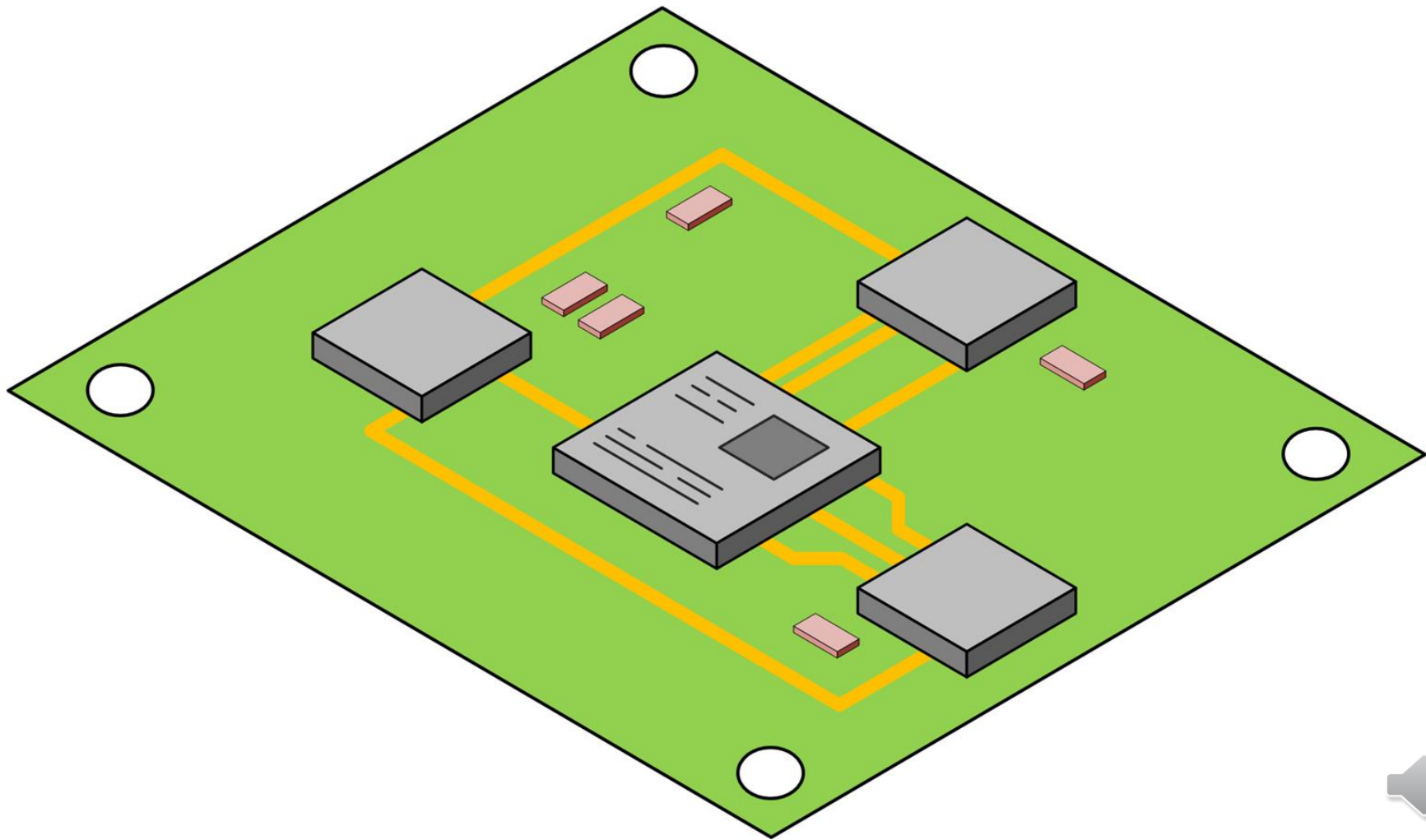



Taxonomy of ground

(from an EMC perspective)







**1) Does it normally
carry current?**




Ground as an equipotential

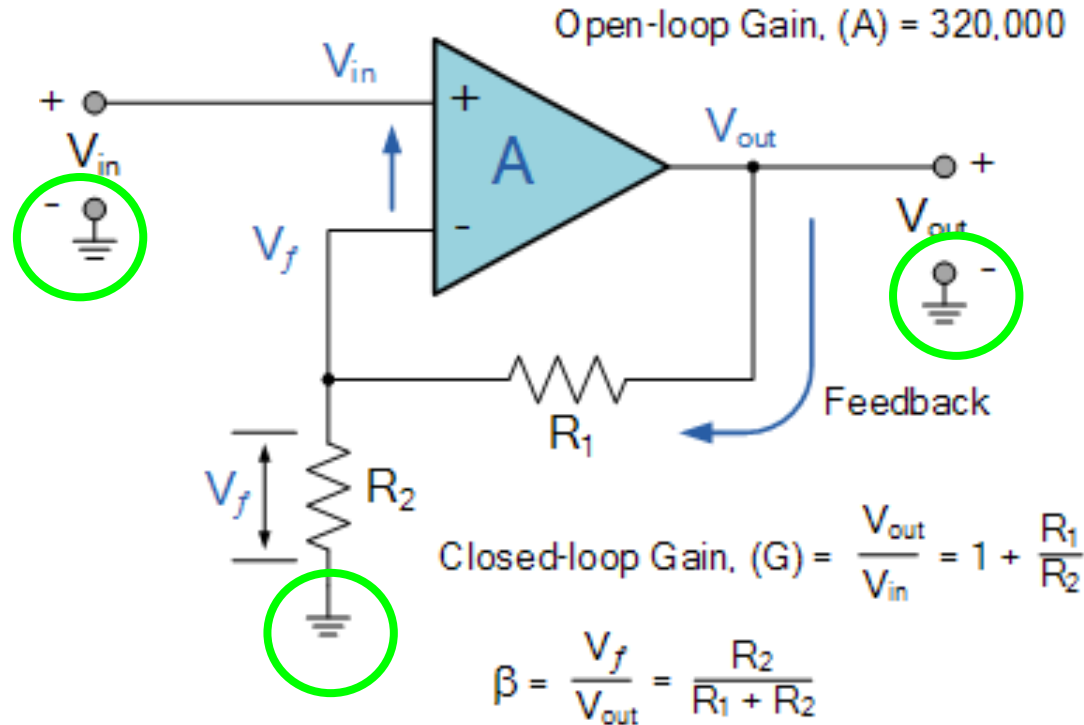

What happens when we close the switch?

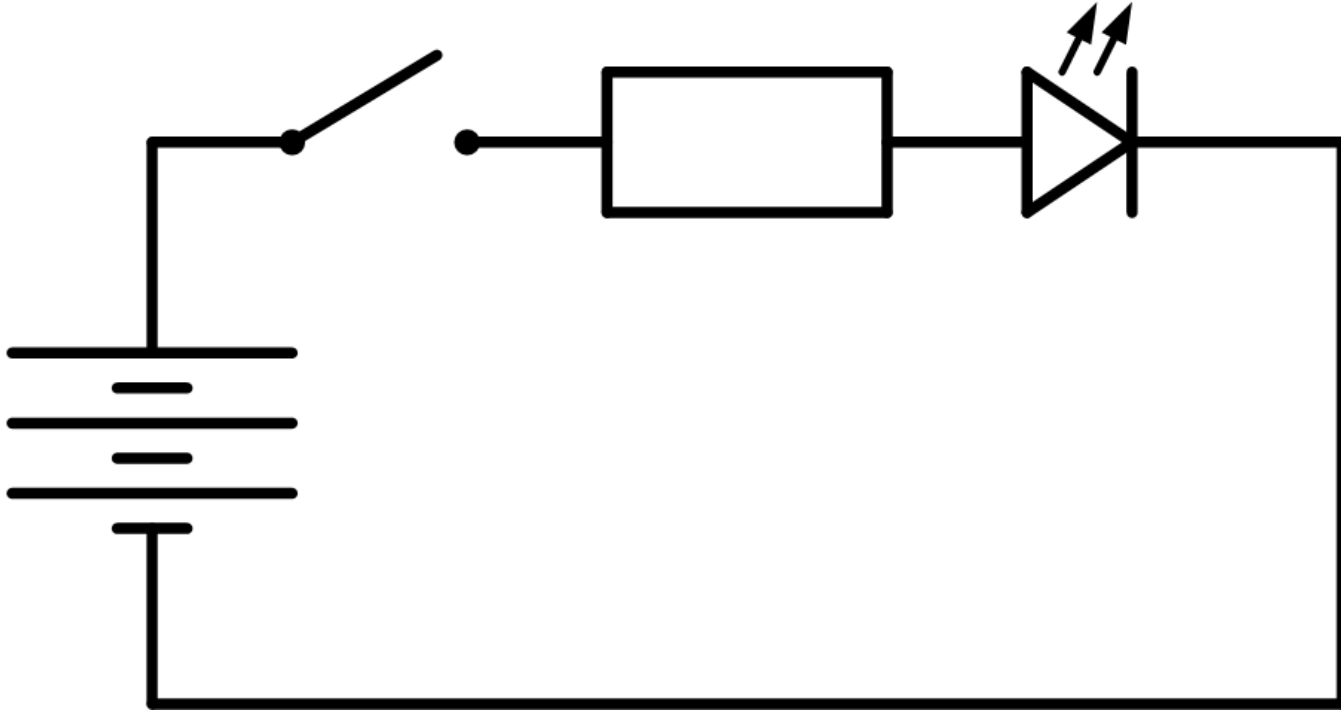

Signal ground current

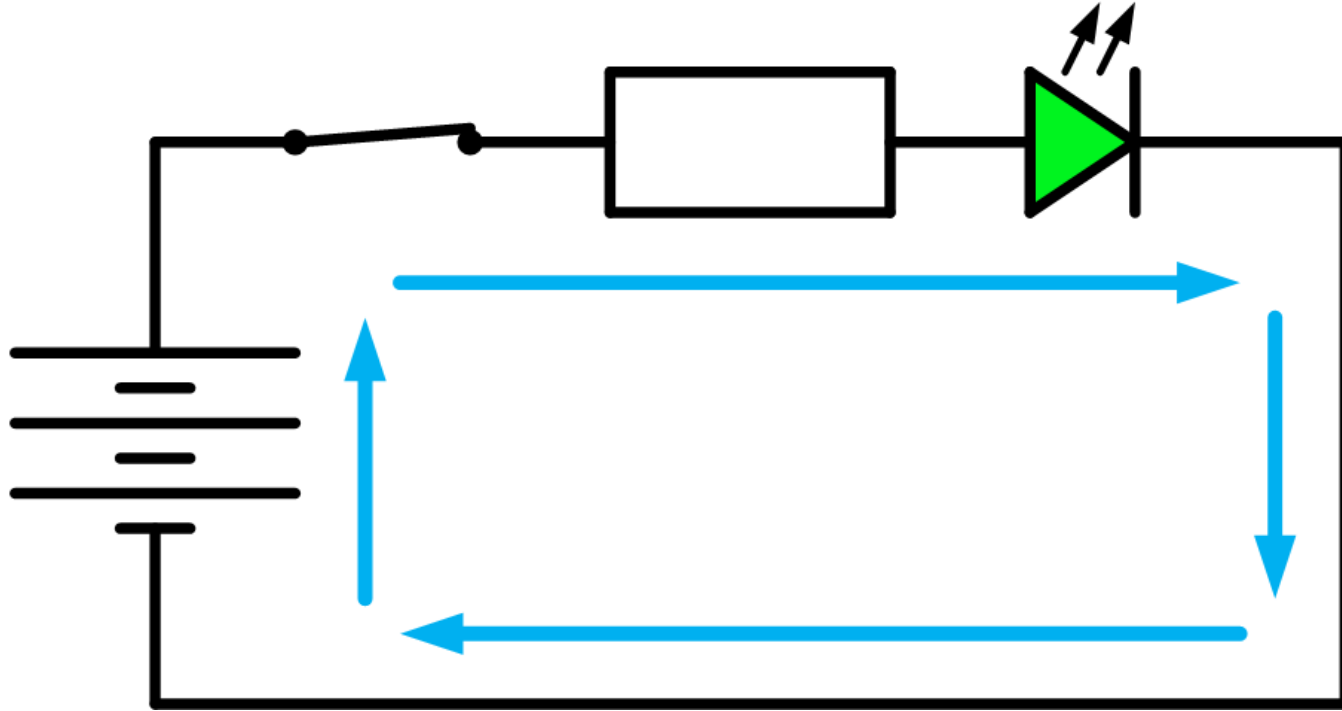

Ground is not a sink



Ground is not a sink

oh hai




we come back






Safety ground current? No.

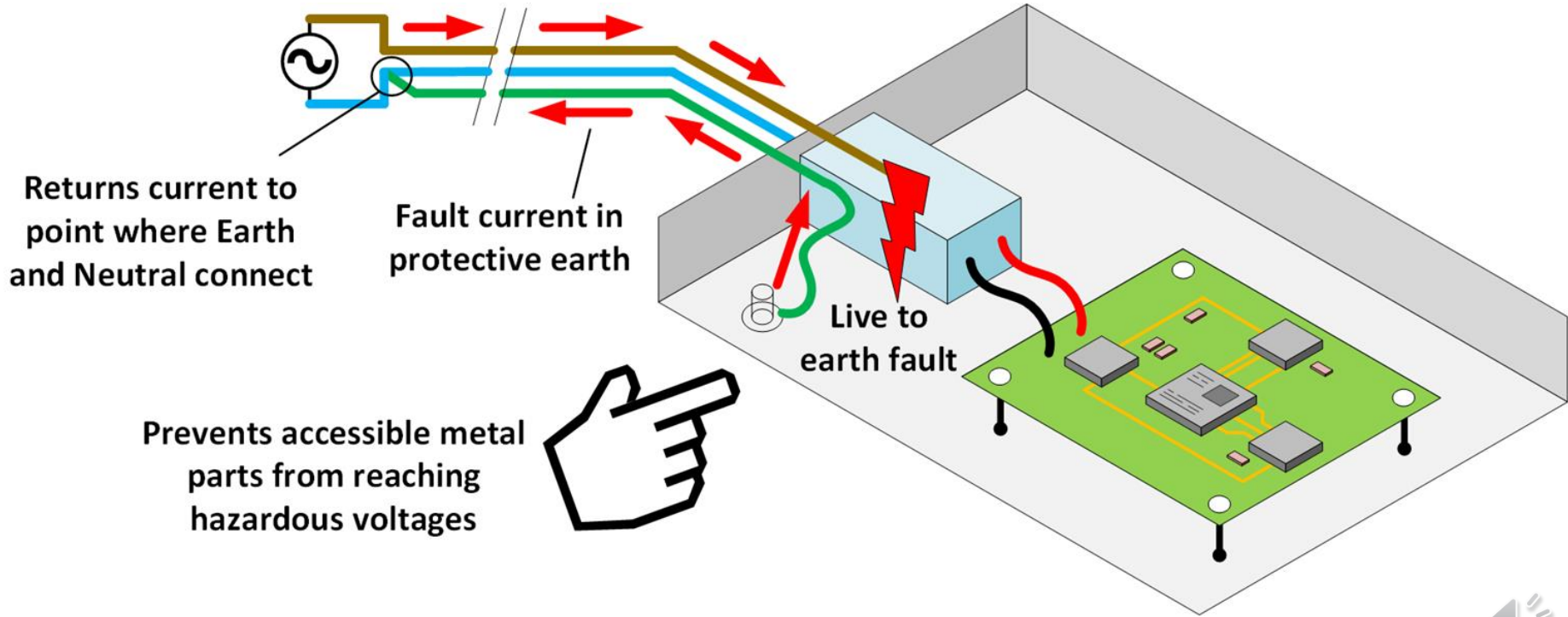

Safety ground current? Yes.

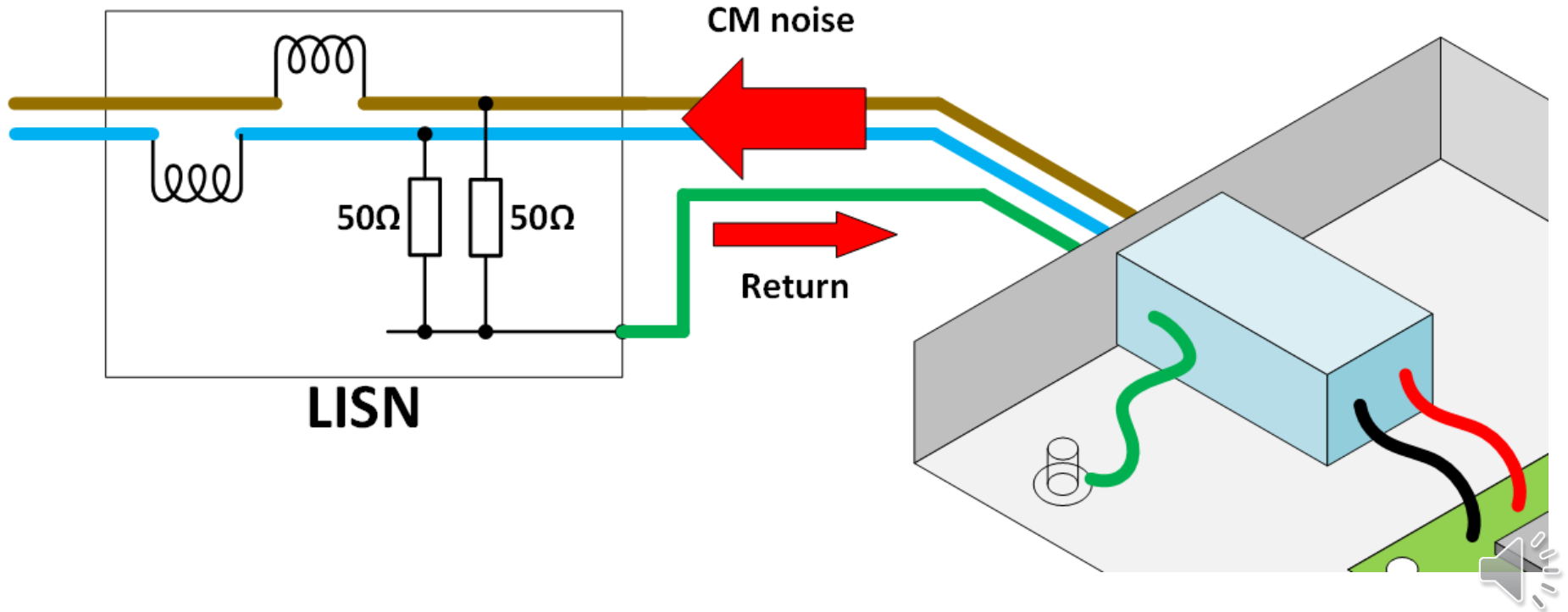



**2) What is the frequency
of this current?**



Current Flow Example




**Thin trace on
Top layer of PCB**


TX

**Ground plane
on Bottom layer**

RX

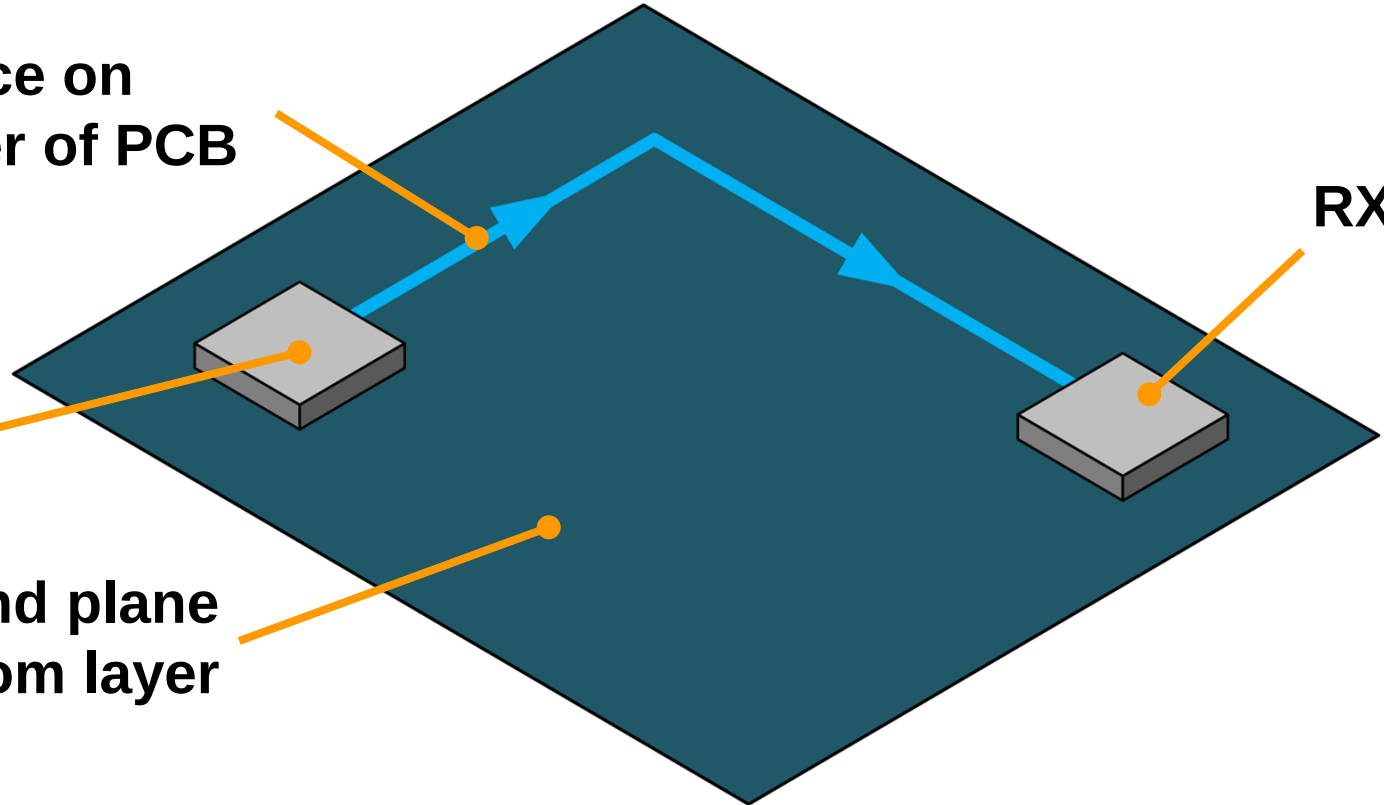


Current Flow Example

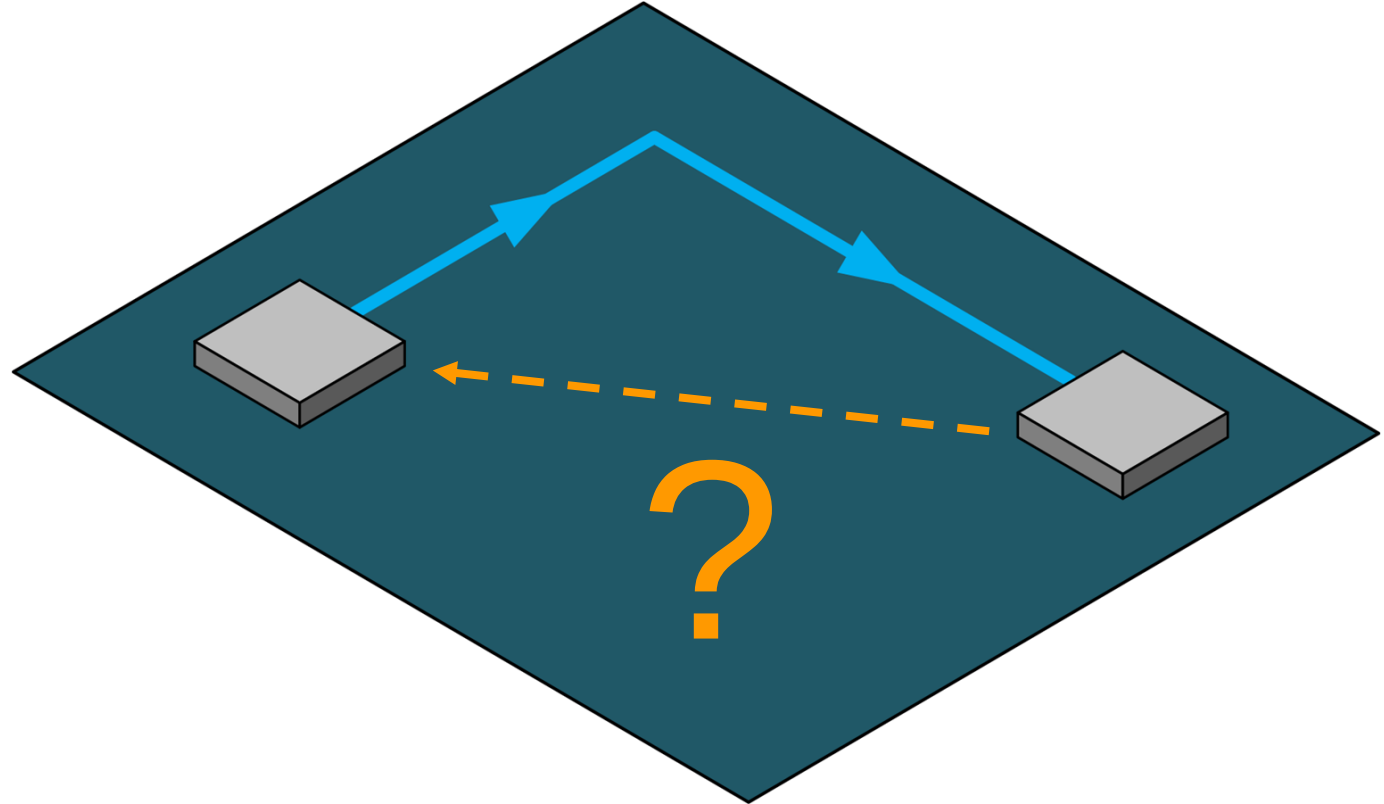

DC Current Flow




DC

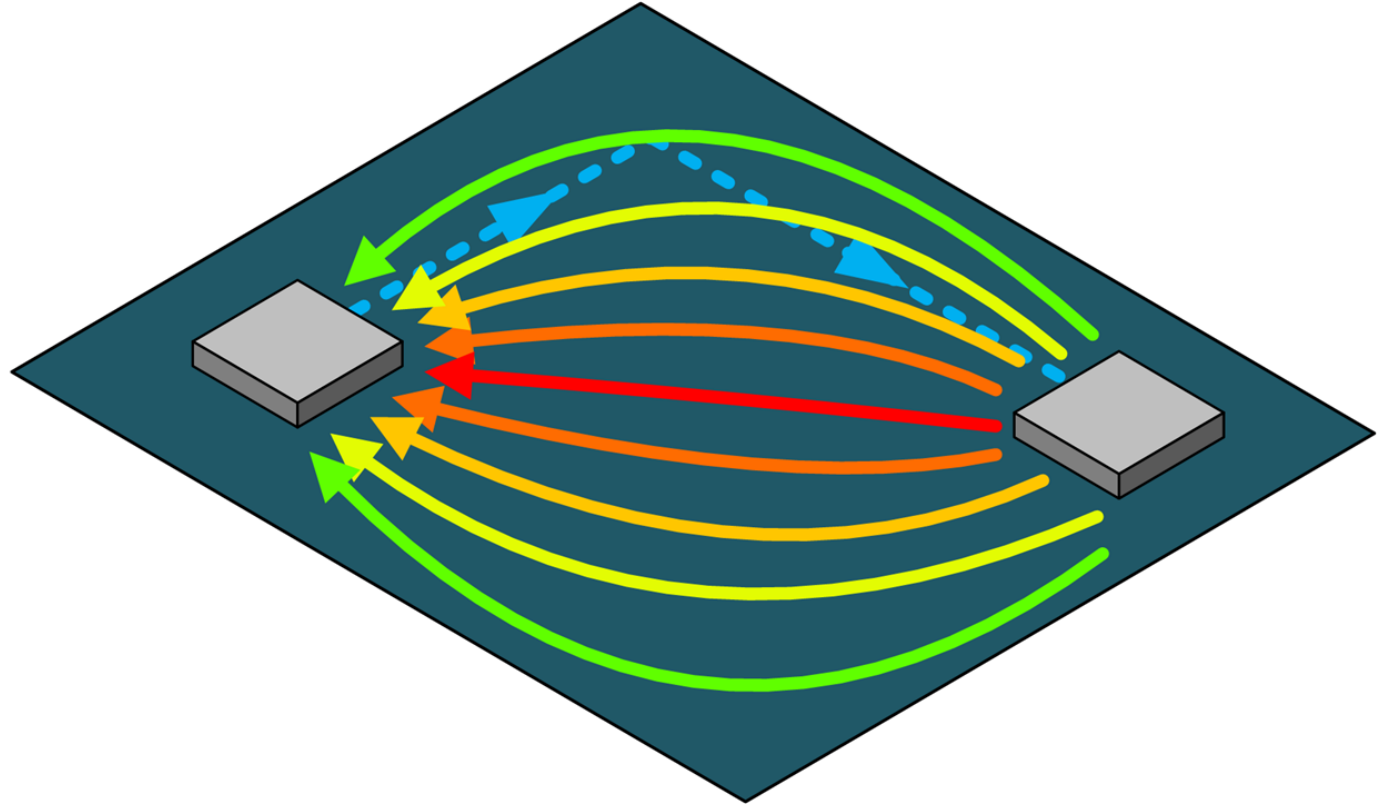



$$R = (\rho \ell) / xsa$$


DC

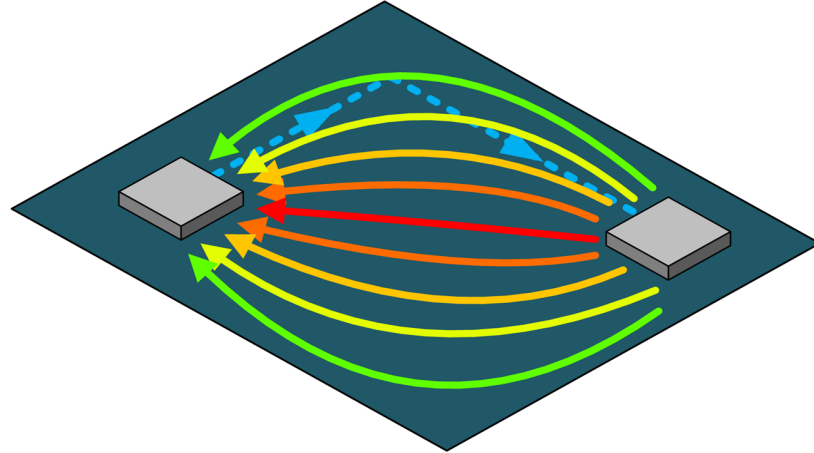

High Frequency Current Flow




50 Hz

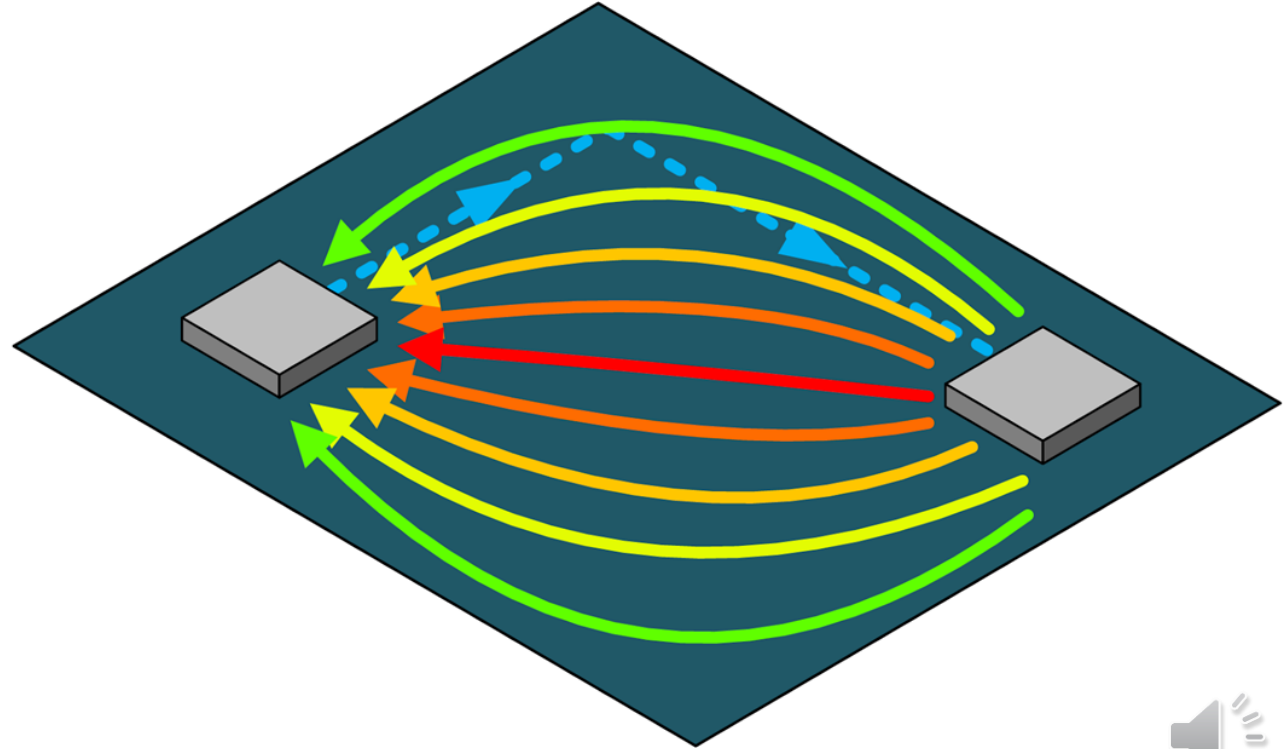

High Frequency Current Flow




500 Hz

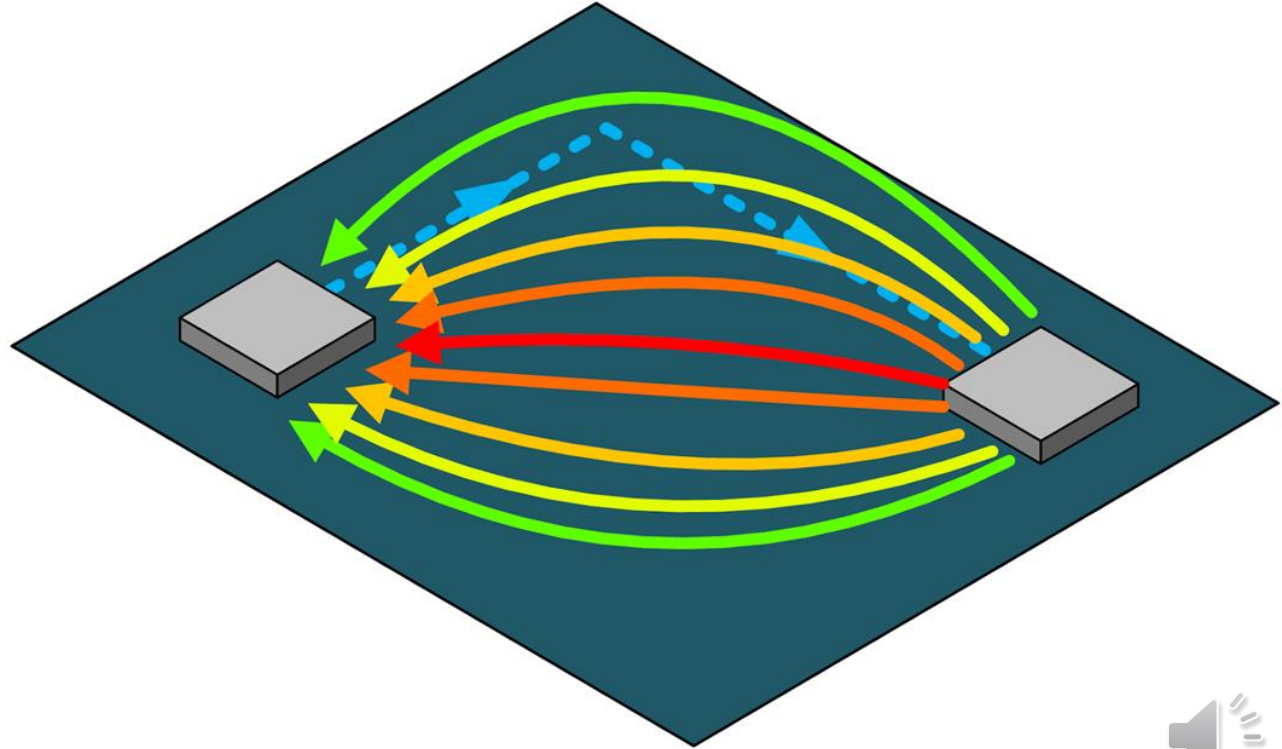

High Frequency Current Flow




5 kHz

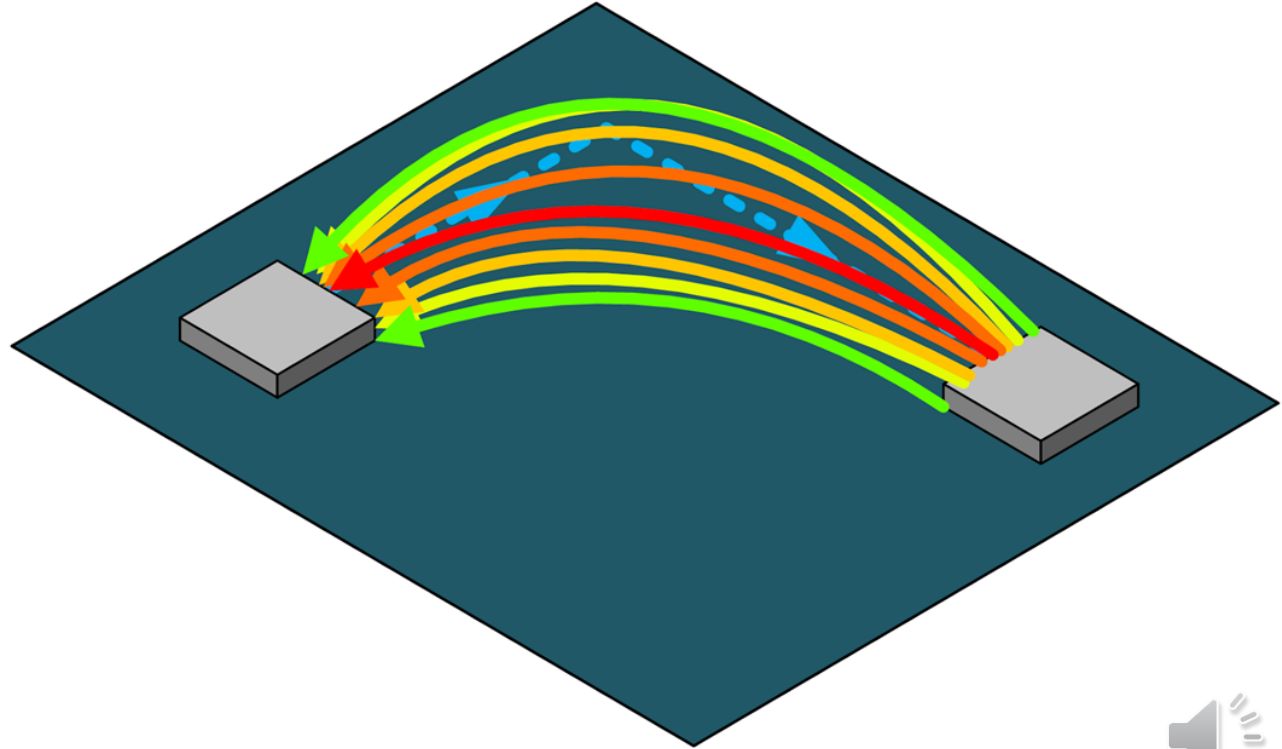

High Frequency Current Flow




50 kHz

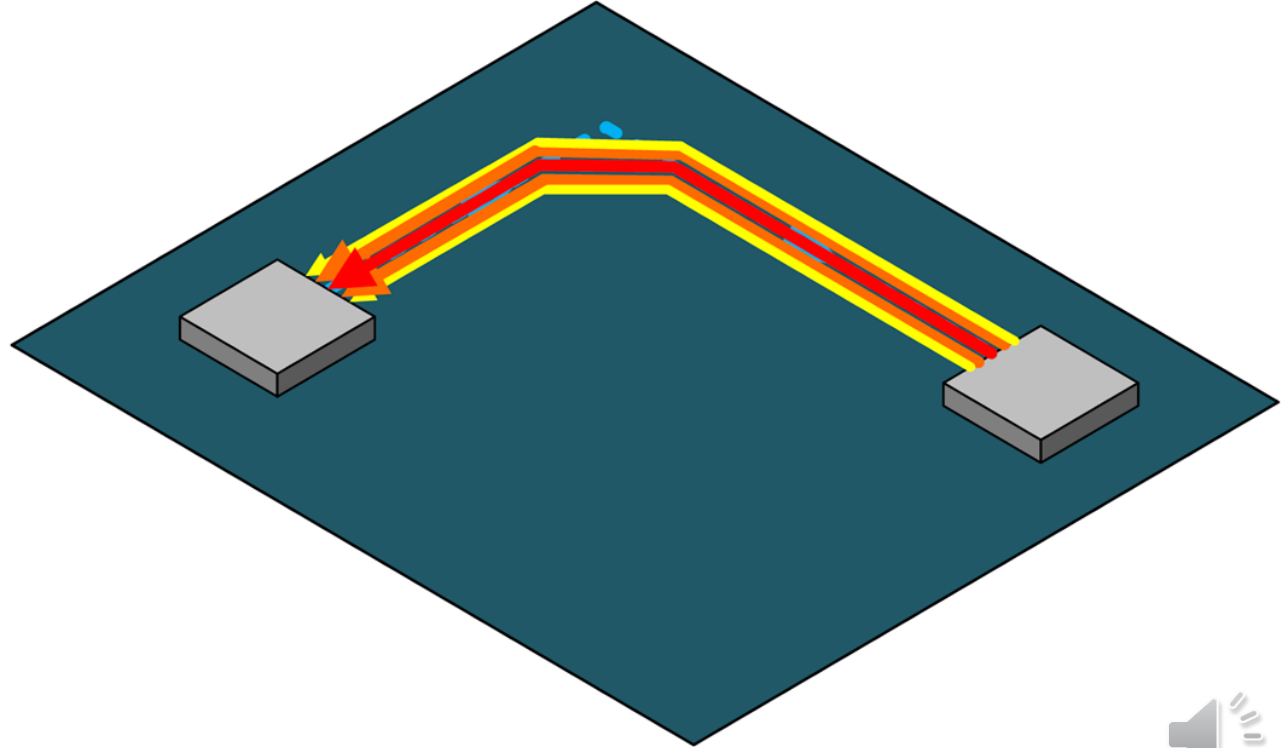

High Frequency Current Flow




500 kHz

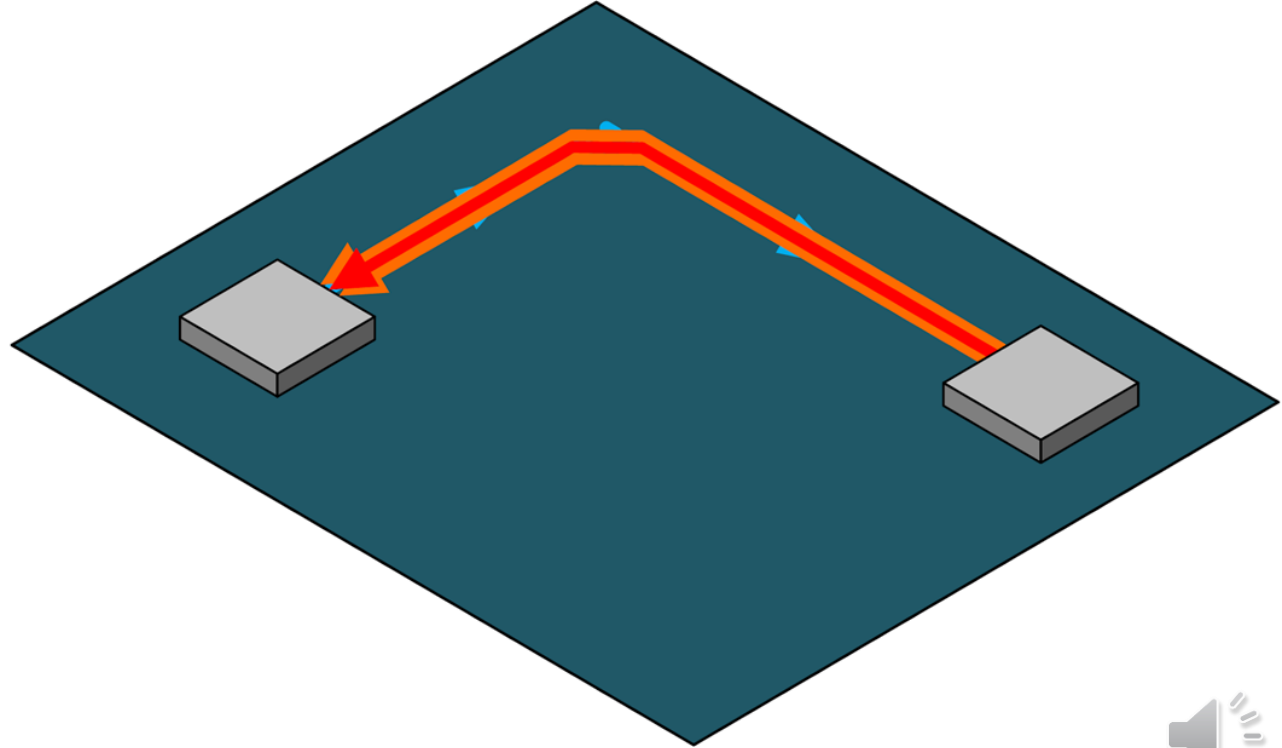

High Frequency Current Flow



5 MHz

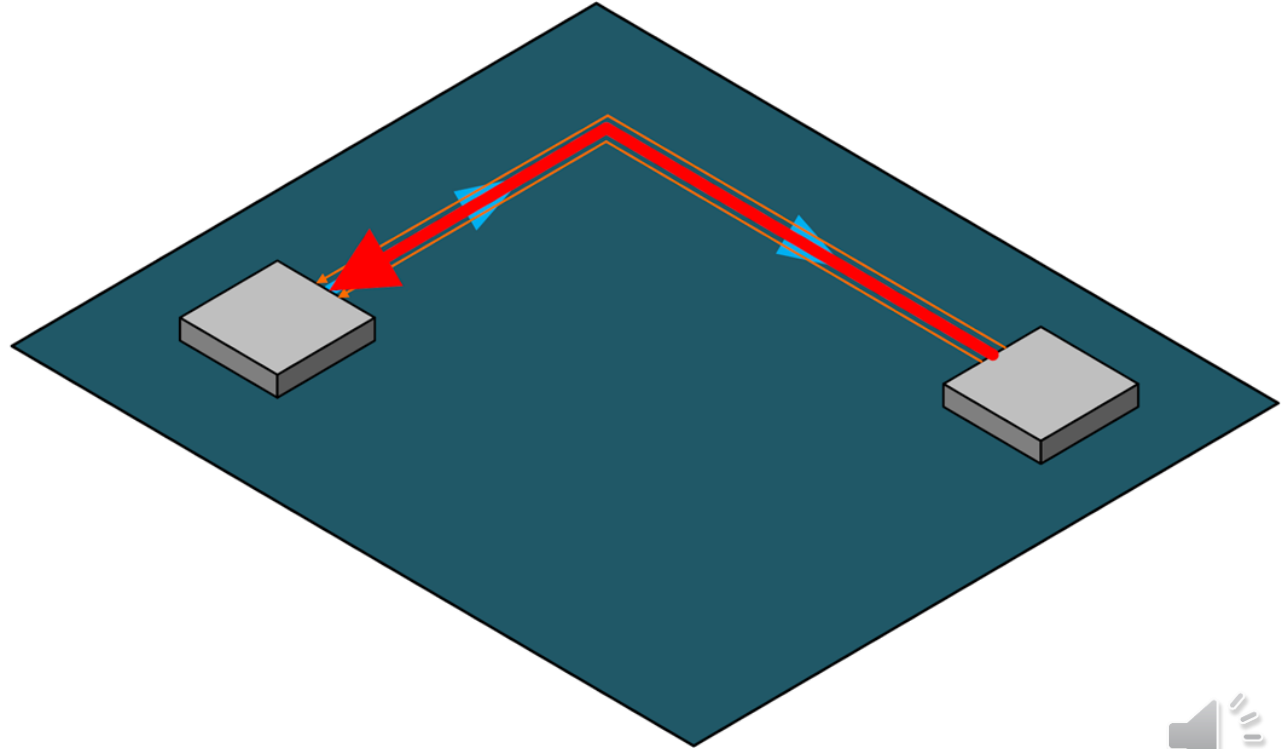



$$R = (\rho \ell) / xsa$$






~~$$R = (\rho \ell) / xsa$$~~

Impedance, $Z_L = 2 \pi f L$


$$L = (\mu N^2 A) / \ell$$



Digital Logic Current

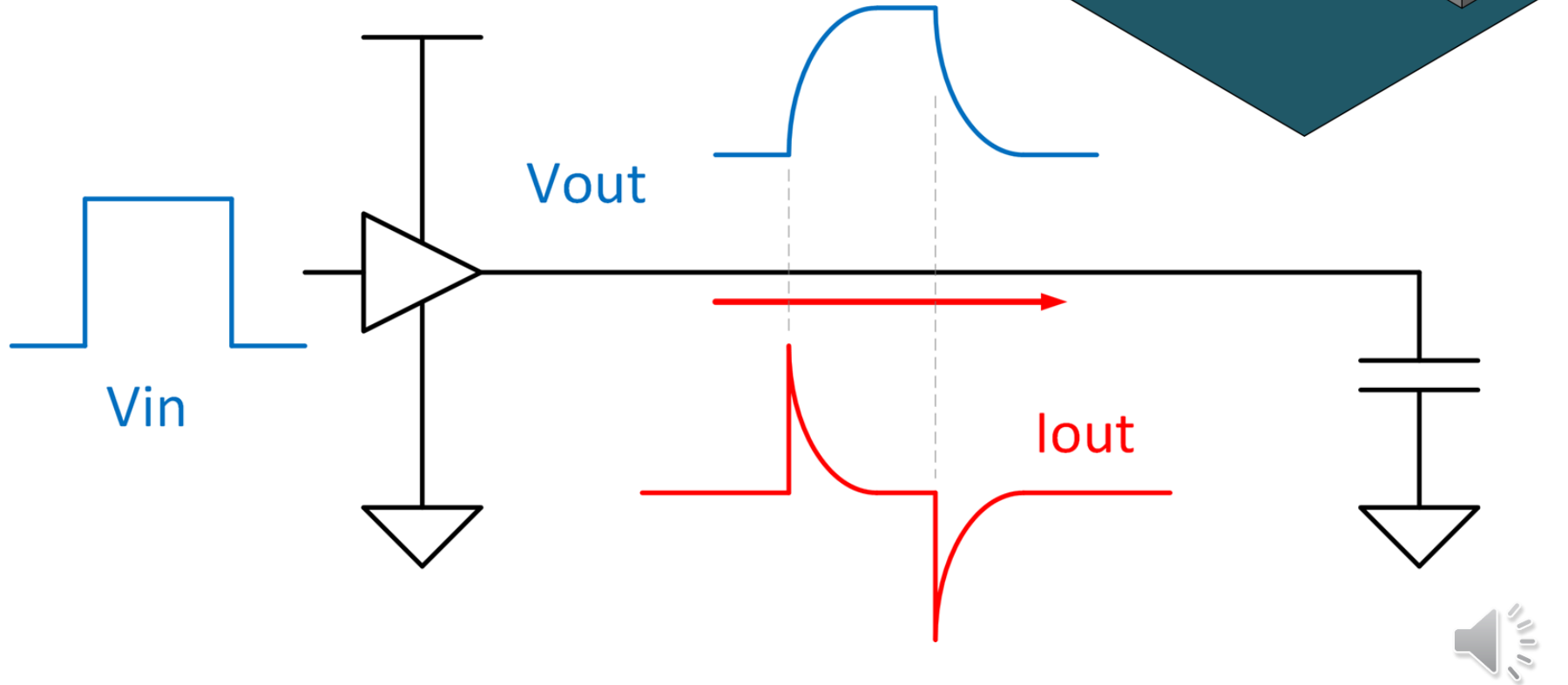


Analogue Power Current

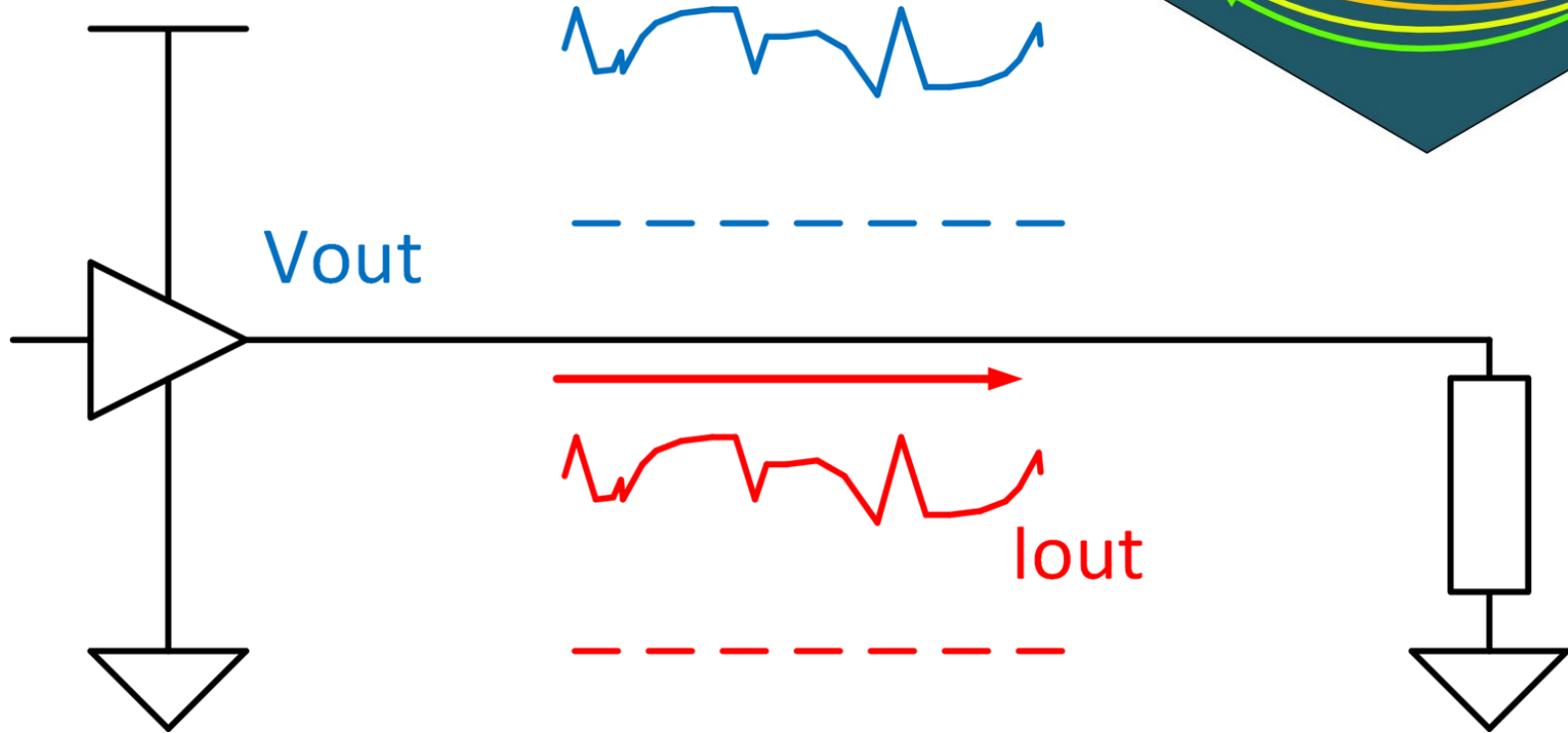

High frequency current flow



DC

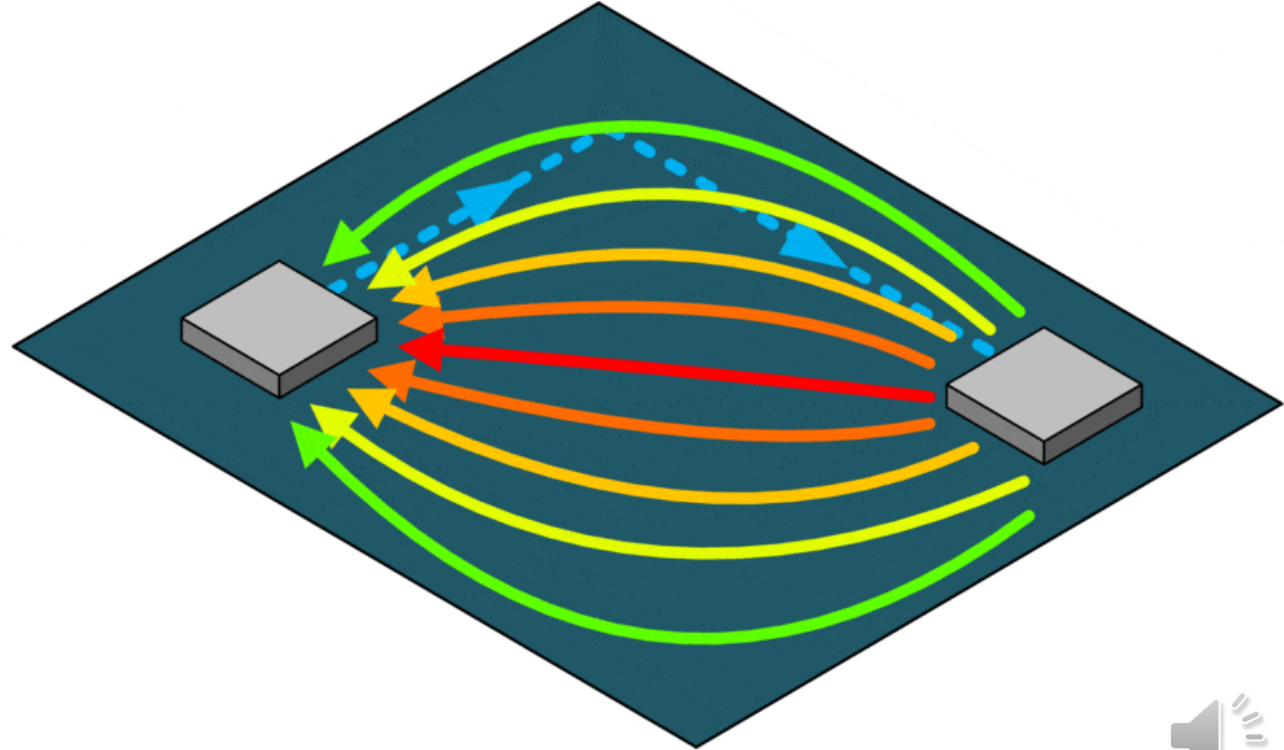




So what?




Implications of non ideal ground?

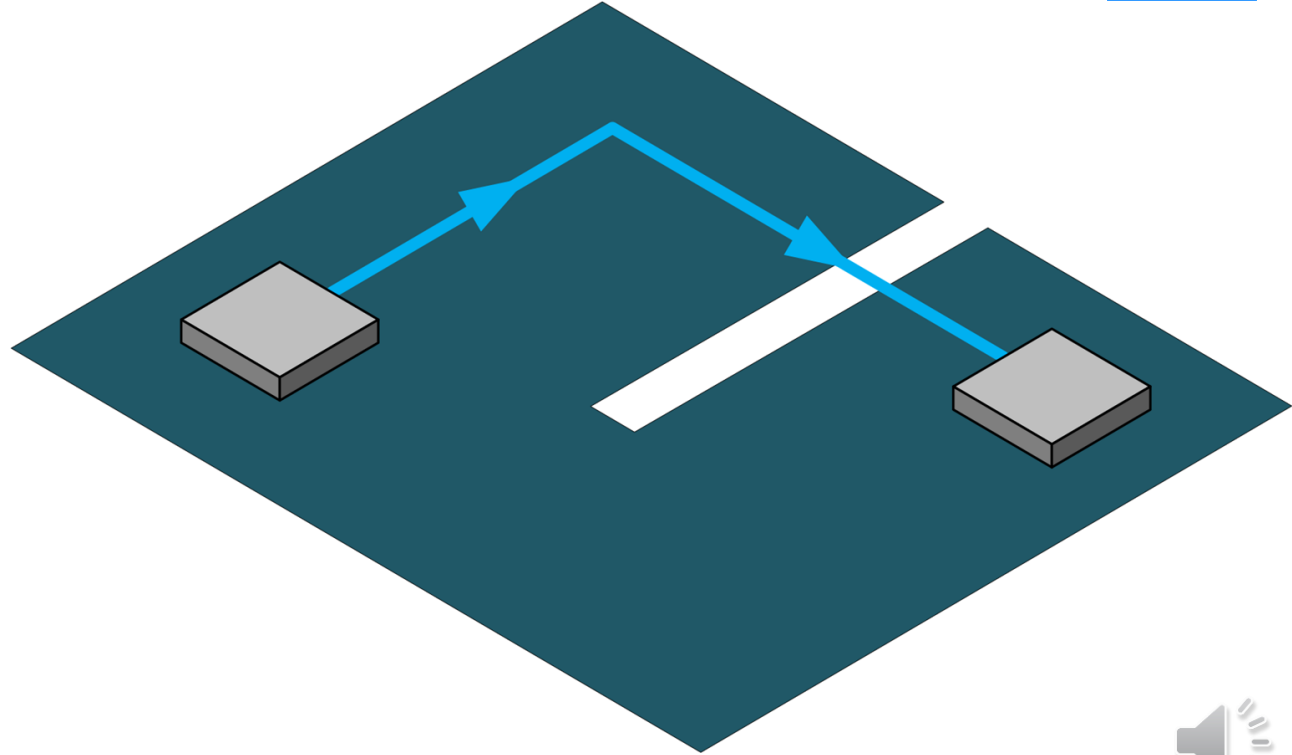

Implications of non ideal ground?




DC

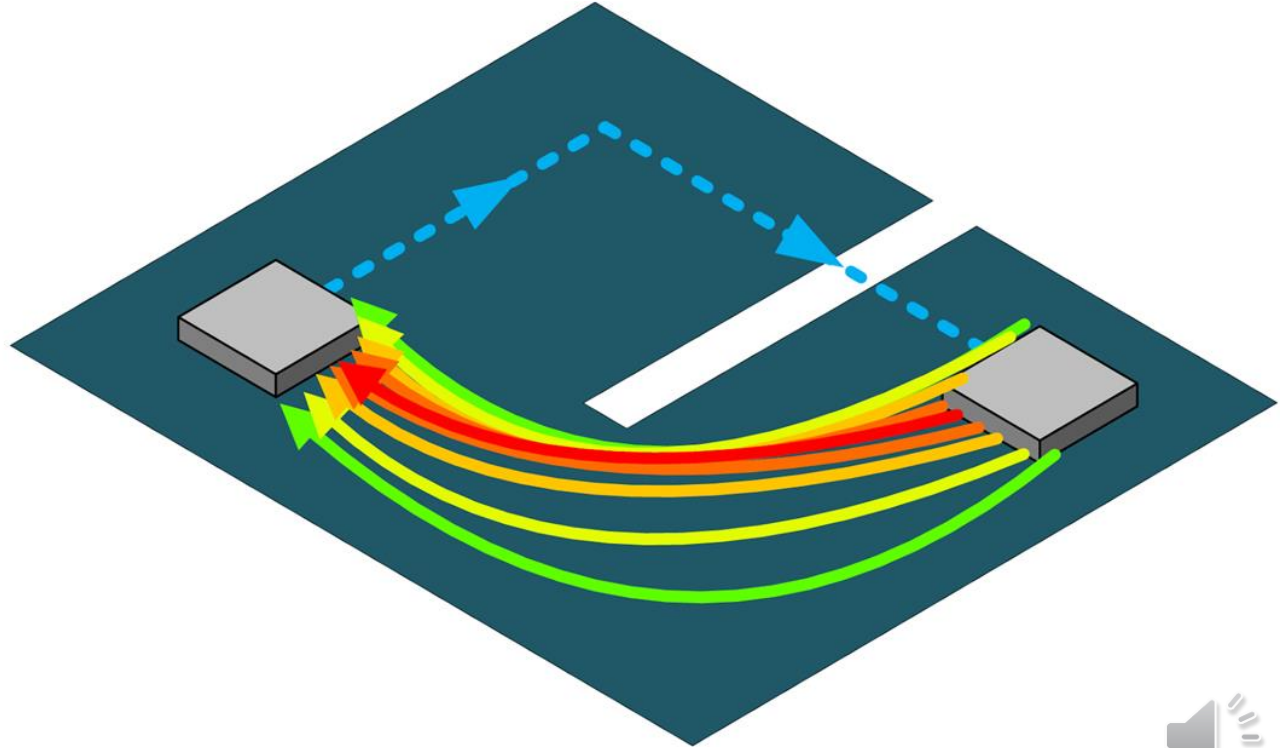


Implications of non ideal ground?




5 MHz

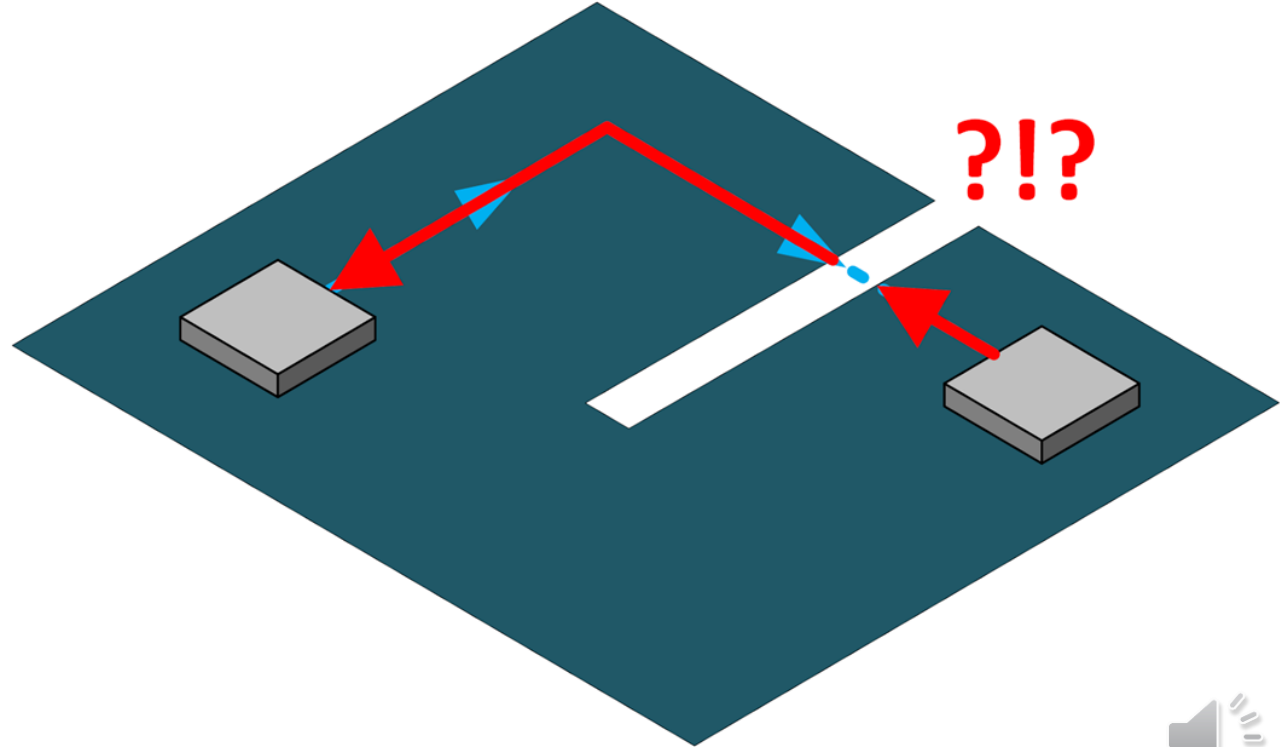


Implications of non ideal ground?

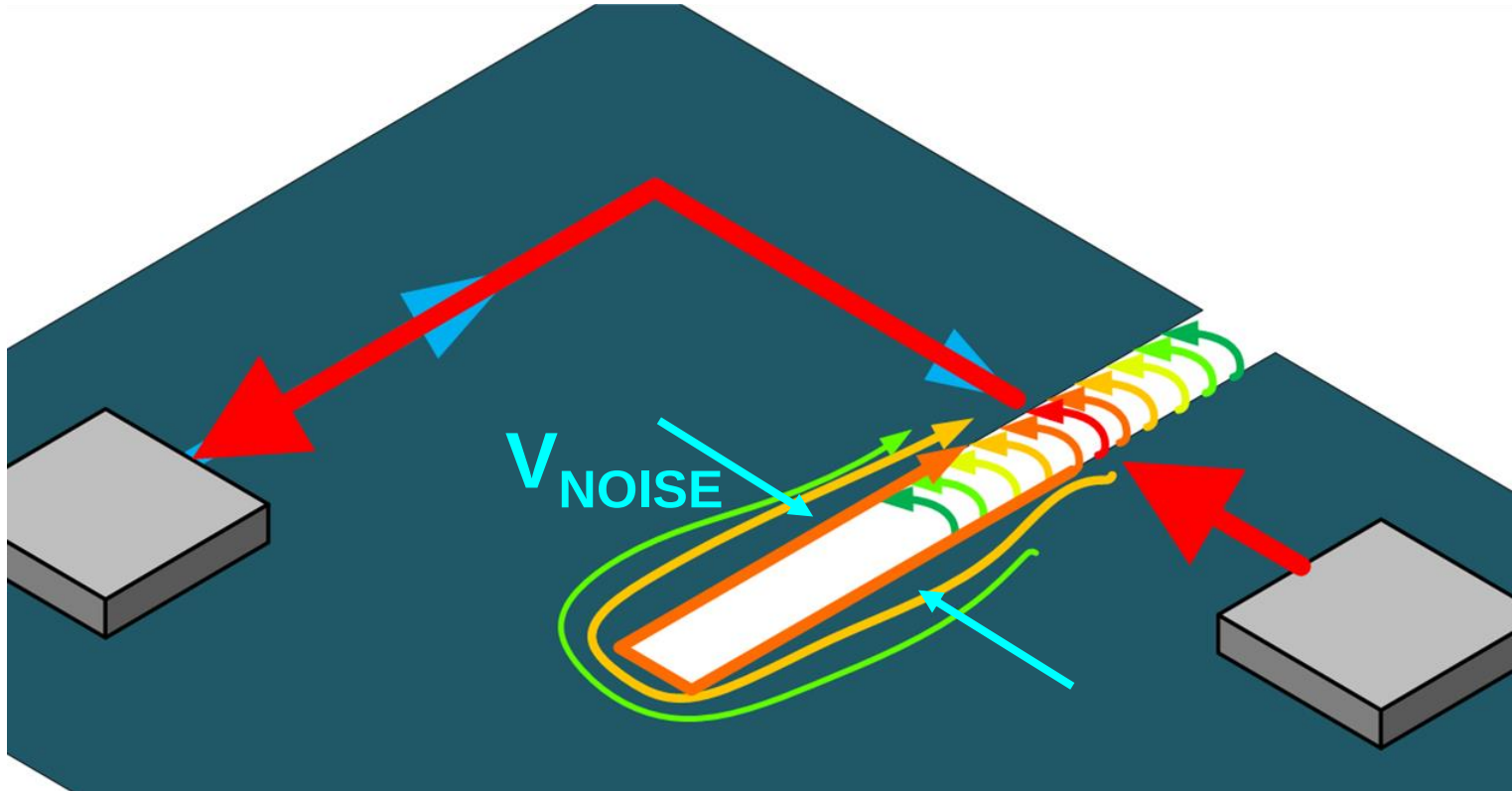


Implications of non ideal ground?

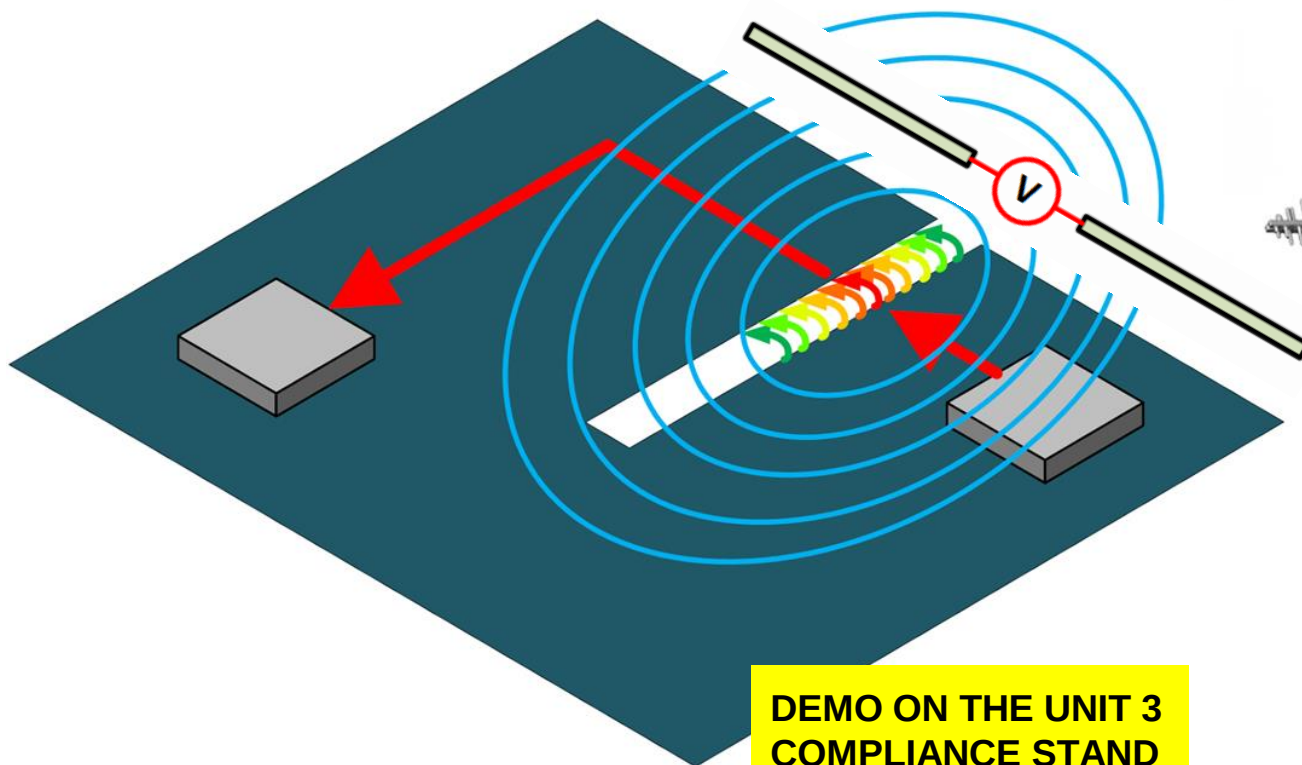



**DEMO ON THE UNIT 3
COMPLIANCE STAND**

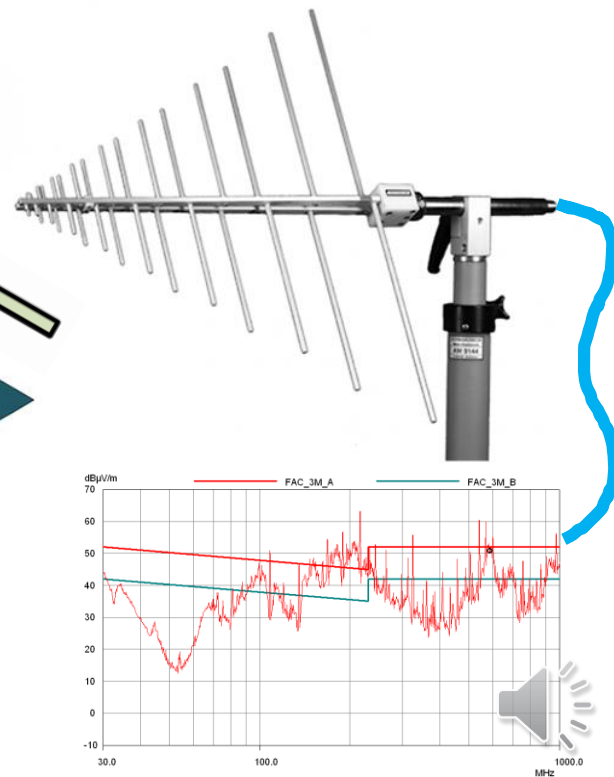


Remediation 1

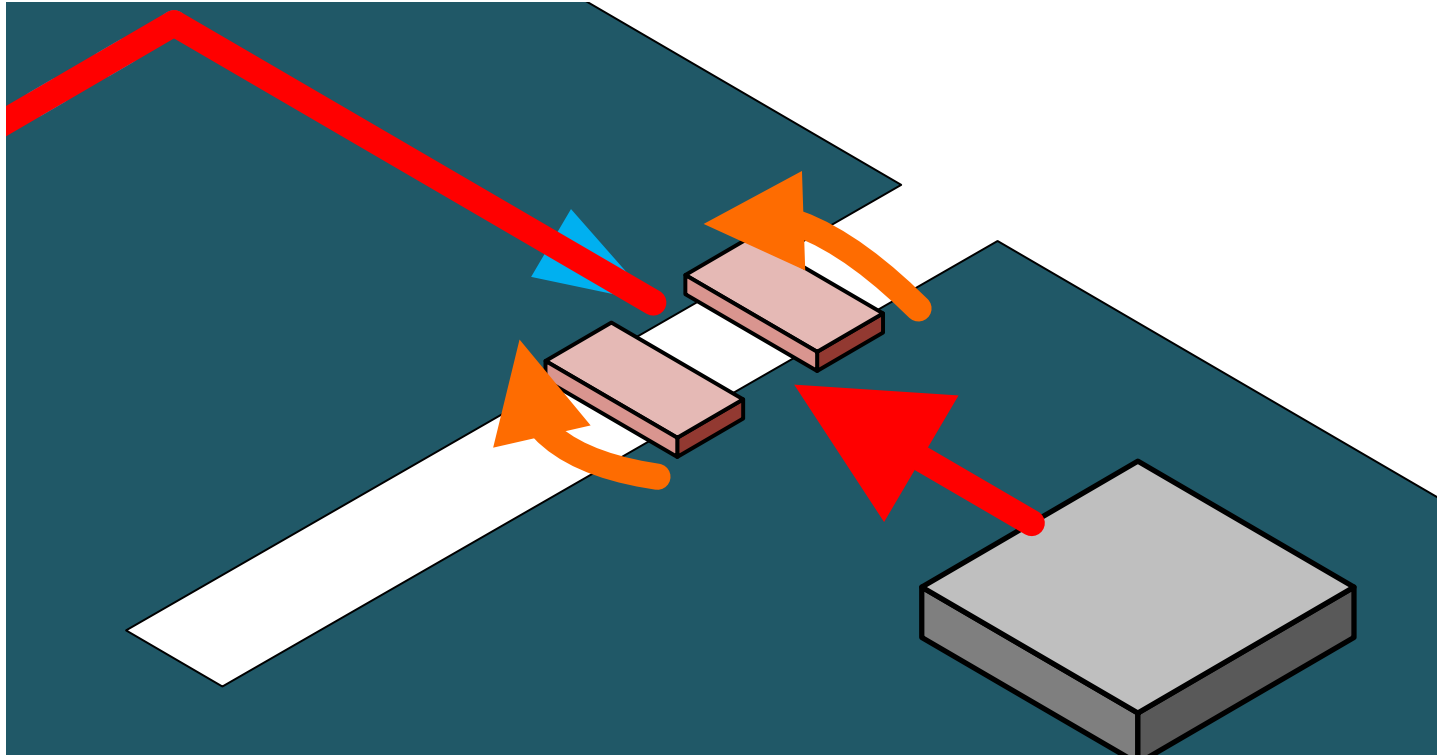

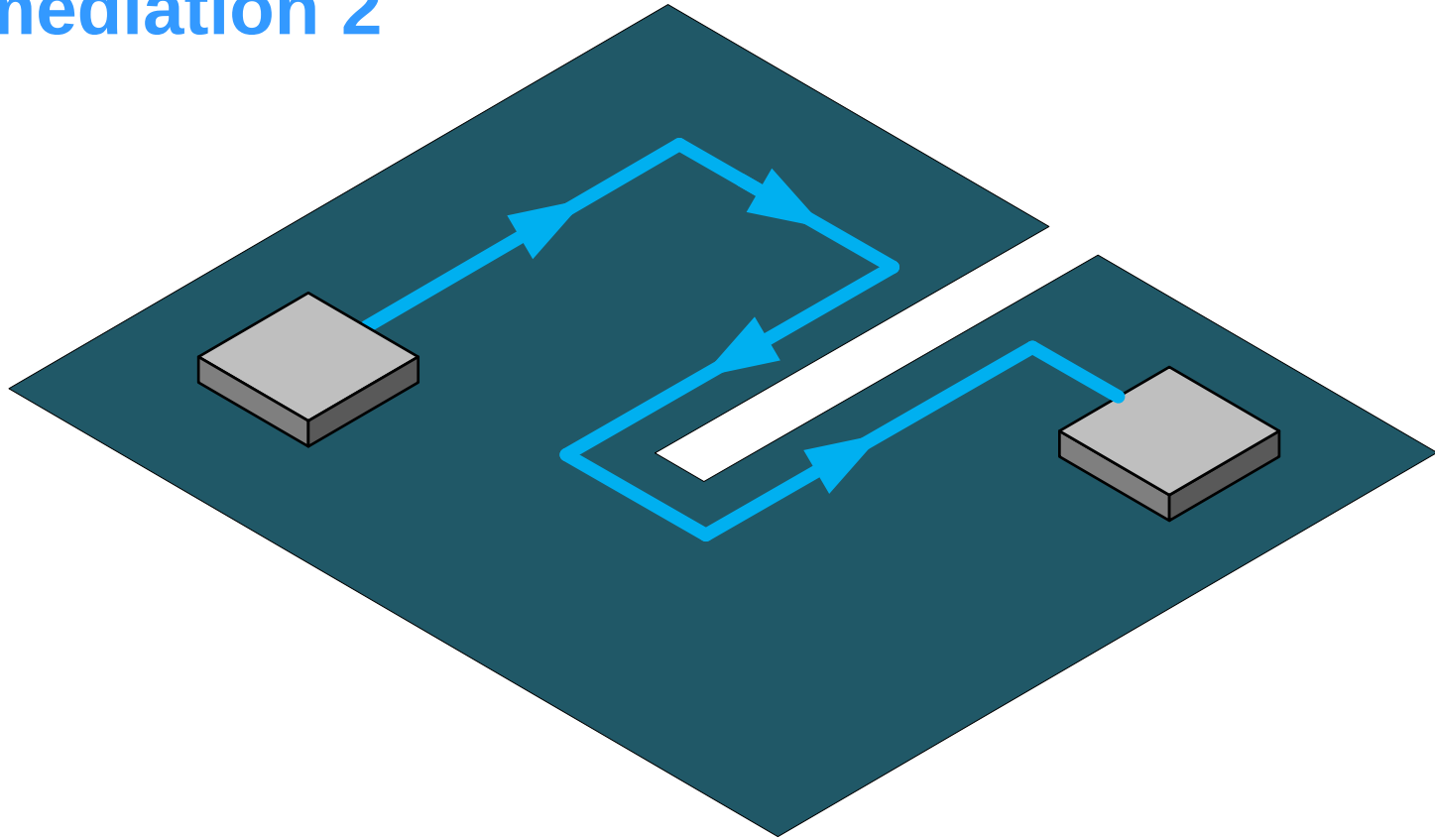


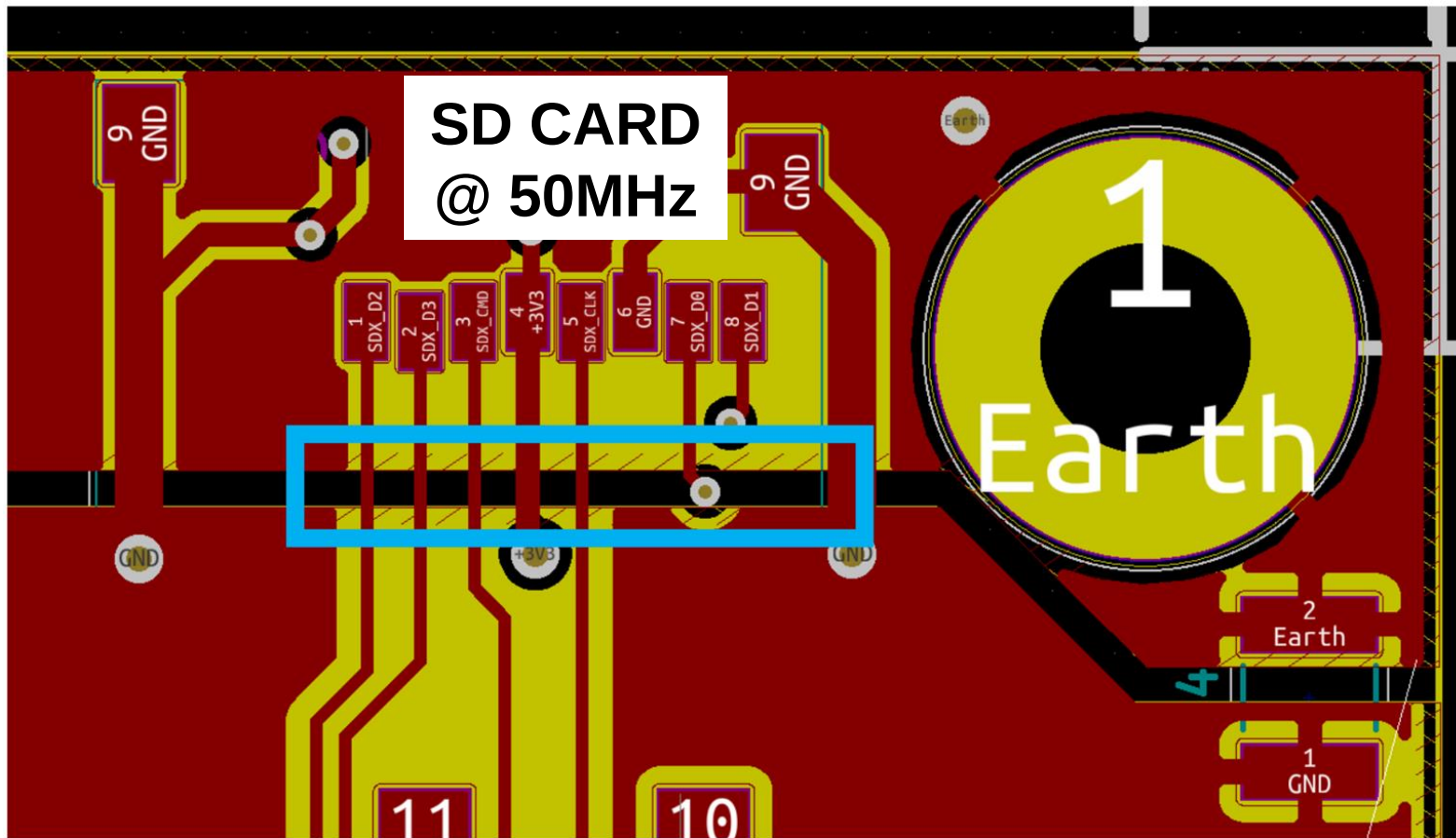


A good return for every signal

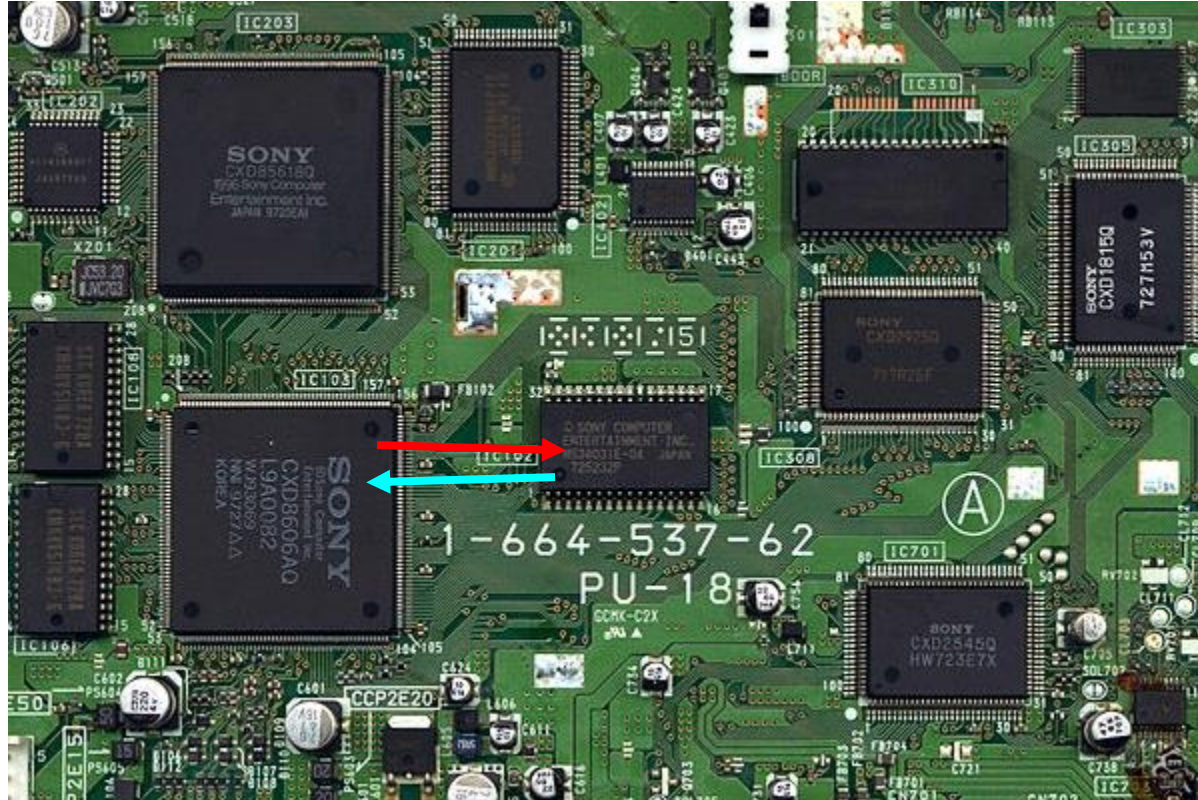

For every signal!

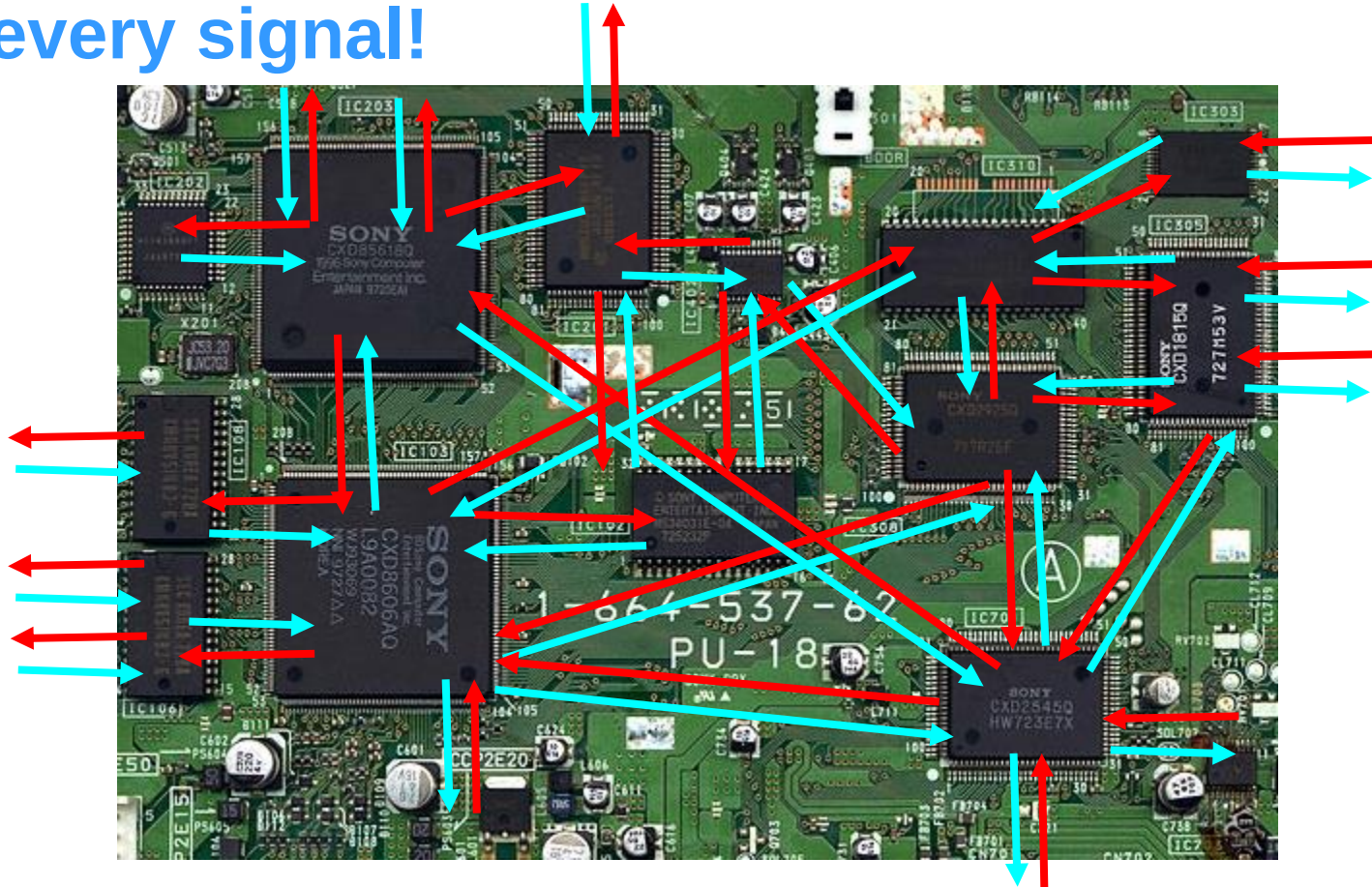

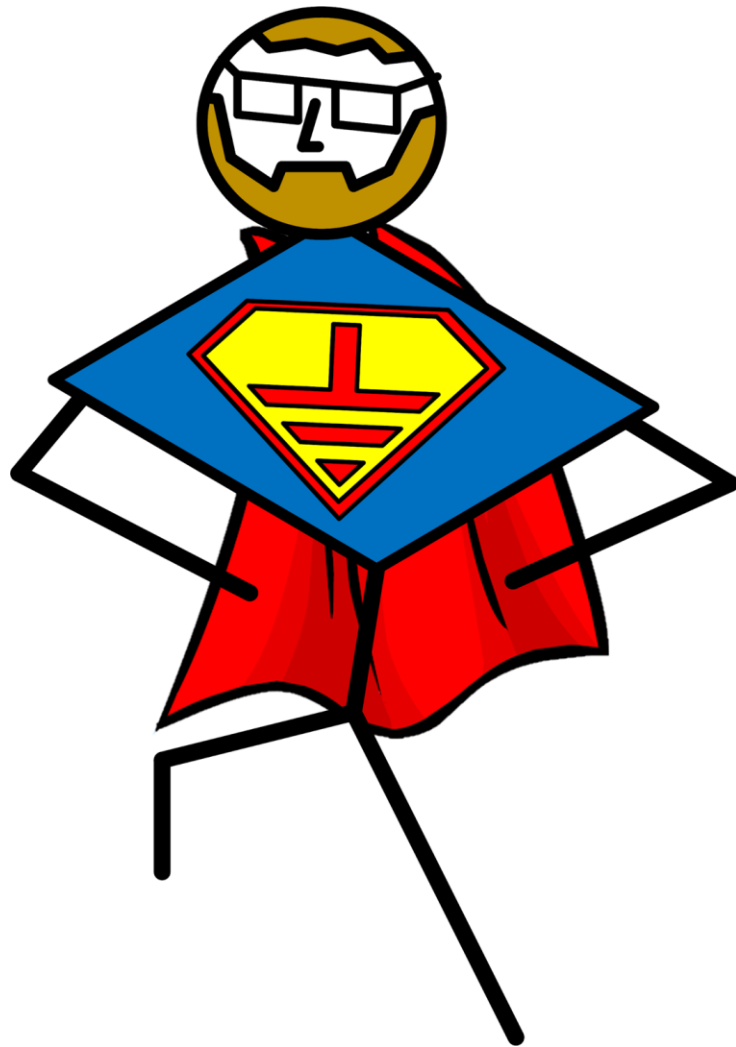



Time to bust some EMC myths

Grab your
safety beret




Let's blow up some
misconceptions





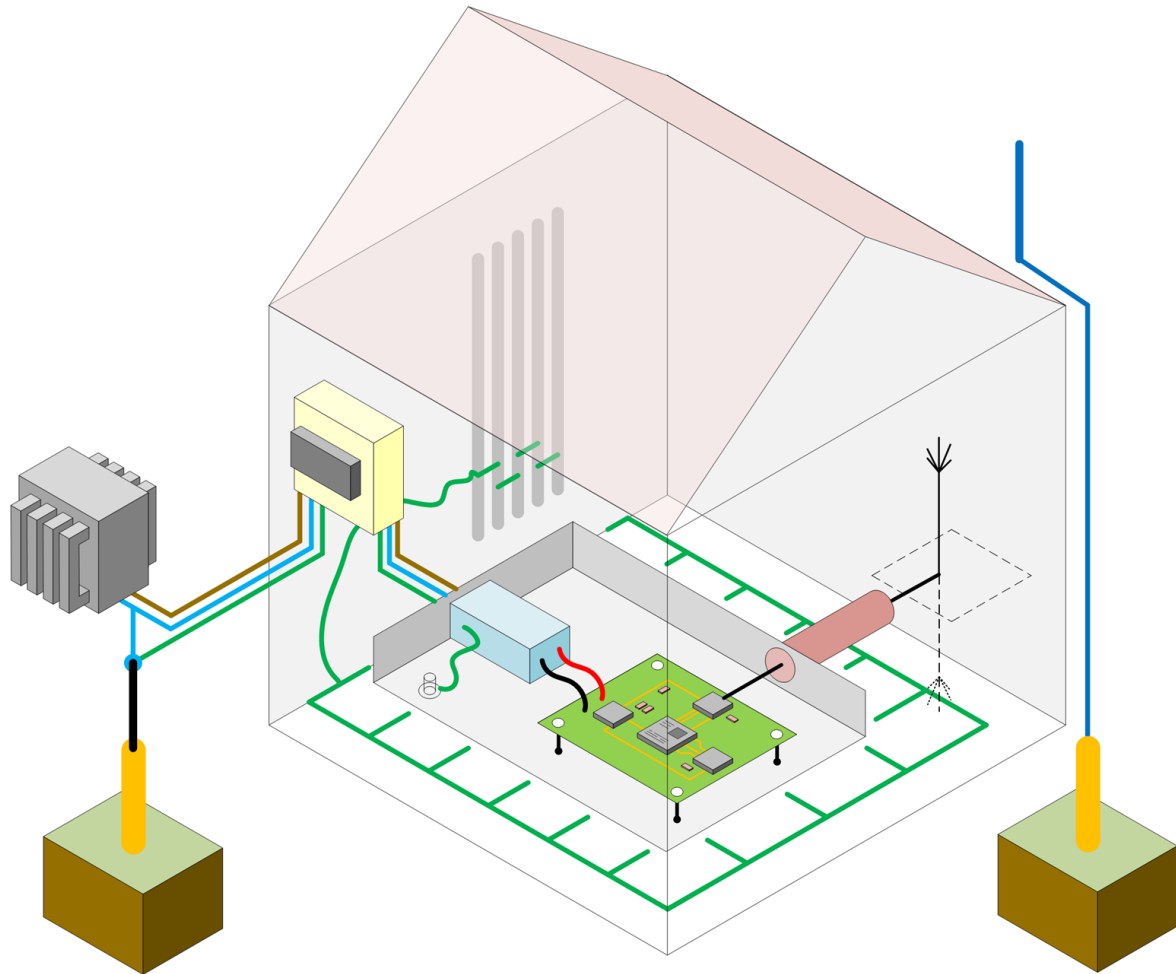**“Could we just connect it to a
quiet ground / to earth to see
what happens?”**






Where is this “quiet” ground?



Where is this “quiet” ground?

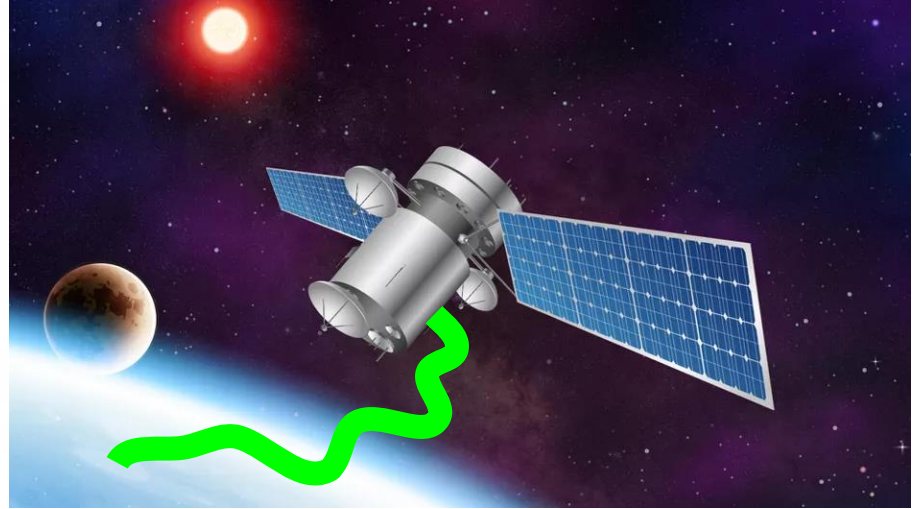





**“I’m trying to avoid creating a
ground loop”**




Ground Loop

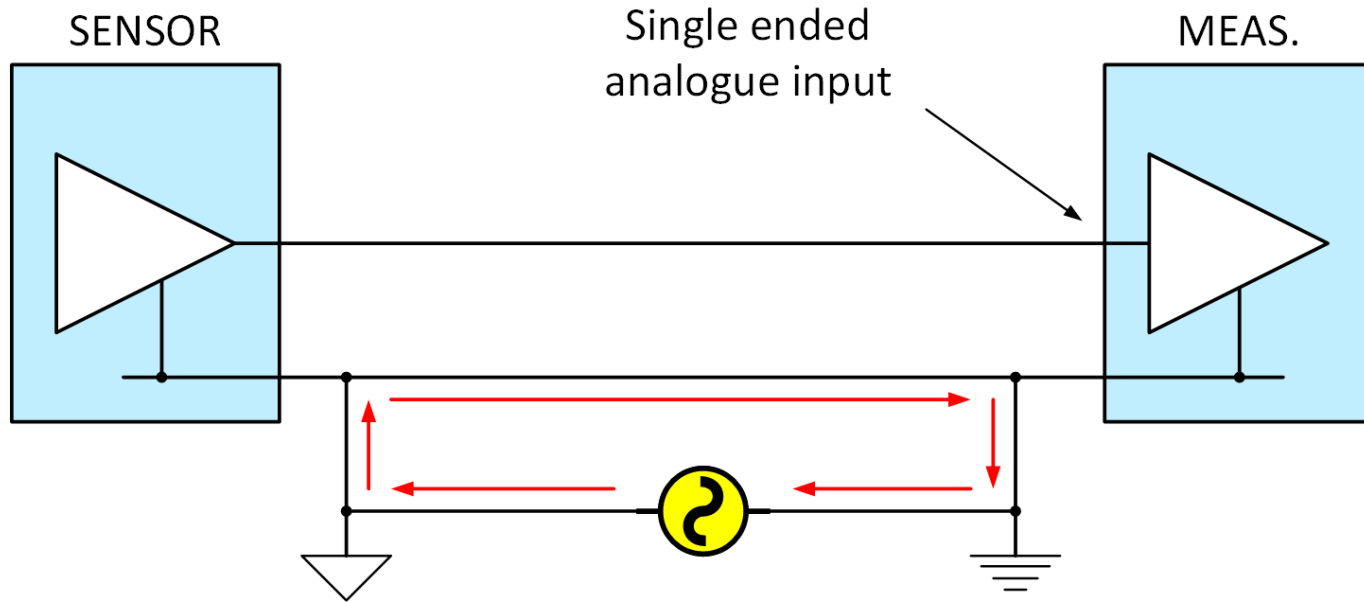


Typical LF Ground Loop

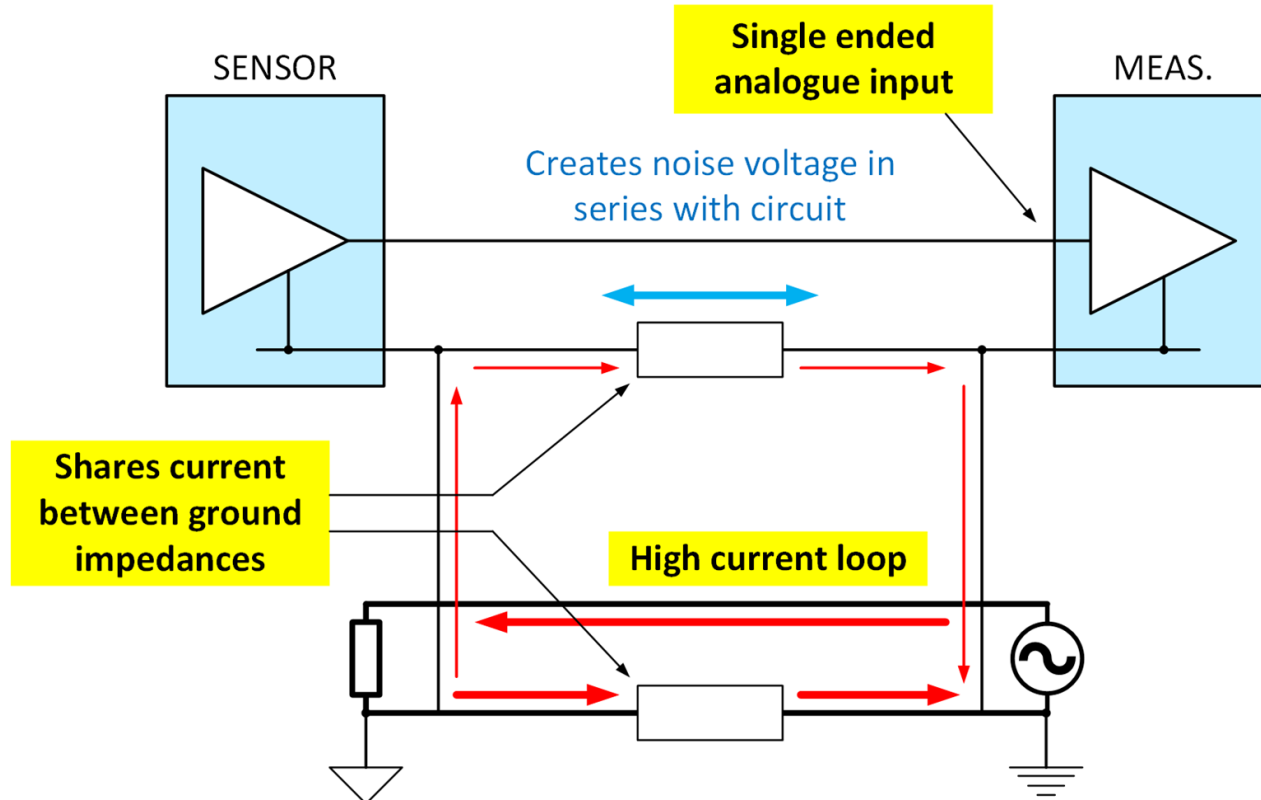


HF Ground Loop = Insignificant

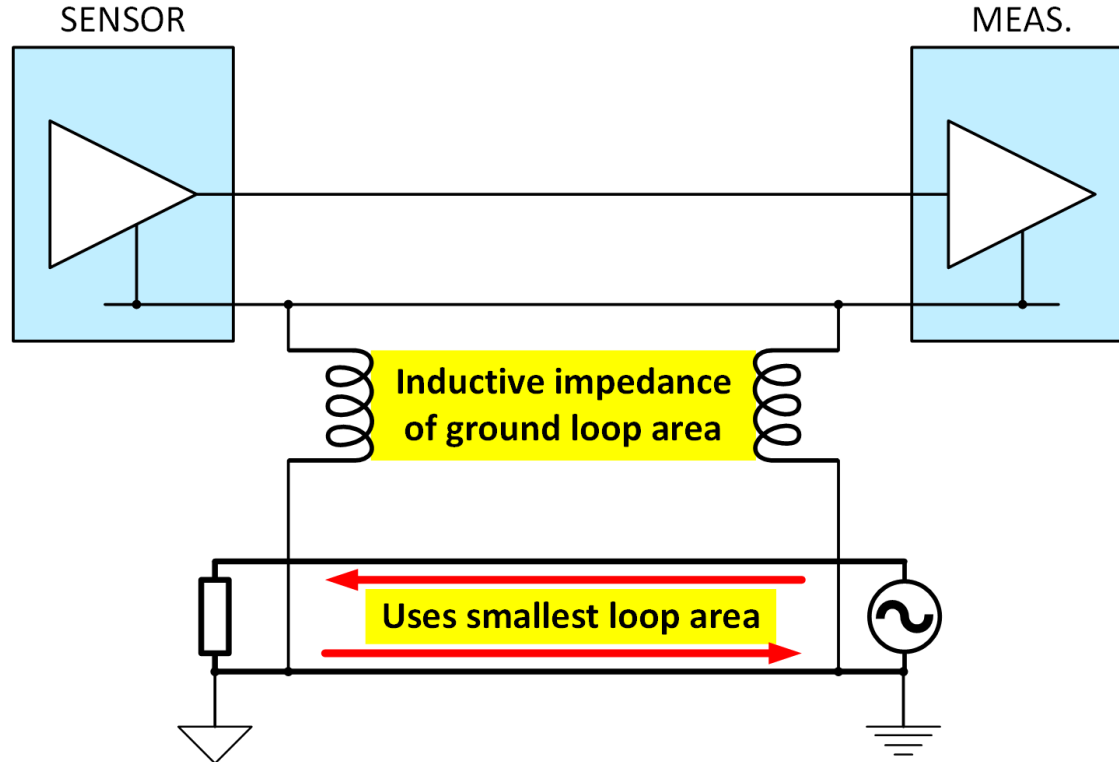

Fixing LF Ground Loops

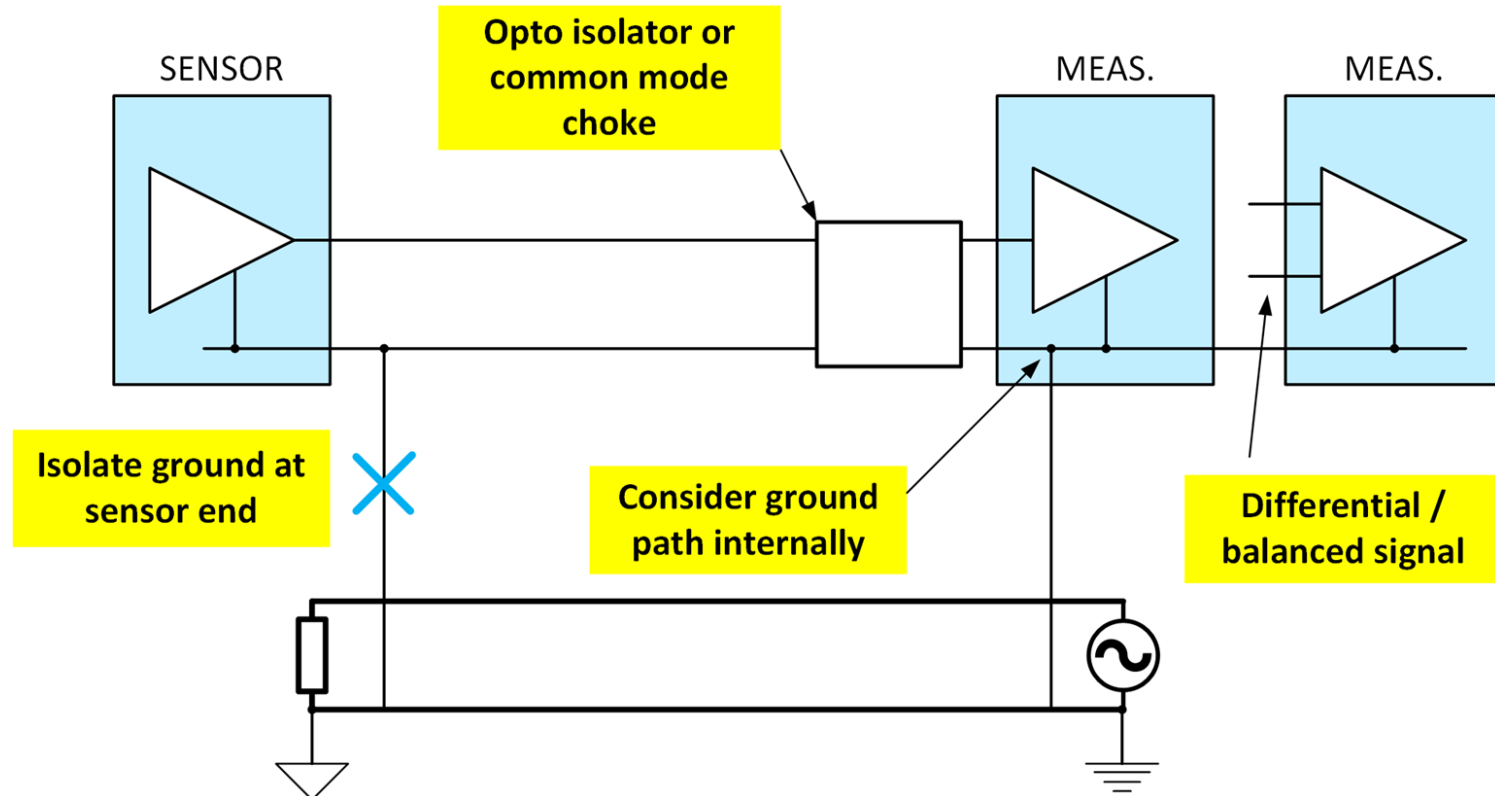

When “Ground Loops” Bite

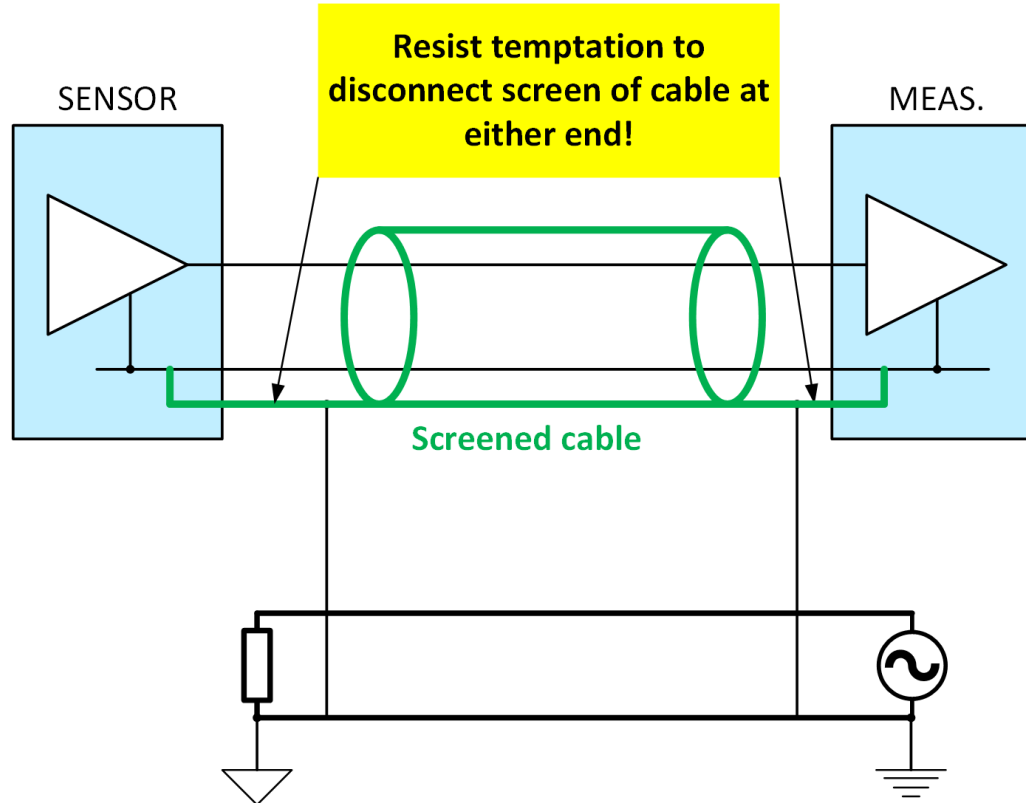





**“I’ve put a capacitor / ferrite
bead / resistor in series with my
cable shield”**




USB cable wiring




SHIELD
no connection
at USB device

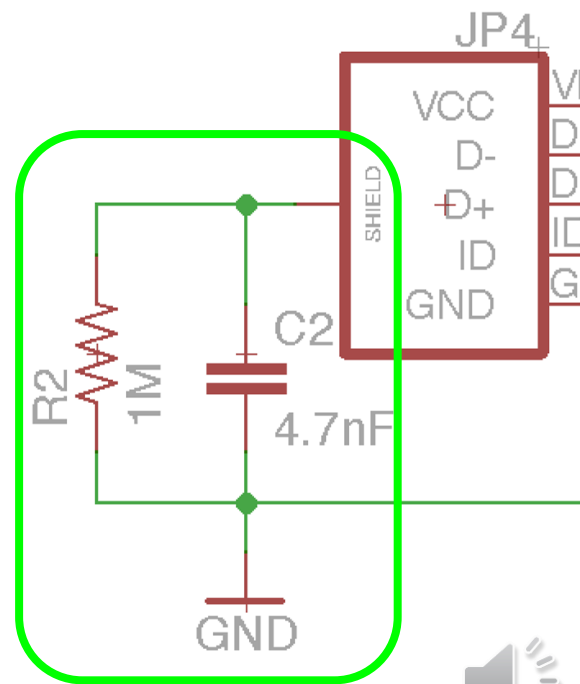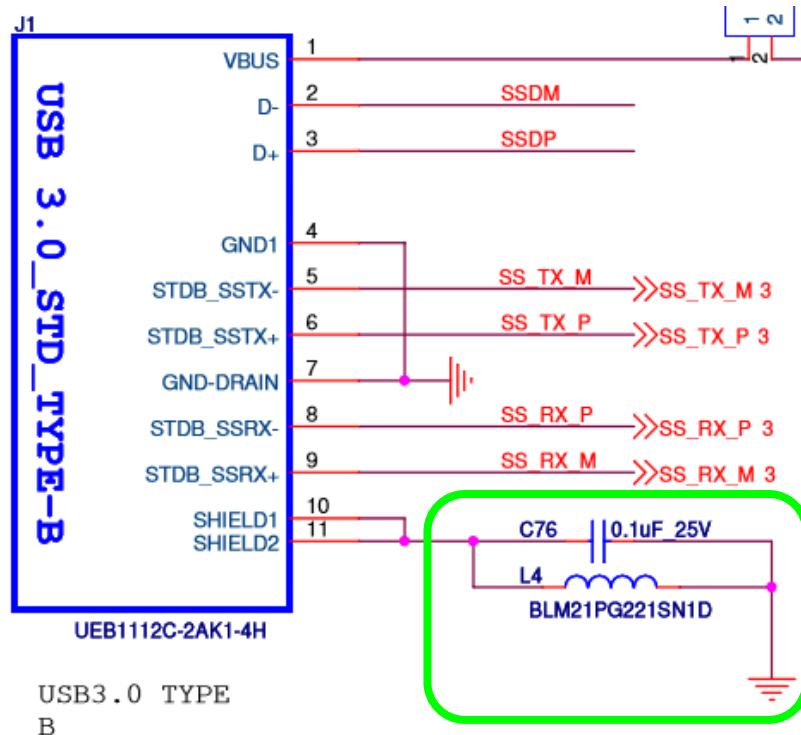


Cable Shield Ground Currents

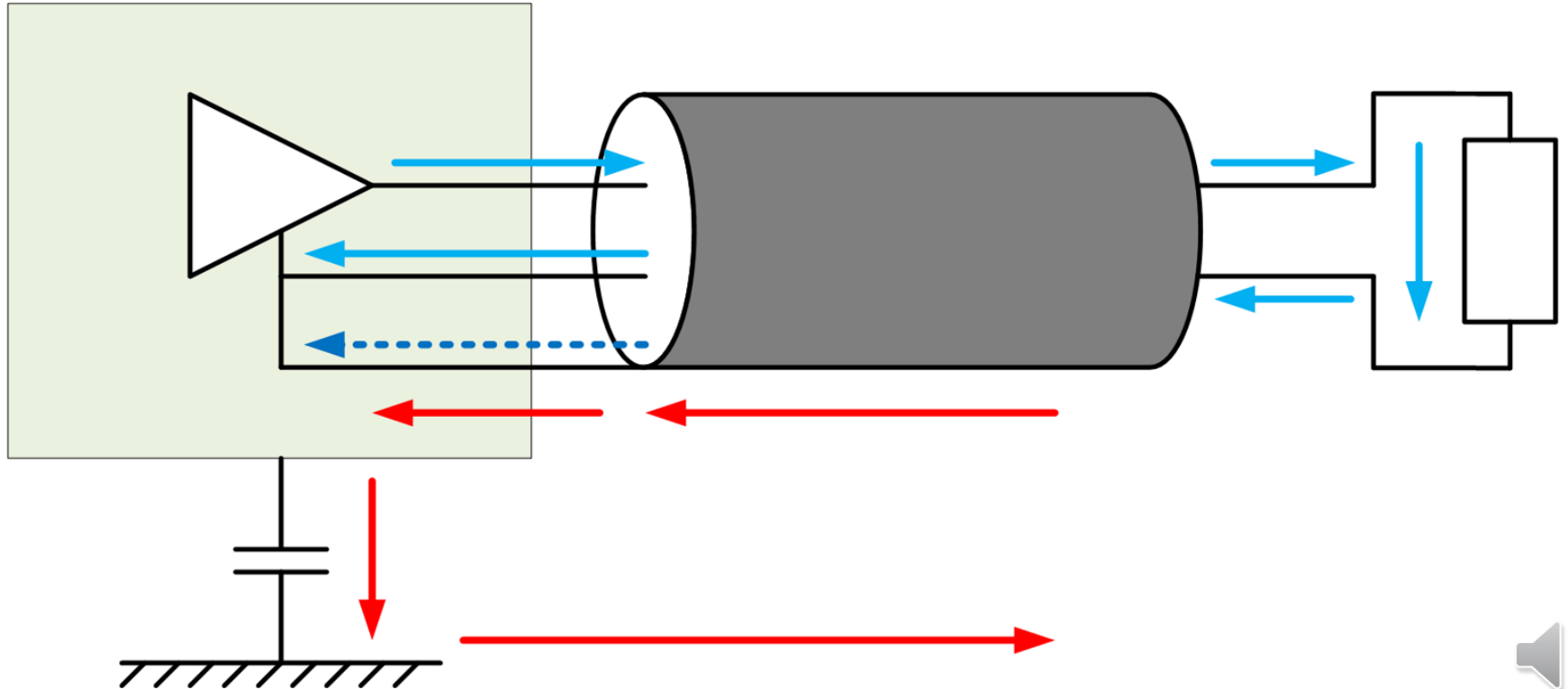

Additional Impedance

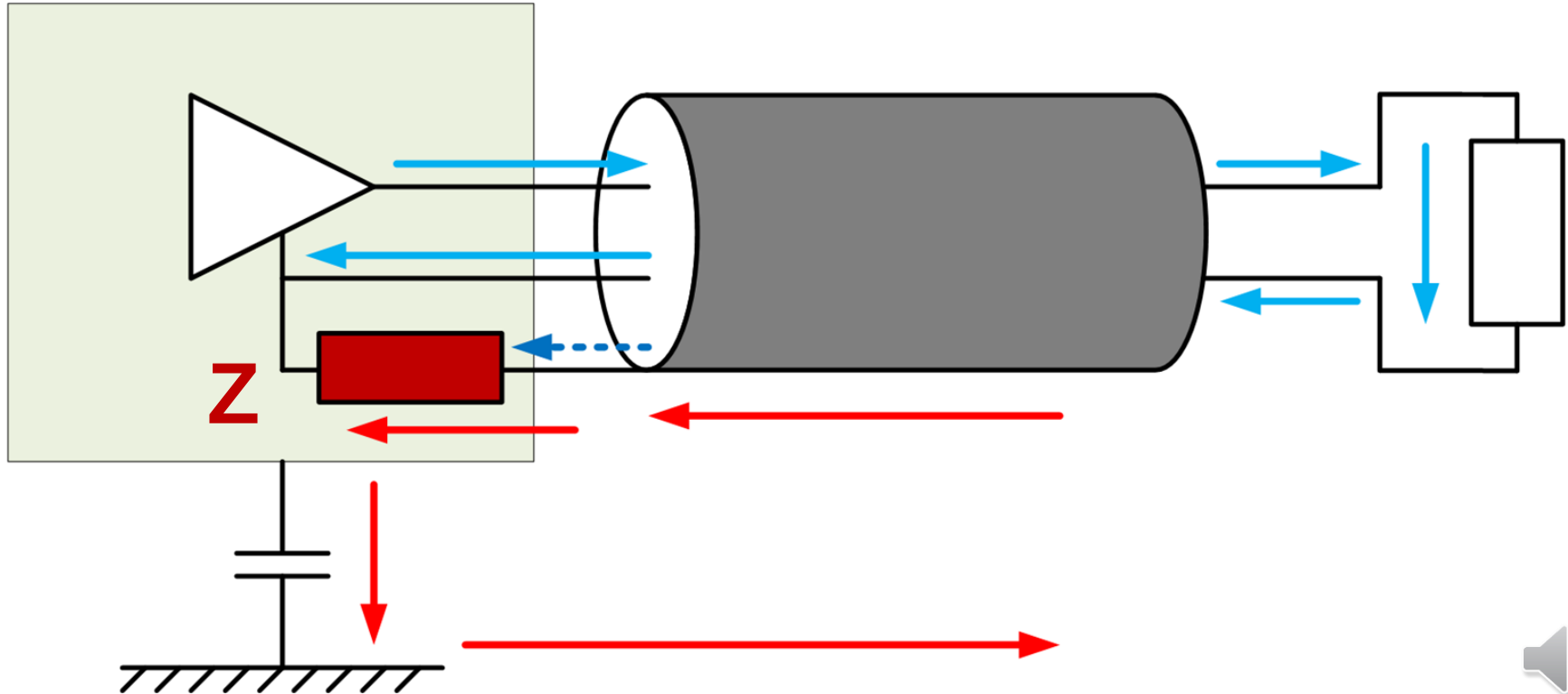

Bad For Emissions

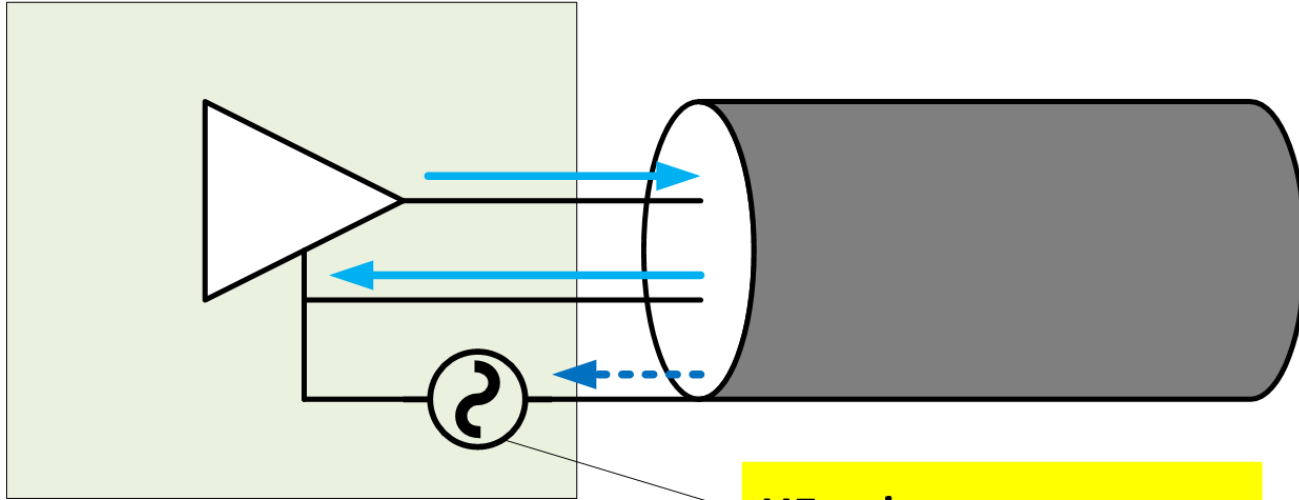

= dipole antenna


**HF voltage appears on
shield of cable =
radiated emissions**



Bad For Immunity



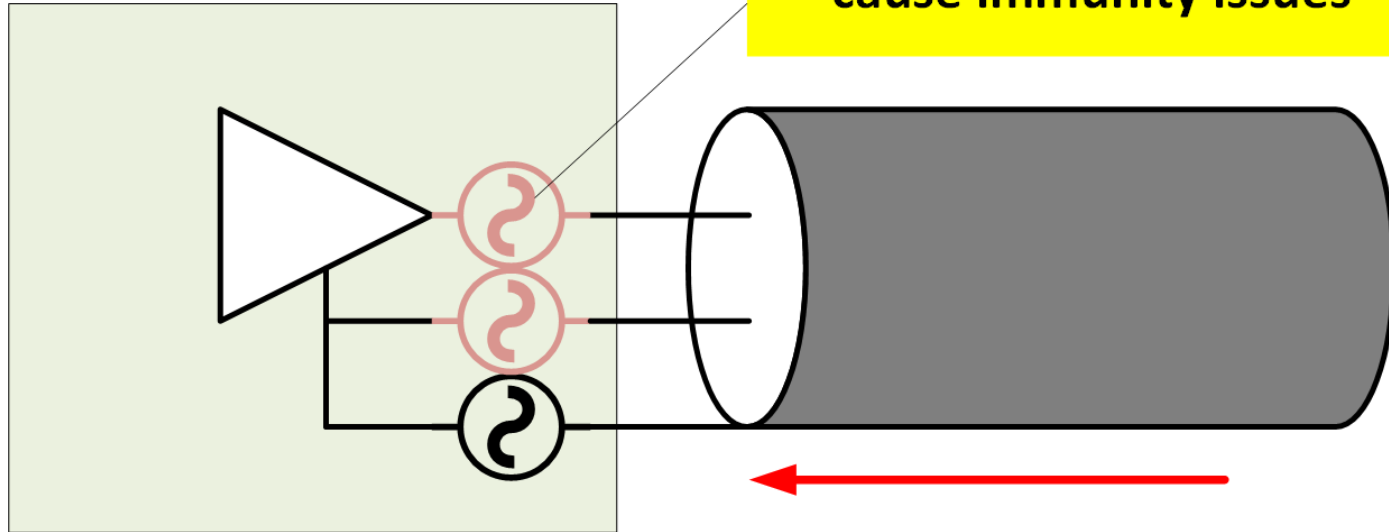Generated voltage can appear common mode and cause immunity issues






**“I’ve only connected the cable
shield at one end.”**



Which end to connect the shield?

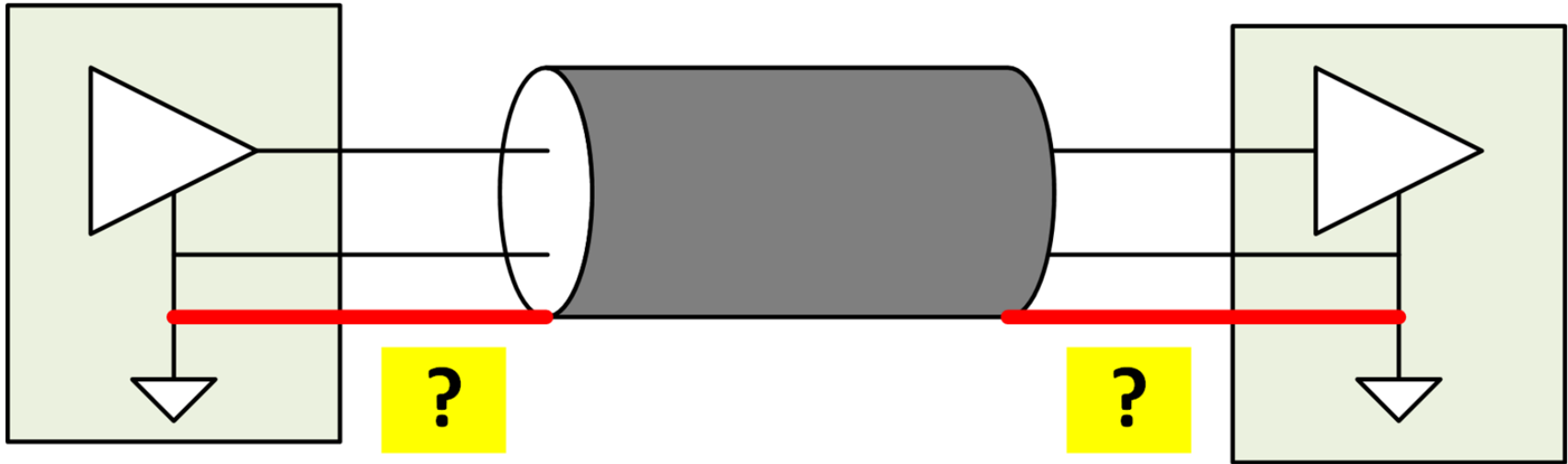

Ans: both







**“The mounting holes are
floating and not connected to
the ground plane”**




Metal Chassis Mounting Hole Currents

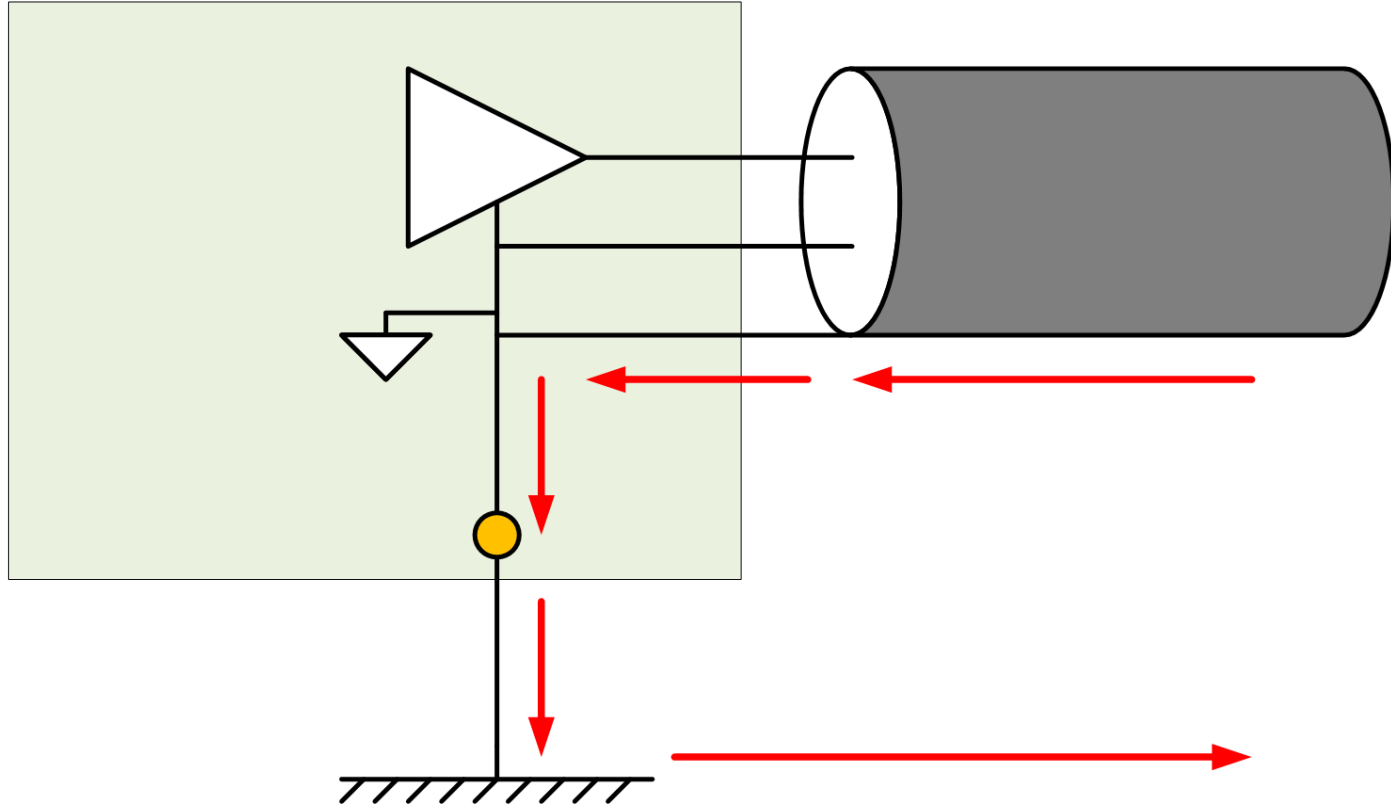


Removed Direct Connection

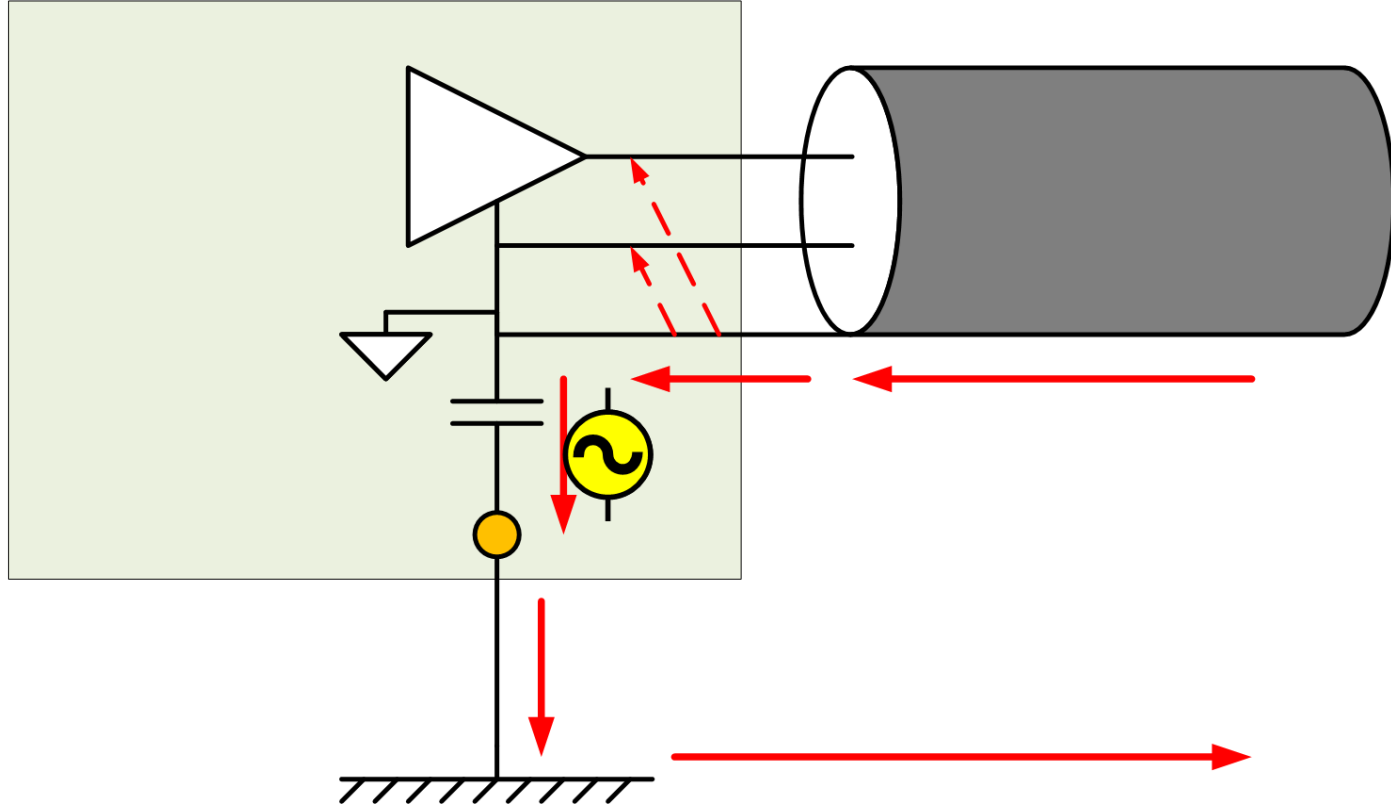


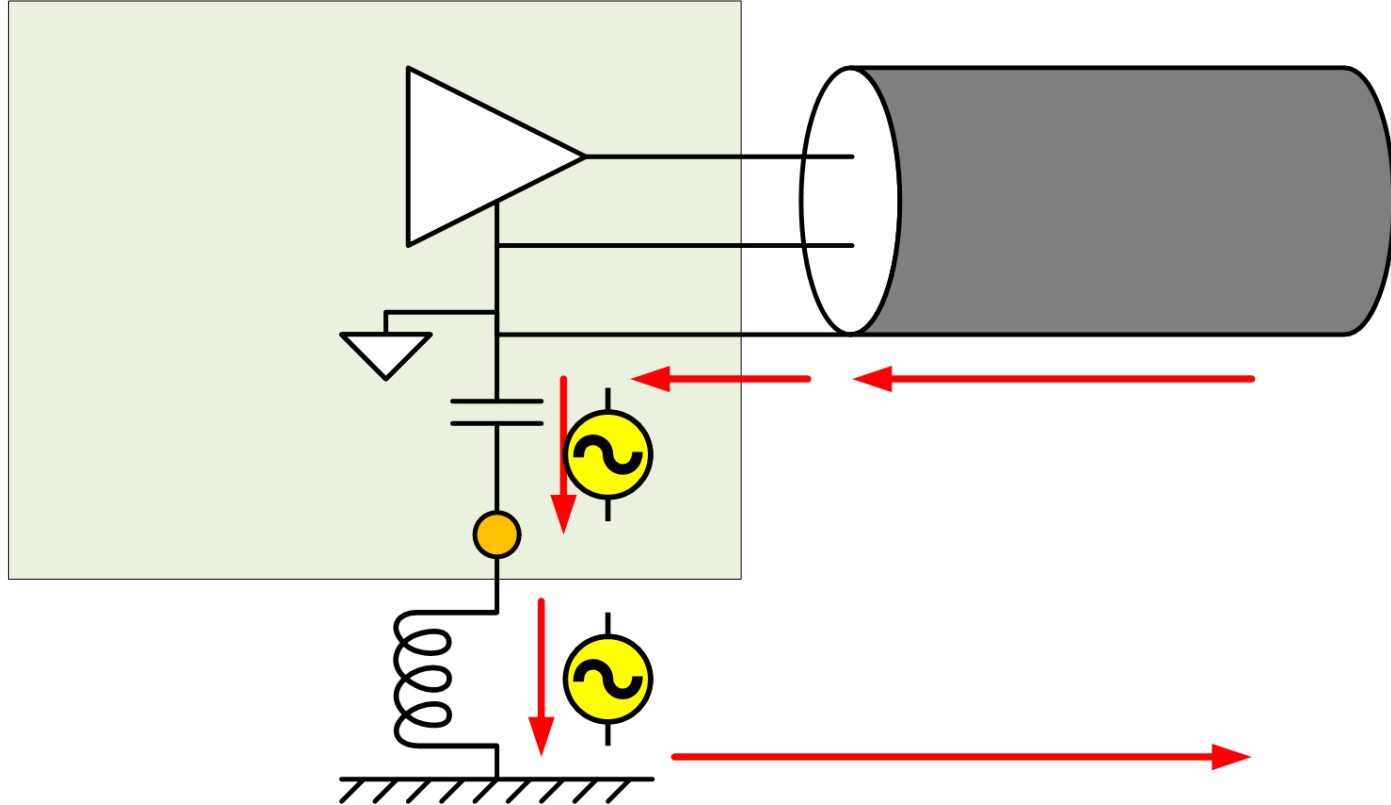


Importance of Connecting Cable Shield

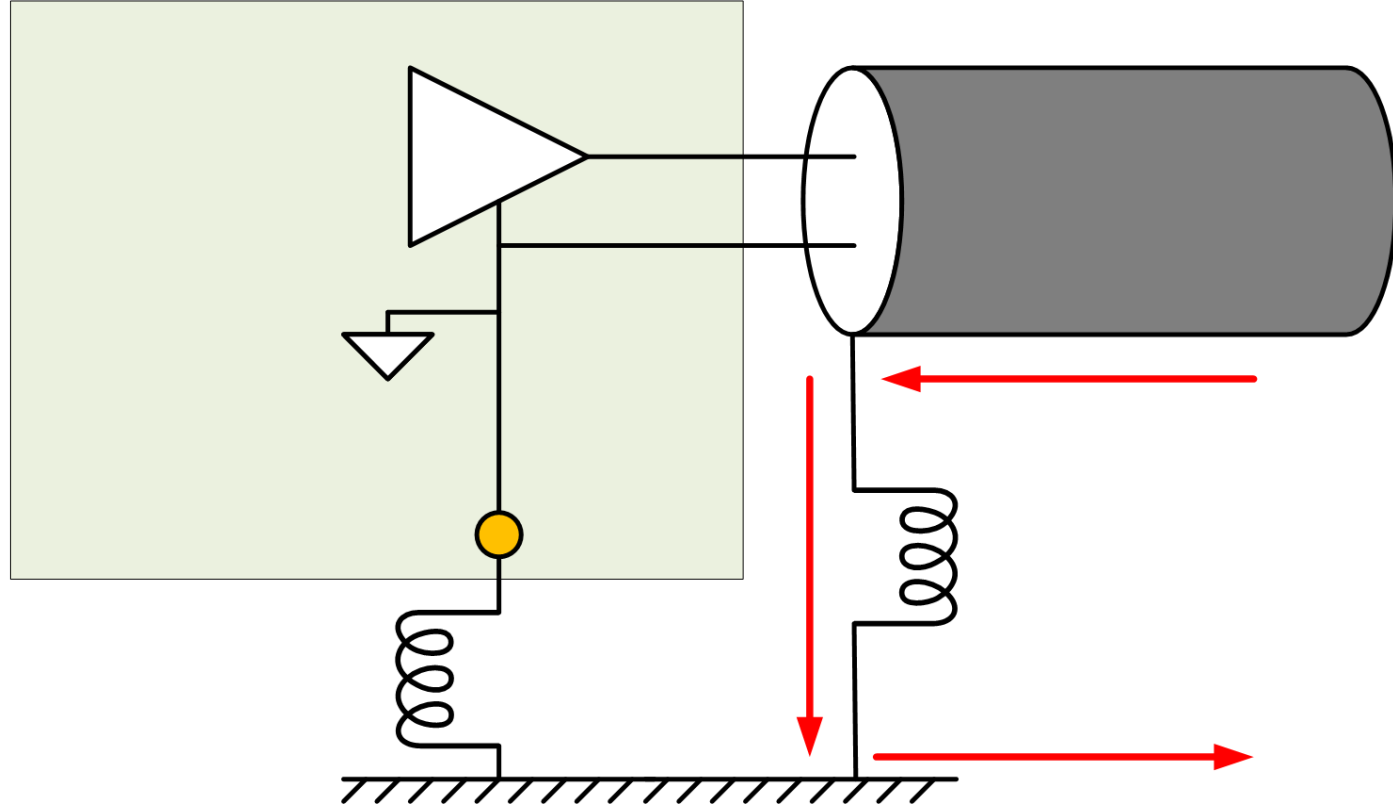



Location of Mounting Hole

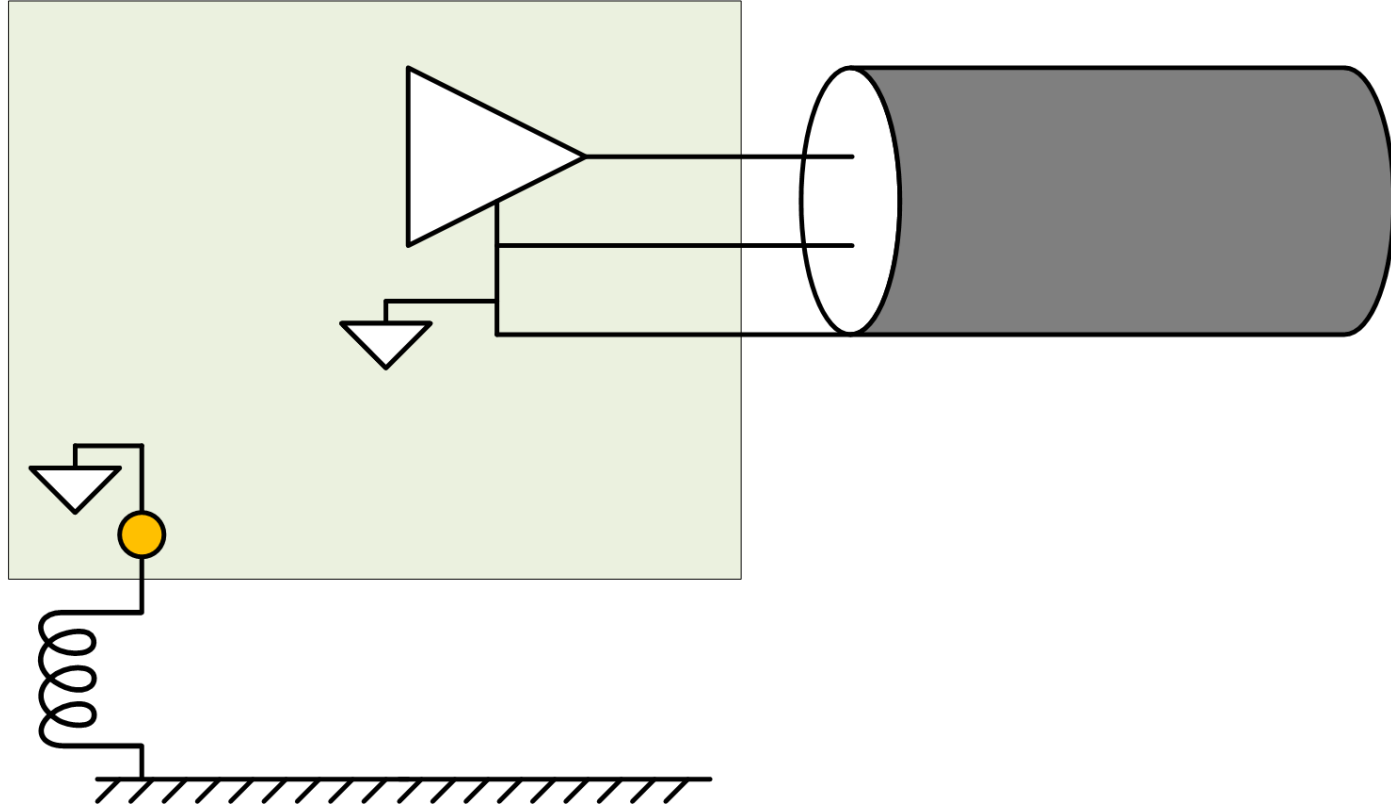


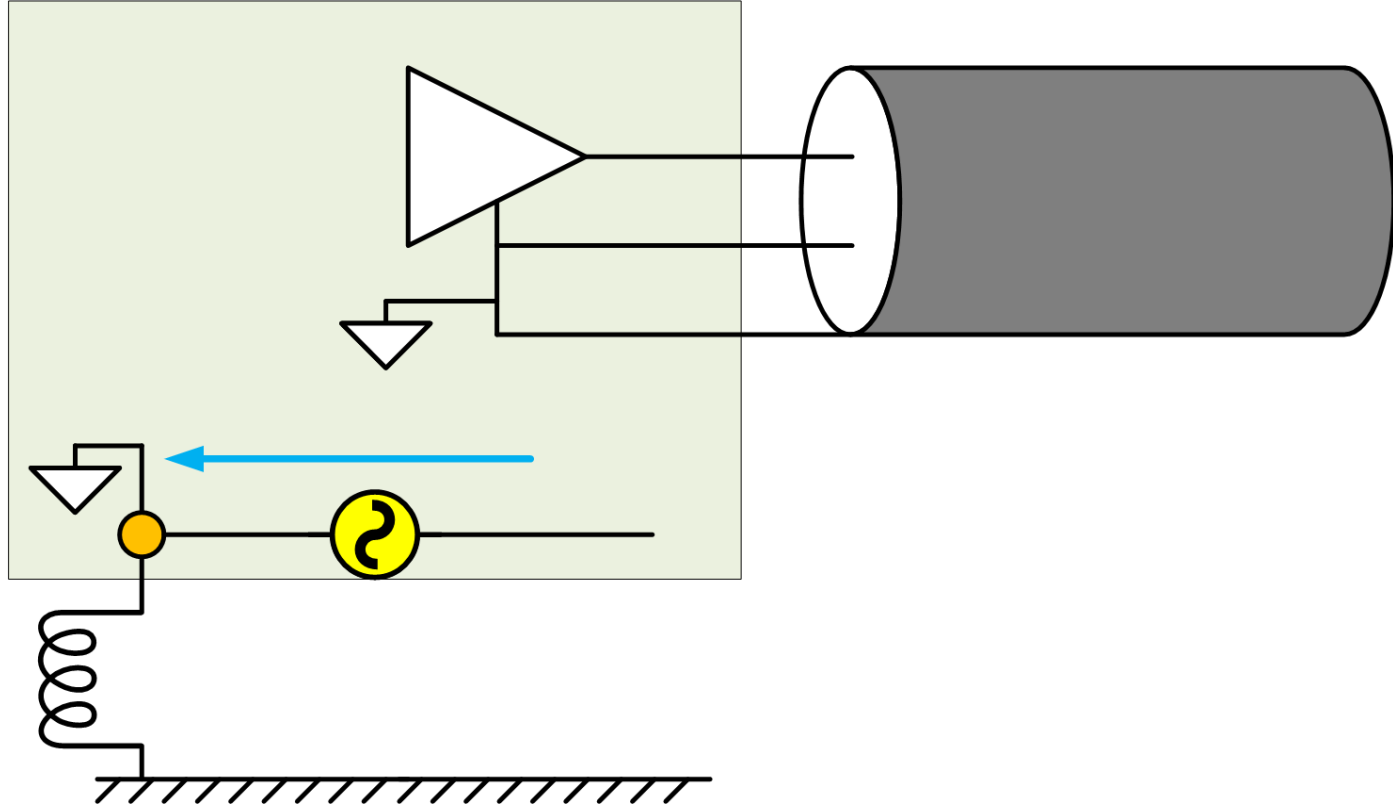

Location of Mounting Hole

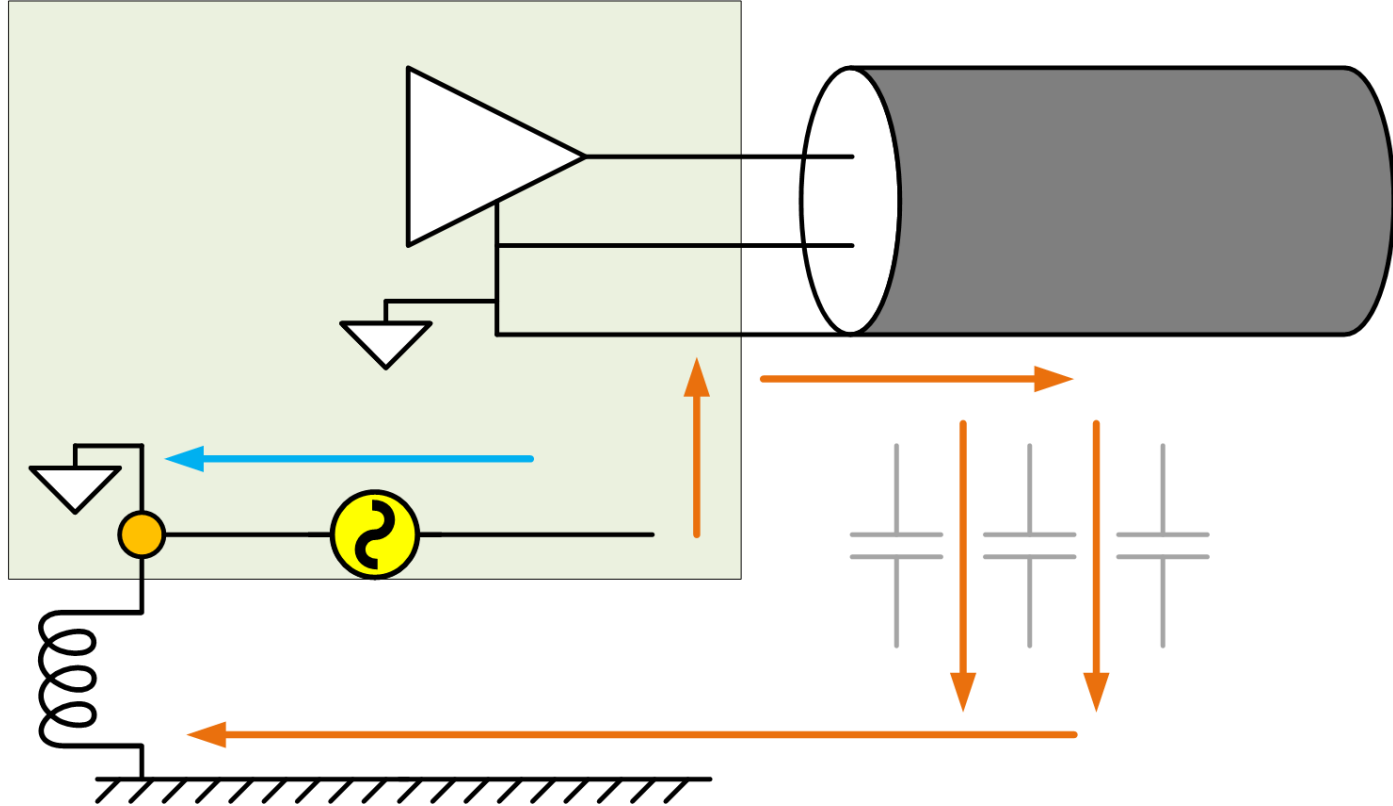

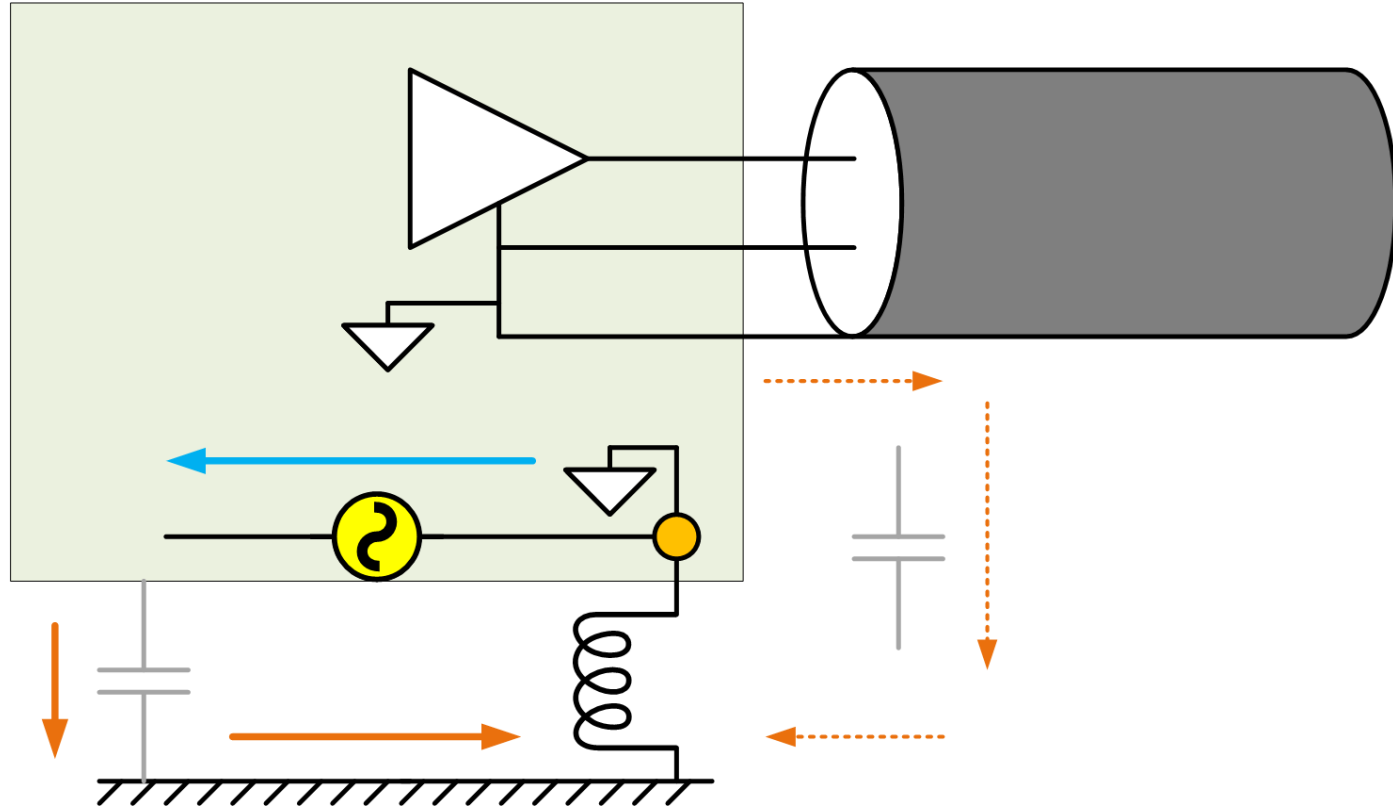

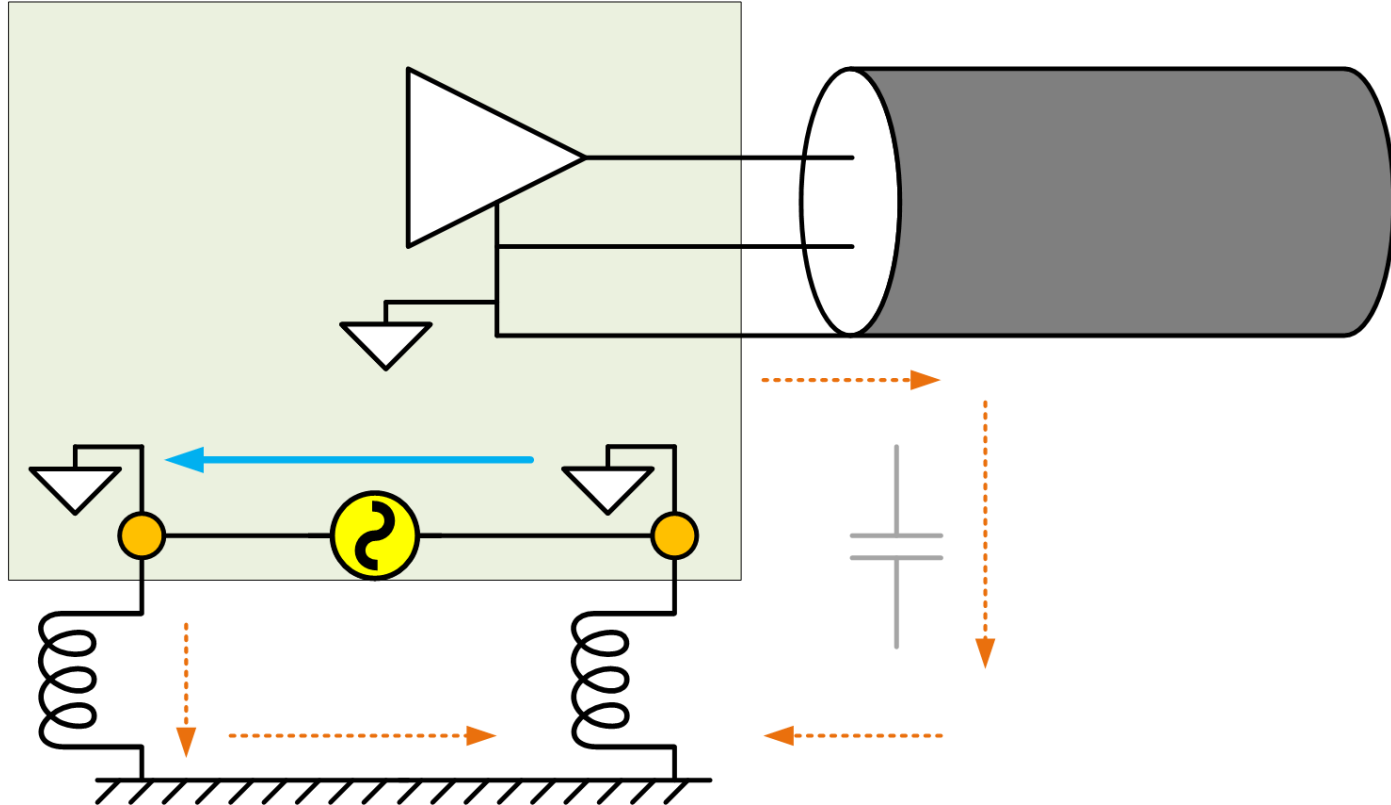




**“I need to provide a separate
analogue ground plane”**




Separate grounds on IC datasheets

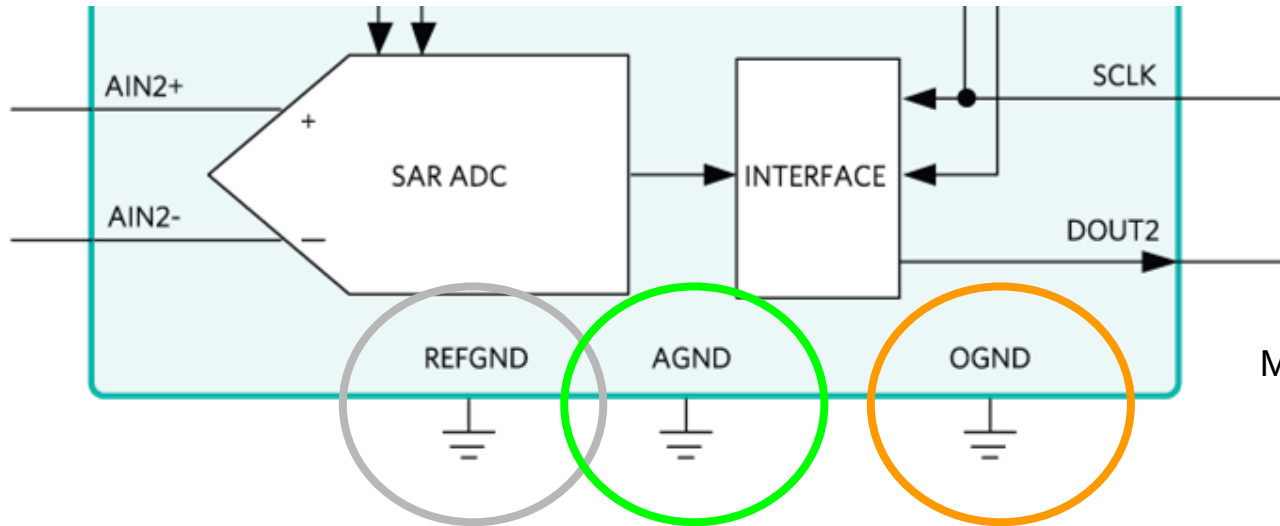

MAX11192




Separate grounds on IC datasheets

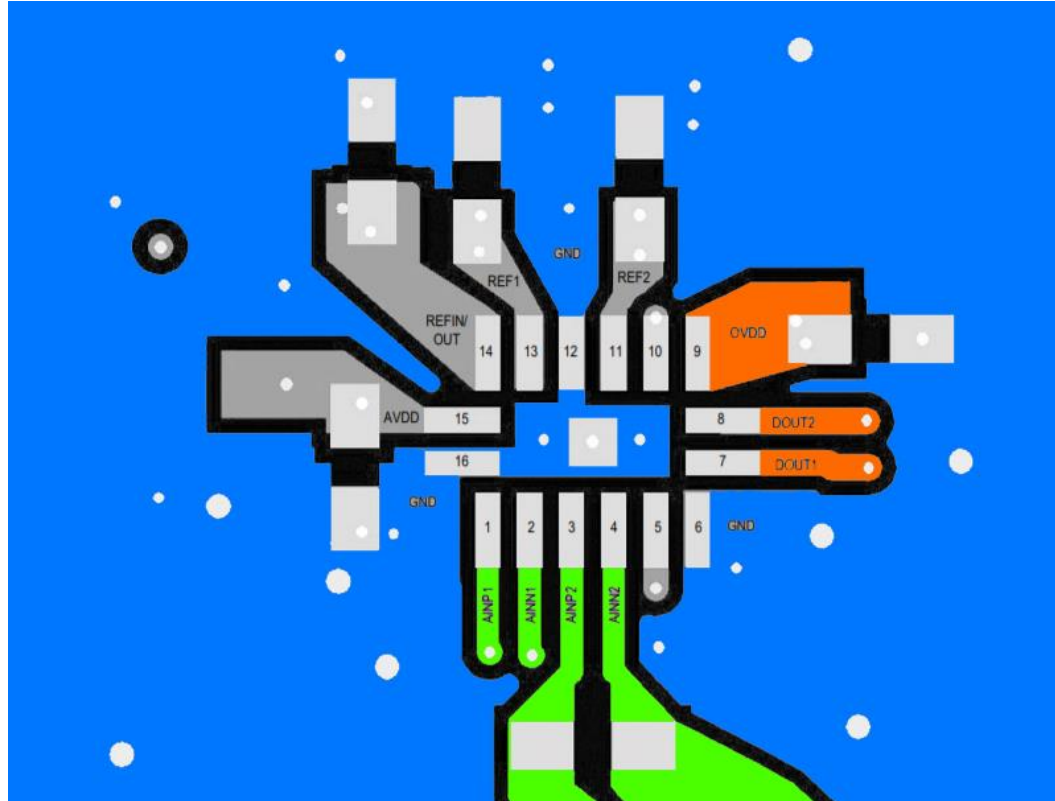

MAX11192




Different analogue and digital grounds?

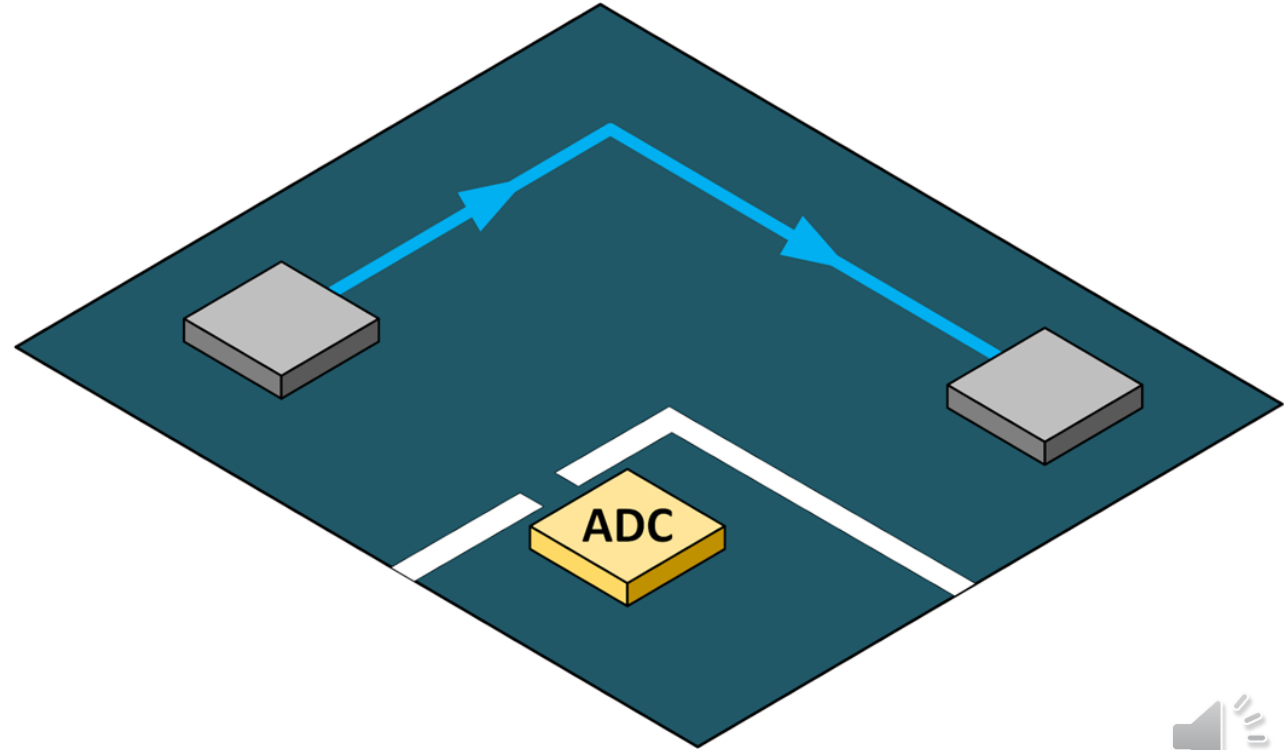

Different analogue and digital grounds?




5 MHz

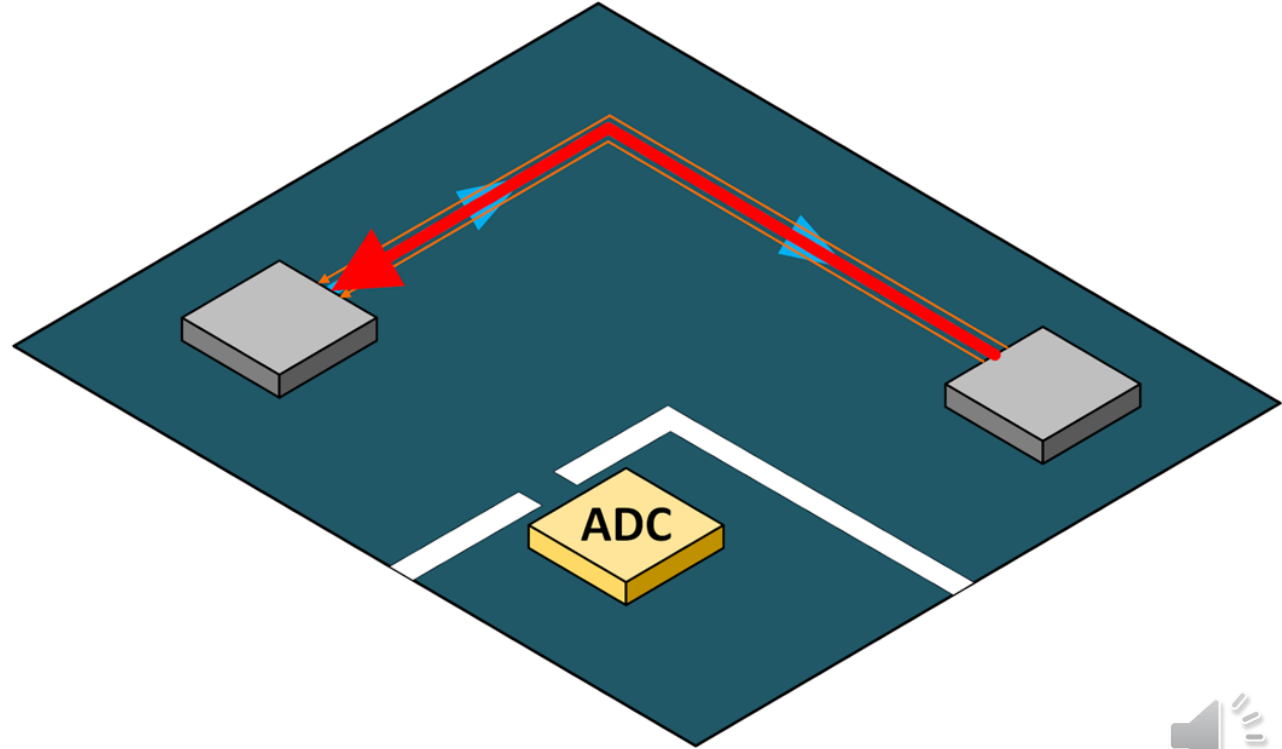

Different analogue and digital grounds?




5 kHz

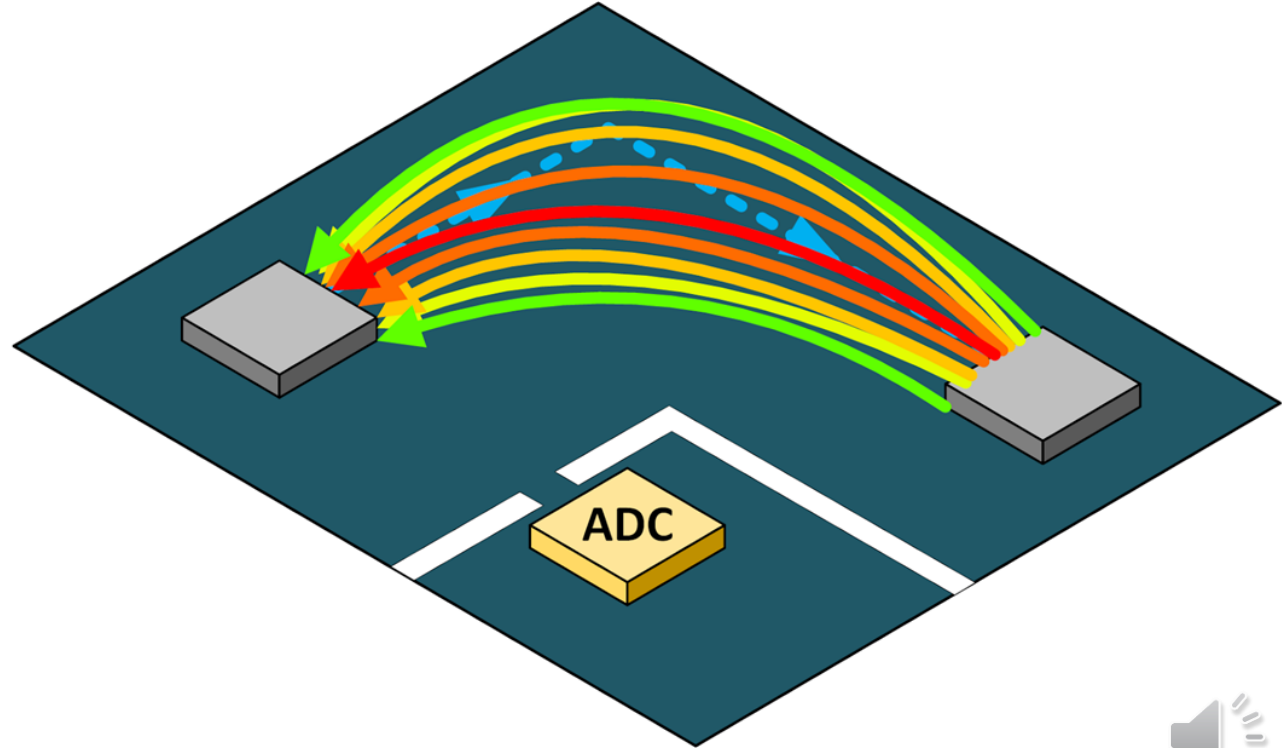

Different analogue and digital grounds?



500 Hz

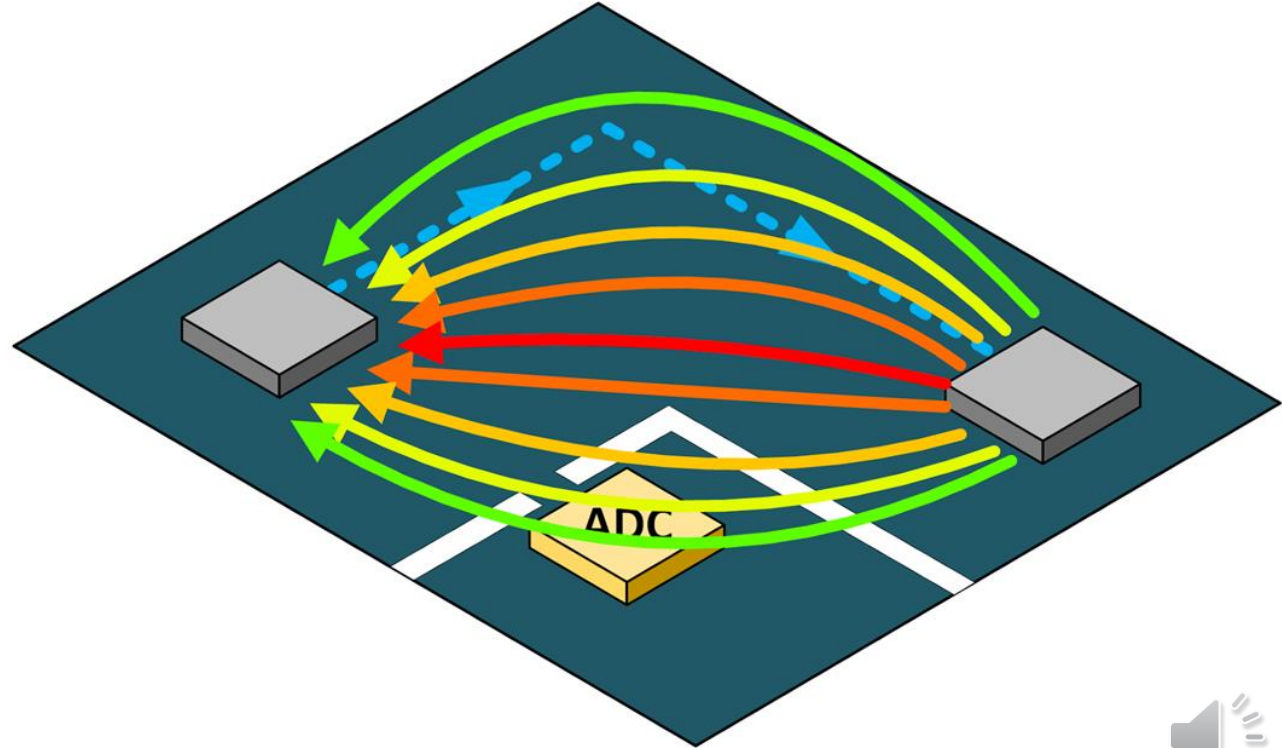





**This is a system design
problem, not an EMC problem.**




Design Partitioning

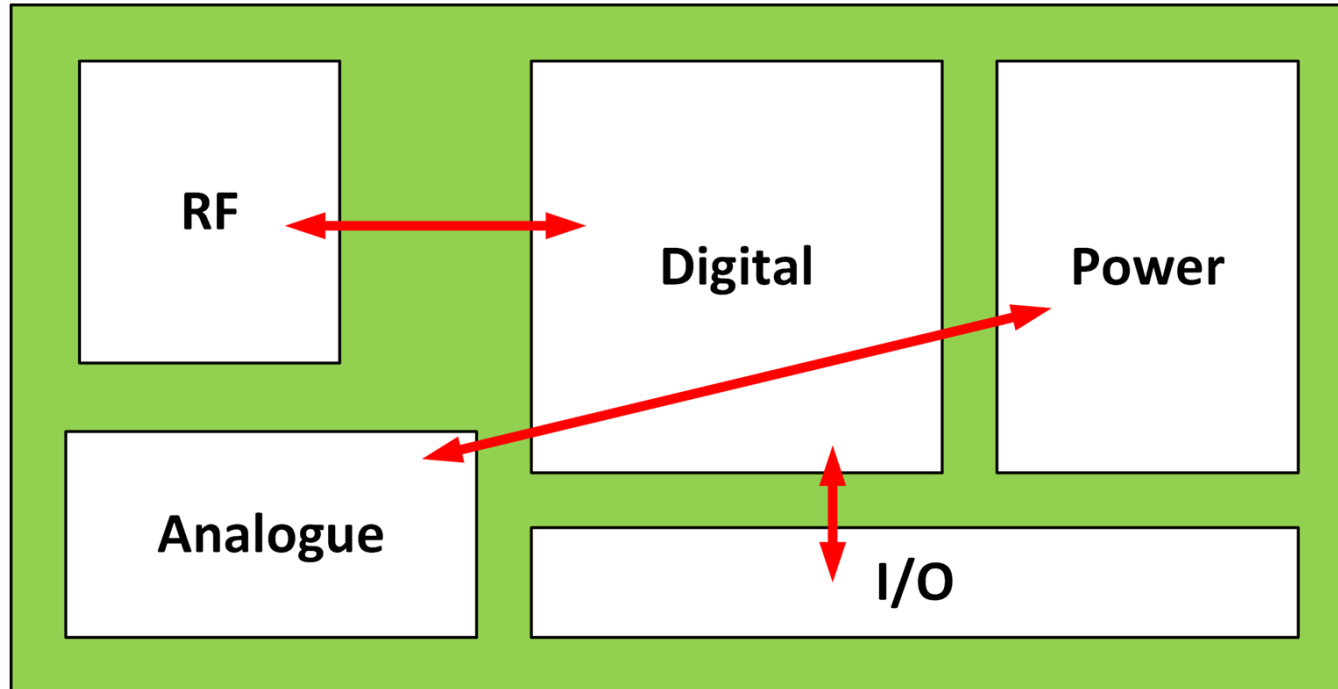


Vertical Partitioning


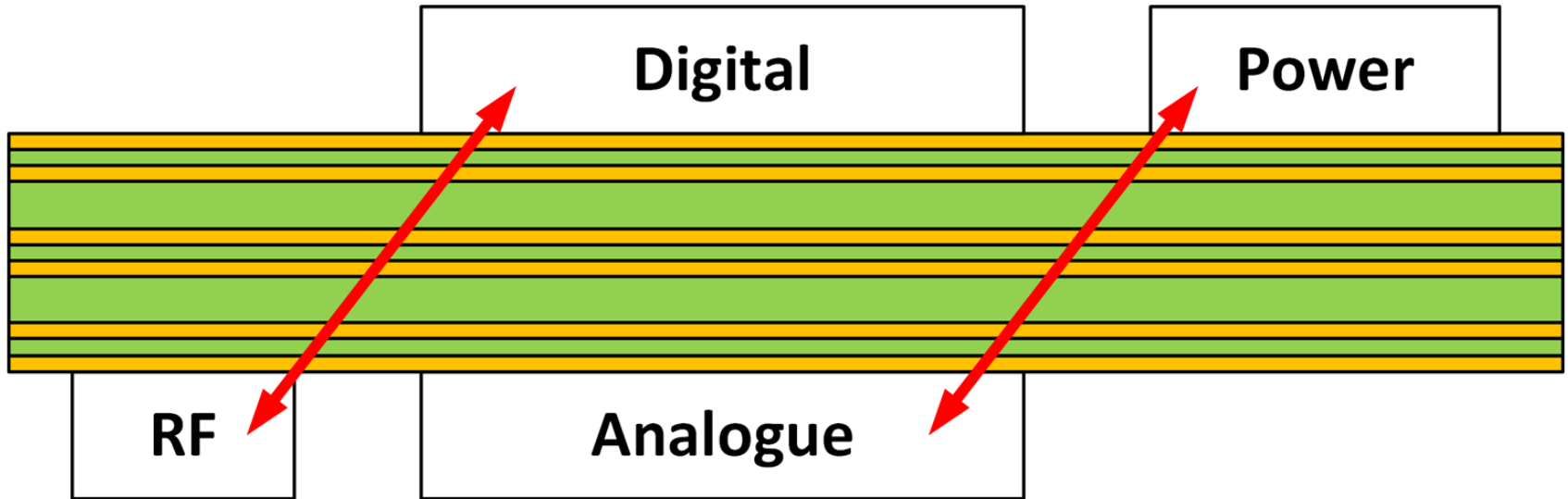


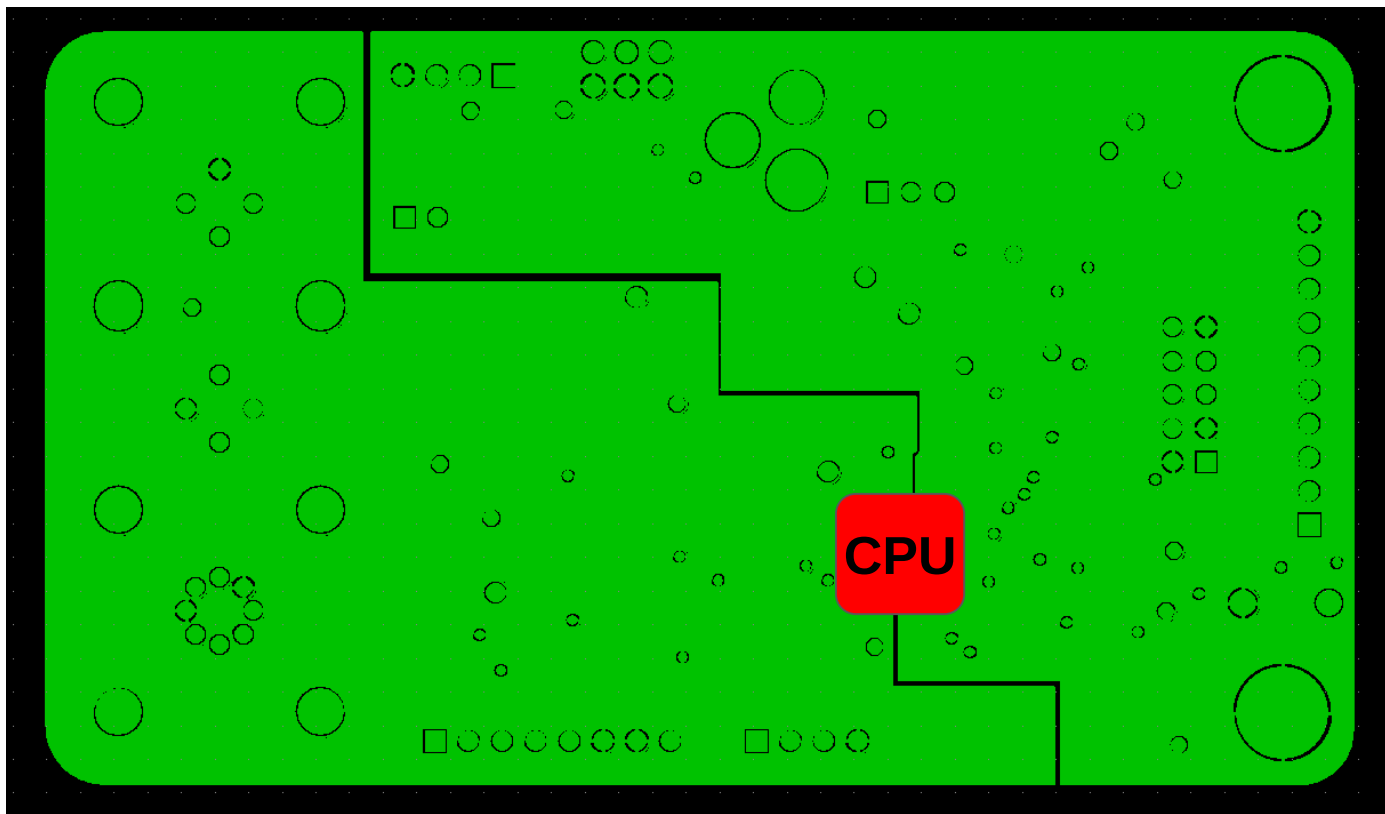

Splitting Grounds

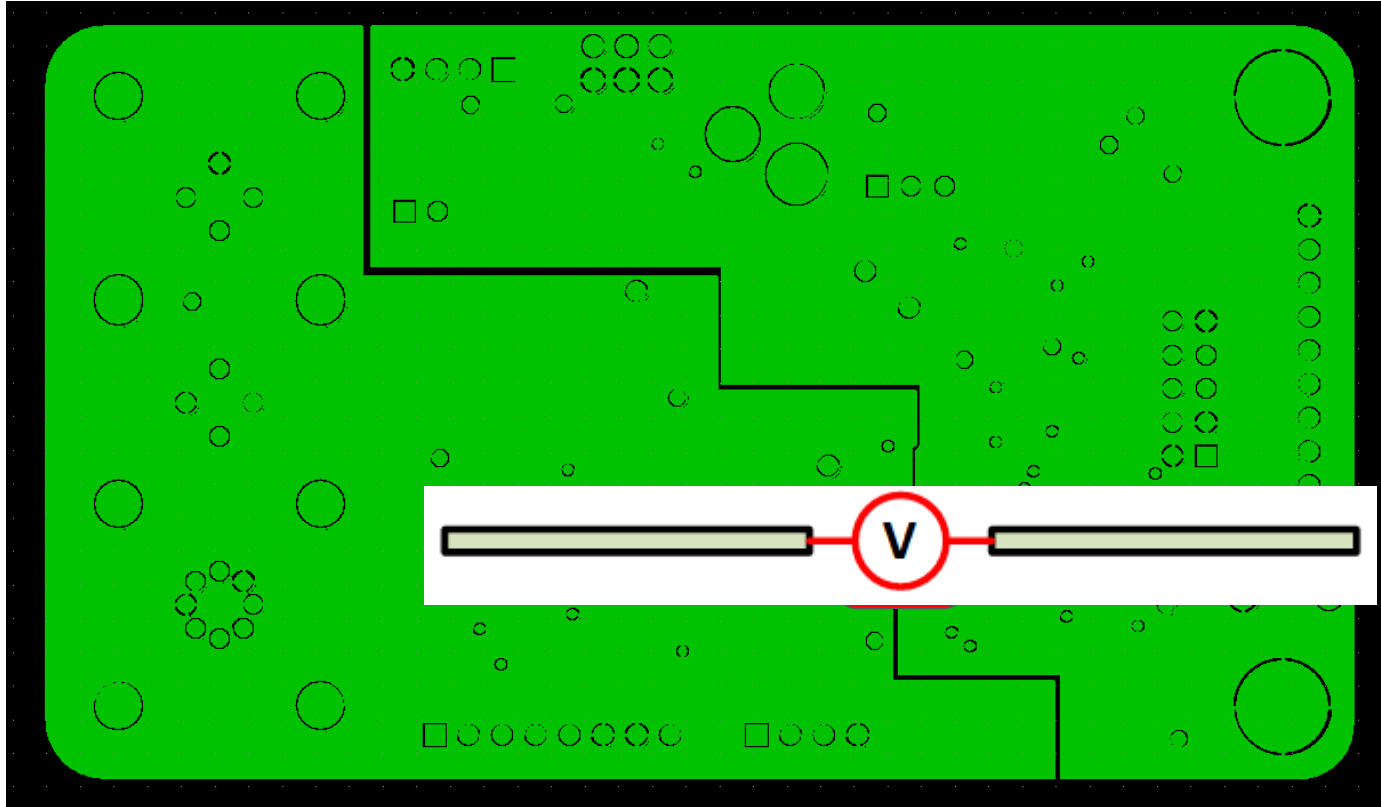

Splitting Grounds

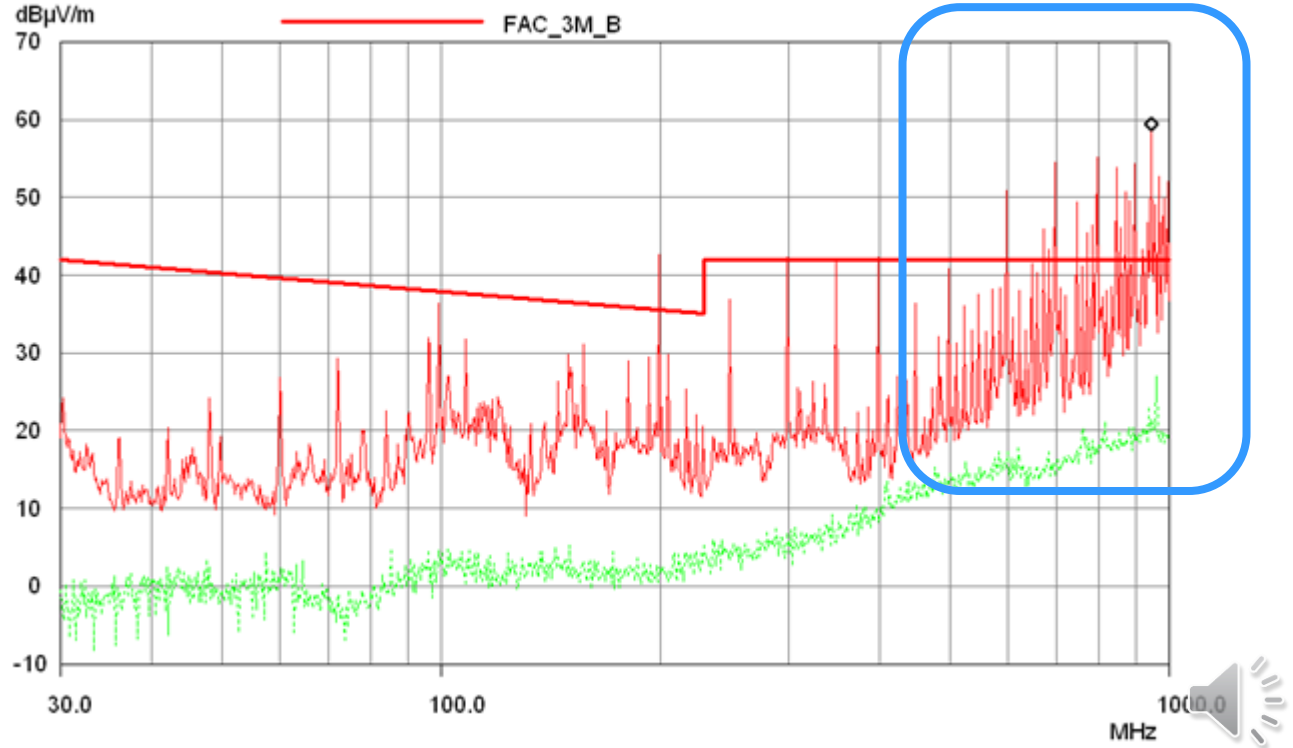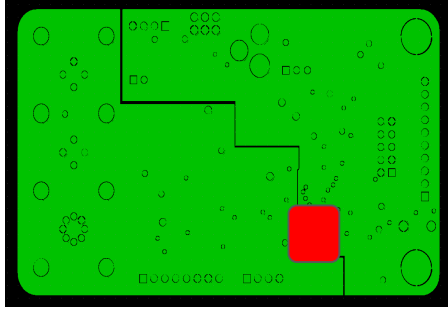



**Q: What do you call an engineer
who splits a ground plane?**





A: A customer





Back down to earth.



Ground vs power as
reference planes in PCBs

Shielding



Decoupling

Resonance in ground

ΔI noise and
ground bounce

Did not cover :(



Ground
maps

Grounding in
larger systems

Hybrid grounds

PCB stackups


...and more 

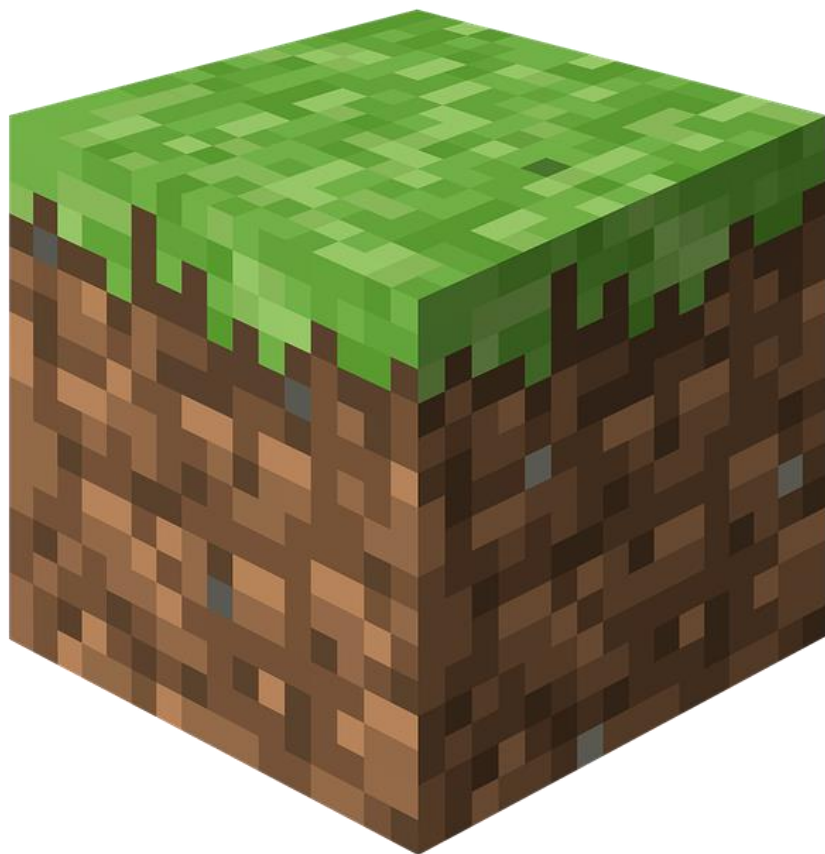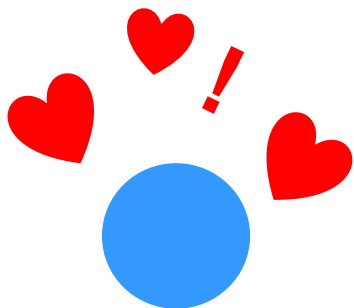

Where does the current flow?



DC

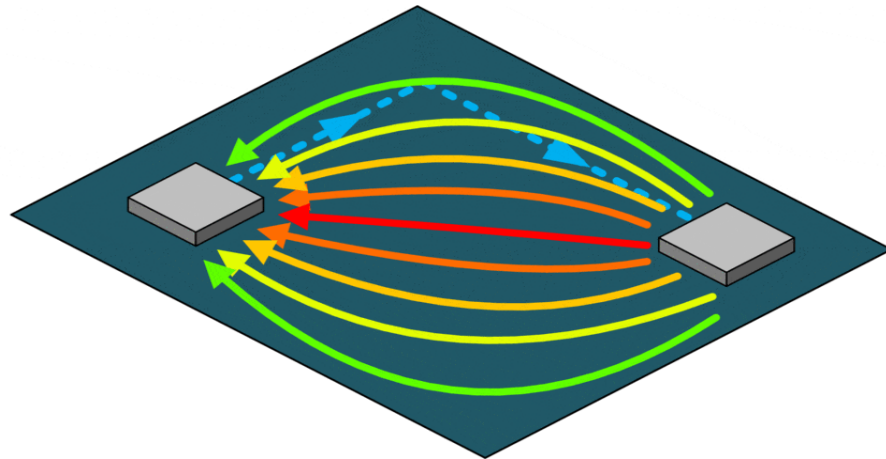



Ambiguity


“Protective Earth”

“DC negative”

“Bond” or “connect x to y”

“PCB ground”



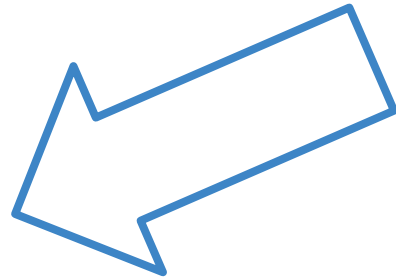

Connect on LinkedIn

@ James Pawson



Thanks :)



Questions?

Come and have a chat > exhibition area

hello @ unit3compliance.co.uk



@ James Pawson

